

3E1147

Roll No. _____

Total No of Pages: **3****3E1147**

B. Tech. III - Sem. (Main) Exam., Dec. - 2018
PCC Electronics & Communication Engineering
3EC4 - 04 Digital System Design
EC, EI

Time: 3 Hours**Maximum Marks: 120****Instructions to Candidates:**

Attempt all ten questions from Part A, selecting five questions from Part B and four questions from Part C.

Schematic diagrams must be shown wherever necessary. Any data you feel missing may suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.

Use of following supporting material is permitted during examination. (Mentioned in form No. 205)

1. NIL2. NILersahilkagyan.com**PART - A****(Answer should be given up to 25 words only)****[10×2=20]****All questions are compulsory**

- Q.1 Write Decimal no. $(125)_{10}$ in BCD. [2]
Q.2 Convert $y = AB + \bar{A}\bar{B}$ (sop) form in equivalent POS form. [2]
Q.3 Define Fan-out of logic system. [2]
Q.4 Write the name of two modeling style in VHDL. [2]
Q.5 Draw the state diagram of any one finite state machine (FSM). [2]
Q.6 Find the total no. of select line, when a 8×1 Mux is implemented using 2×1 Mux. [2]
Q.7 Draw the circuit diagram of any two Dynamic memory cell. [2]
Q.8 Write any one use of tristate logic. [2]
Q.9 Write the name of one Parallel Adder. [2]
Q.10 Write VHDL code for $y = A\bar{B}$ in structural model. [2]

PART - B

(Analytical/Problem solving questions)

[5×8=40]

Attempt any five questions

- Q.1 Derive a minimum cost circuit that implement the function-
 $f(x_1 \dots x_n) = \sum m(4,7,8,11) + D(12,15)$ [8]
- Q.2 Draw the output waveform of a four bit serial in parallel out shift register for six clocks. Assume the Data input is = 10111011... [8]
- Q.3 Implement $y = A + BC$ in ECL logic and explain its working. [8]
- Q.4 How SR FF is converted to JK FF? Draw its circuit diagram and explain. How the JK FF determine output when both $J = K = 1$? [8]
- Q.5 Write VHDL code for a Half Adder in Data flow style. [8]
- Q.6 How Mux is used for implement combinational logic? Implement $y = A + BCD$ using a Mux. <http://www.rtuonline.com> [8]
- Q.7 Draw the general diagram of a single bit serial Adder. Calculate the total delay taken in Addition of two four bit data in it. [8]

PART - C

(Descriptive/Analytical/Problem Solving/Design Question)

[4×15=60]

Attempt any four questions

- Q.1 Draw the 2 input NAND gate using TTL logic and calculate its minimum noise level at input that disturb the true output for $A = B = 0$. Assume the supply is $V_{DD} = 9$ volt. [15]
- Q.2 The state diagram of a FSM is given below, design its logic (fig-2(c)) [15]

 


fig - 2(c)

Show its state table, state assignment table and final implemented logic.

Q.3 Draw the state diagram for the logic circuit shown in fig 3(c).

[15]

 


fig - 3(c)

Q.4 Design a 4 bit synchronous down counter using D-FF. Draw its state diagram and all design tables.

[15]

Q.5 How FPGA are used for logic implement? Show the OR and AND Space for a 2 variable input. Also show the connection in FPGA for implement $y = \bar{A} \bar{B}$ in it.

[15]