

6E6053

Roll No. _____

Total No of Pages: **3****6E6053**

B. Tech. VI-Sem. (Back) Exam., October - 2020
Electronic Instrumentation & Control Engineering
6EI3 (O) Industrial Electronics
AI, EC, EI

Time: 2 Hours**Maximum Marks: 48**www.ersahilkagyan.com**Min. Passing Marks: 16***Instructions to Candidates:*

Attempt three questions, selecting one question each from any three unit. All Questions carry equal marks. (Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly. Units of quantities used/ calculated must be stated clearly. Use of following supporting material is permitted during examination. (Mentioned in form No.205)

1. NIL2. NIL**UNIT-I**

- Q.1 (a) Illustrate the basic layered structure, construction and transistor analogy of Silicon Controlled Rectifier. [8]
- (b) Discuss the differences between forward and reverse blocking mode of SCR. [8]

OR

- Q.1 (a) Briefly explain various triggering methods used for thyristor. [8]
- (b) Explain the following for IGBT, FET and MOSFET – [8]
- (i) Operation mode
 - (ii) Input/ output Impedance
 - (iii) Amplification
 - (iv) Switching property

UNIT- II

Q.2 A single phase bridge rectifier is connected to 240 V_{rms}, 60Hz source. The output of the rectifier is connected to 20 ohm resistor load. If the average output voltage is 40% of the maximum output voltage, determine – [16]

- (a) The delay angle α
- (b) The rms & average output current
- (c) The average & rms thyristor current
- (d) The input power factor

OR

Q.2 What is an Inverter? List a few industrial applications of inverters. Explain its principle of operation with the aid of diagram. [16]

UNIT- III

Q.3 (a) Distinguish between Buck-Boost and Boost converters. Give typical applications. [8]

(b) What is a dual converter? For simultaneous operation of single phase dual converters, find the relationship between firing angle α_1 and α_2 . [8]

OR

Q.3 (a) Describe the principle of step-down chopper with different waveforms. [8]

(b) Derive an expression for the average output voltage in terms of input d.c. voltage and duty cycle. [8]

UNIT- IV

Q.4 (a) Discuss the speed-torque curves for a chopper controlled induction motor. [8]

(b) Explain in various schemes of d.c. motor speed control with their specific applications & limitations. [8]

OR

- Q.4 (a) Draw and explain the operation of a speed control of d.c. series motor by a single phase full converter for continuous motor control. Draw a neat diagram along with associated voltage & current waveforms. [8]
- (b) On the basis of 'four quadrant' operation and configuration, explain the working of a dc-dc chopper. [8]

UNIT- V

- Q.5 (a) Identify the major constructive difference between a permanent magnet and variable reluctance type motor. [8]
- (b) A step motor has 130 steps per resolution. Find the input digital pulse rate that produces continuous rotation at a speed of 10.5 revolutions/sec. [8]

OR

- Q.5 (a) Distinguish between the terms full stepping and half stepping. [8]
- (b) Explain with schematic diagram, open loop & closed loop control schemes used for stepper motor. [8]
-