

## DC circuit

### Introduction :-

Q. What is electrical engineering?

Ans. Electrical engineering is a branch of engineering which deals with the aspect of electrical energy, its system, component & devices. Every equipment & component of an electrical system can be represented by an equivalent electrical network which consists of a very few elements such as energy source, resistor, capacity & inductors.

\* Electric Current  $\Rightarrow$  It is the rate of flow of charges w.r.t. time.

$$I = \frac{dQ}{dt}$$

\* Electric potential  $\Rightarrow$  It is the amount of work done required to move a unit positive charge b/w two points

$$V = \frac{W}{q} \quad (\text{Unit - Volts})$$

\* Electro motive force  $\Rightarrow$  It is the force or voltage that drives an electric current to flow in an electric circuit.

Electric power  $\Rightarrow$  It is the rate of doing work per unit time.

$$P = \frac{W}{t} = VI = I^2 R$$

\* Ohm's Law :- A current flowing through the conductor is directly proportional to the potential applied across its ends with the physical condition that is temperature, pressure, Resistance etc.  $I \propto V$

$$[V = IR]$$

Resistance :- It is the properties of the conductor by which it oppose the flow of current.

$$[R = \frac{\rho l}{A}]$$

Inductance :- It is the properties of the conductor by which change in the current through it induces & EMF.

$$[V = L \frac{di}{dt}]$$

$$[L = \frac{\mu N^2 A}{l}]$$

Capacitance :- It is the ability of a conductor to store electric charge

$$[C = \frac{Q}{V}]$$

[Unit -  $\text{F}$  or  $\text{C/V}$ ]

Basic circuit elements :-

- 1.) Active elements  $\Rightarrow$  The circuit elements which supply energy to the circuit is known as Active elements.  
eg - Battery, generator, cells etc.

2) Passive element  $\Rightarrow$  The elements which either dissipate or store energy are known as passive.

eg- Register, capacitor etc.

3) Linear element  $\Rightarrow$  The elements whose output is directly proportional to the input are said to be linear element.

eg- pure register, inductor, capacitor etc.

4) Non Linear element  $\Rightarrow$  The elements which are not linear are called non-linear.

eg- Diode  $\cdot$  Diode.

5) Bilateral element  $\Rightarrow$  Elements whose conduction of current are in both the directions.

eg- register, capacitor, inductor.

6) Unilateral element  $\Rightarrow$  Elements whose conduction of current is only one direction.

eg- Diode, transistor etc.

7) Lumped element  $\Rightarrow$  Elements which are pure and physically separable.

eg- pure register, inductor, capacitor etc.

8) distributed element  $\Rightarrow$  Distributed element are the elements which are not pure and can not be separated physically.

eg- transmission line.

\* Faraday's First Law  $\Rightarrow$  When ever the conductor cuts the magnetic flux line and emf is induced in conductor.

\* Faraday's second Law  $\Rightarrow$  The magnitude of induced emf in a conductor is directly proportional to the rate of change of flux linkage.

\* Lenz's Law  $\Rightarrow$  According to this Law and induced emf will give rise to a current whose magnetic field opposes the change in original magnetic field.

**Energy Source** :- Energy sources may be some time called as network sources as these sources provide necessary excitation to an electric network. There are two types of energy source :-

- Voltage Source
- Current Source

Further these sources classified as ideal and practical and dependent and independent

Ideal

\* Voltage Source :- It is an energy source

whose terminal voltage is constant and independent of current

thought it.

2) **Ideal current source** :- It is energy source which can supply a constant magnitude of current irrespective of the voltage across its terminal.

3) **Practical Voltage source** :- It can be represented by an ideal voltage in series with an internal resistance ~~'r'~~. This resistance accounts for the drop in voltage across its terminals.

4) **Practical Current source** :- It can be represented by an ideal current source in parallel with an internal resistance 'r'.

5) **Dependent energy source** :- Dependent energy sources are the sources whose output depends on the voltage or current of certain elements of the network in which they are connected.

\* Network Analysis  $\Rightarrow$

Voltage Divider Rule :-




$$V_1 = \frac{V \times R_1}{R_1 + R_2}$$

$$V_2 = \frac{V \times R_2}{R_1 + R_2}$$


## Current Divider Rule :-

$$I_1 = \frac{V_1}{R_1 + R_2}$$

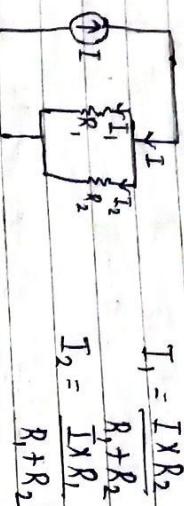

Kirchoff's Law :-

$\rightarrow$  KCL :-

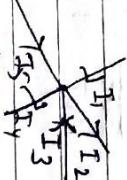


According to this Law in an electric circuit the algebraic sum of all the current meeting at a point is equal to zero.

$$I_1 - I_2 + I_3 - I_4 + I_5 = 0$$

$$I_1 + I_3 + I_5 = I_2 + I_4$$


NOTE →

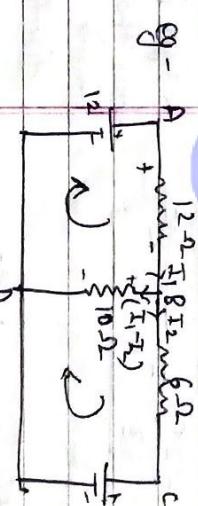\* KV L :- According to this law the algebraic sum of all the voltages in a closed path is equal to zero.



$$\begin{aligned} & V_1 - V_2 + V_3 - V_4 + V_5 = 0 \\ & -V_1 + V_2 - V_3 + V_4 - V_5 = 0 \end{aligned}$$

## NETWORK ANALYSIS :-

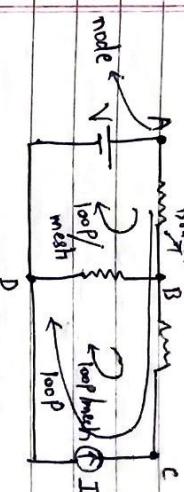

(i) NODE :- A node is the point at which two or more circuit elements are interconnected.

(ii) Branch :- A branch is a part of a network which lie b/w two points or nodes.

(iii) Loop :- A loop in a network is any closed conducting part path through two or more elements of the network.

(iv) mesh :- A mesh is the most elementary form of a loop which can not be further divided.

Apply KV L in ABDAB loop :-

$$12 - I_1 \times 12 - (I_1 - I_2)(10) = 0$$

$$12 - 22I_1 + I_2 \times 10 = 0$$

$$10I_2 + 12 = 22I_1$$

$$\begin{aligned} & \frac{V_3}{10} - \frac{V_4}{10} = I_1 - I_2 \\ & \frac{V_4}{10} - \frac{V_5}{10} = I_2 - I_1 \end{aligned}$$

$$5I_2 + 6 = 11I_1 \quad \text{--- (1)}$$



$$\begin{aligned} I_3 &= 2I_1 - 2I_1 - 2I_2 + 2 \cdot 2 \\ I_3 &= 4I_1 - 2I_2 + 2 \cdot 2 \\ I_3 + 22 &= 4I_1 + 2I_2 \\ 2 - I_1 - I_2 + 24 &= 4I_1 + 2I_2 \quad (4) \\ 3I_2 + 5I_1 &= 26 \end{aligned}$$

$$\begin{cases} I_1 = I_2 + 2 \\ 3I_2 + 5I_1 = 26 \end{cases}$$

$$3I_2 + 5(I_2 + 2) = 26 \Rightarrow I_2 = 2 \text{ A}$$

$$8I_2 = 16 \Rightarrow I_1 = 4 \text{ A}$$


$$I_3 = 2 - 2 - 4 \Rightarrow I_3 = 4 \text{ A}$$

$$I_4 = I_1 + I_2 - 11 = -5 \text{ A} = I_4$$


$$I_1 = \frac{V}{R_1} = V \times G_1$$

$$I_3 = \frac{I}{R_3} \times G_3$$

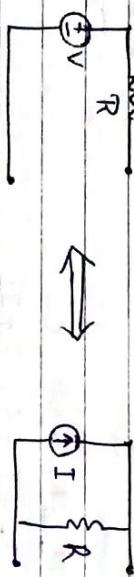
Voltage - current source change  $\Rightarrow$


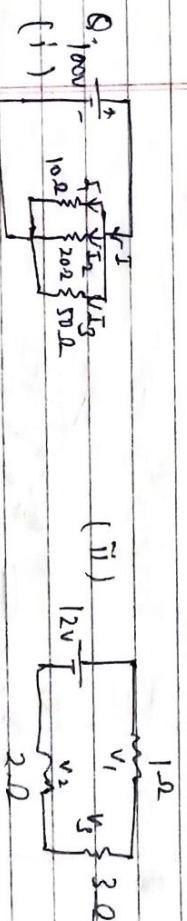
$$\text{Q100N} \quad \text{(ii)} \quad I = \frac{V_{12}}{10 \Omega} = \frac{12V}{10 \Omega} = 1.2 \text{ A}$$



Series parallel network:-

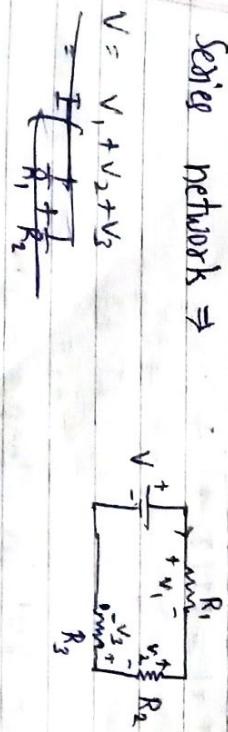

(W)

I1 =

$\frac{I}{G_{\text{eq}}}$

=

$\frac{V}{R_{\text{eq}}}$

=

$\frac{V}{100}$

=


1.2

A

1.2

20/IV 2.5 2.2

DATE: / /  
PAGE NO.:

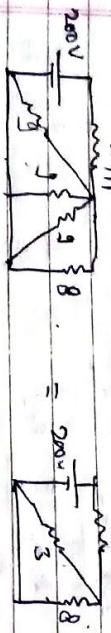


$$\frac{94}{11} + \frac{20}{11} = \frac{114}{11} = 4.$$

$$R_{eq} = 4\Omega \quad R_4 = 4\Omega$$

$$V = IR = 4 \times 10 = 200$$

$$I = 50A$$

### Star - Delta Transformation :-

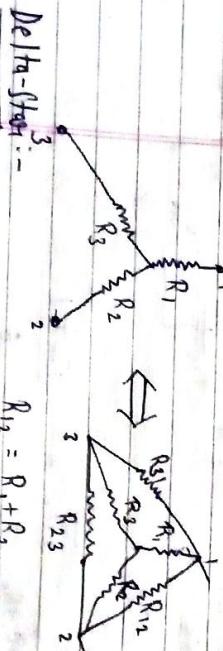

Delta - Star :-

$$R_{12} = R_1 \| (R_2 + R_3)$$

$$R_1 + R_2 = \frac{R_{12}}{R_{12} (R_{23} + R_{31})} \quad (1)$$

$$R_{12} + R_{23} + R_{31} = \frac{R_{12} (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad (2)$$

$$R_3 + R_1 = \frac{R_{12} (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad (3)$$

Adding - ①, ② & ③

$$R_1 + R_2 + R_3 = \frac{R_{12} R_{23} + R_{23} R_{31} + R_{31} R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$R_{12} + R_{23} + R_{31} = \frac{R_{12} R_{23}}{R_{12} + R_{23}}$$

$$R_{31} = \frac{R_{12} R_{23}}{R_{12} + R_{23}}$$

Star - Delta :-

$$R_{12} = R_1 + R_2 + \frac{R_2 R_3}{R_3}$$

$$R_{31} = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$

$$R_{12} = 2.5, \quad R_{23} = 1, \quad R_{31} = 1.5$$


$$R_1 = \frac{2.5 \times 1.5}{2.5 + 1.5} = 1.5$$

$$R_2 = \frac{2.5 \times 1.5}{2.5 + 1.5} = 1.5$$

$$R_3 = \frac{2.5 \times 1.5}{2.5 + 1.5} = 1.5$$

$$R_2 = \frac{2.5}{5} = 0.5, \quad R_3 = \frac{1.5}{5} = 0.3$$

$$R_1 = \frac{1.5}{5} = 0.3$$

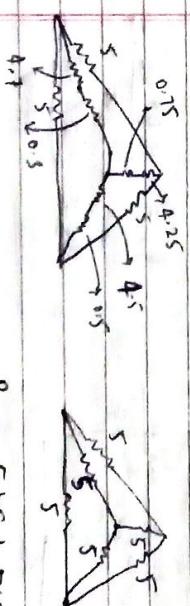

$$R_{12} = 5 + 5 + \frac{5 \times 5}{5} = 15$$

$$R_1 = \frac{1}{3} + \frac{1}{15} = \frac{4}{15} \Rightarrow R_1 = \frac{15}{4} = 3.75$$

$$R_2 = \frac{1}{3} + \frac{1}{7.5} = \frac{10}{15} = \frac{2}{3}$$

$$R_3 = \frac{1}{15} = \frac{1}{15} = 0.066$$

Ans

$$R_{eq} = \frac{75}{30} = 2.5 \Omega$$


$$R_{eq} = 30 + \frac{575}{12} = \frac{360+575}{12} = \frac{935}{12} = 77.9 \Omega$$

6.   $R_{eq} = ?$


$$R_1 = \frac{30 \times 20}{100} = 6$$

$$R_2 = \frac{50 \times 30}{100} = 15$$

$$R_3 = \frac{50 \times 20}{100} = 10$$

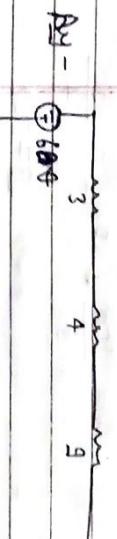7.  find current through 4 ohm resistor  
using source conversion.

$$I = \frac{33}{16}$$

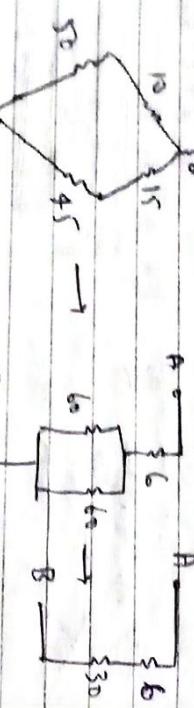


$$R_{eq} = 36 \Omega$$

9. 

$$R_1 = \frac{100 \times 60}{200} = 30$$


$$R_2 = \frac{40 \times 100}{200} = 20$$


$$R_3 = \frac{60 \times 40}{200} = 12$$

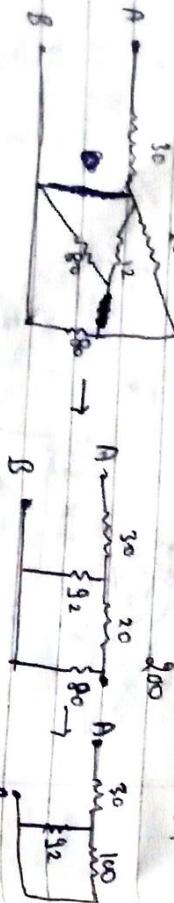10. 

$$\nabla_{xy} = 4x - \left(-\frac{5}{6}\right) - 2 + \left(-\frac{10}{7}\right) = \frac{30}{6} - \frac{24}{7} = \frac{140 - 168}{42} = \frac{-108}{42}$$

$$= -\frac{25}{7} = -\frac{64}{42} = -\frac{32}{21} = -1.5$$

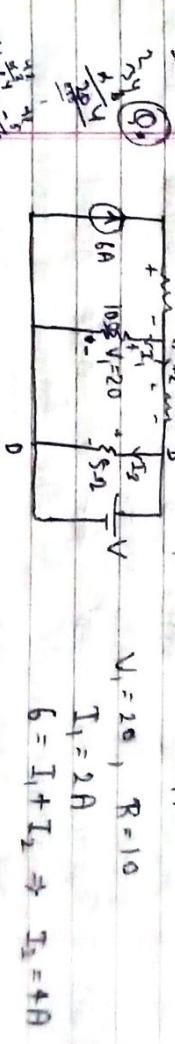Q. 

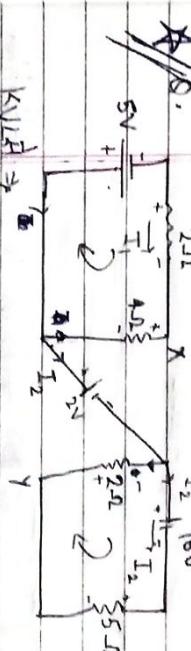

$$\nabla_1 = 20, R = 10$$


$$I_1 = 2A$$

$$I_2 = 2A$$

$$I_B = I_1 + I_2 \Rightarrow I_B = 4A$$

$$-I_2 - \nabla_{BD} + 20 = \nabla_{BD} = 20 - \frac{8}{\sqrt{10}} = \frac{\sqrt{100} - 8}{\sqrt{10}} = 12V$$

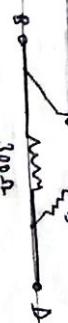Q. Case-I when C & D are short.  
Case-II when C & D are open.



(I)  $\frac{1}{R} = \frac{1}{300} + \frac{1}{300} = \frac{8}{300}$   
 $R = \frac{300}{8} = 37.5\Omega$



$$R = \frac{1500}{8} = 187.5\Omega$$

$$37.5\Omega$$

$$\boxed{V = 10 \text{ Volt}}$$

(II)

$$R = 400\Omega$$

Solve  $\rightarrow$  To KCL Rule:- (At node 1)  
 $I = I_1 + I_2$   
 $I = \frac{V_1}{10} + \frac{V_1 - V_2}{10} = 2V_1 - V_2 = 10 \rightarrow ①$

At node 2

$$I_3 + I_4 = I_2$$

$$\frac{V_2 + 10}{20} + \frac{V_2 - V_3}{20} = \frac{V_1 - V_2}{10} \Rightarrow V_2 + 10 + V_2 - V_3 = 2V_1 - 2V_2$$

$$4V_2 + 10 = 2V_1 + V_3$$

$$8V_1 - 40 + 10 = 2V_1 + V_3$$

$$I_4 + 0.5 = I_5$$

$$\frac{V_2 - V_3}{20} + 0.5 = \frac{V_3}{20}$$

$$6V_1 = V_3 + 30 \quad ②$$

$$\sqrt{2} - \sqrt{3} + 10 = \sqrt{3}$$


$$\sqrt{2} + 10 = 2\sqrt{3} \quad ③$$

$$2\sqrt{1} - 10 + 10 = 2\sqrt{3}$$

$$\boxed{\sqrt{3} = \sqrt{3}}$$

$$6V_3 = \sqrt{3} + 30 \quad \boxed{V_3 = 6}$$


$$V_1 = V_3 = 6 \text{ Volt}$$

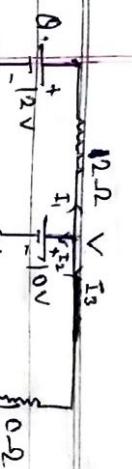

node A KCL  
 $I_1 + I_2 + I_3 = 0$   
 $\frac{V - 10}{10} + \frac{V}{10} + \frac{V}{10} = 0$   
 $V - 60 + 10V - 100 + V = 0$

$$10$$

$$5V - 60 + 10V - 100 + V = 0$$

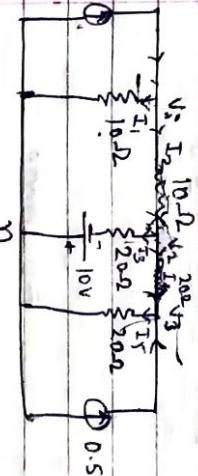

node A KCL  
 $I_1 + I_2 + I_3 = 0$   
 $\frac{V - 10}{10} + \frac{V - 10}{10} + \frac{V}{10} = 0$   
 $V - 60 + 10V - 100 + V = 0$

- (i) Identify all the nodes in the network and assume one node as a reference node.  
 Assume node voltages at each node except the reference one/ node because voltage of reference node is zero volt.  
 Right KCL eqn for all node except the reference node in the form of node voltage and solve them.
- 'n' mode  $\Rightarrow R_{eqn} [n-1] \text{ step}$

$$6V_3 = \sqrt{3} + 30$$

$$2\sqrt{1} - 10 + 10 = 2\sqrt{3}$$

$$\boxed{\sqrt{3} = \sqrt{3}}$$

$$V_2 = 2\sqrt{3} + 10$$

$$3V_2 - \frac{664}{91} = 18 \Rightarrow 3V_2 = 18 + \frac{664}{91}$$

$$\boxed{V_2 = 16.5 \text{ V}}$$

$$= 16.5 \text{ V} \text{ O.H.S}$$

Apply KCL at node 1

$$\frac{V_1 - e_1}{R_1} + \frac{V_1 + e_2 - V_2}{R_5} = 0$$

At node 2

$$\frac{V_2 - e_2 - V_1}{R_2} + \frac{V_2 + e_3}{R_3} + \frac{V_2 + e_4}{R_4} = 0$$

At node 1

$$\frac{V_1 + 1 - V_3}{R_1} + \frac{V_1 - V_3}{R_3} + \frac{8}{R_2} = 0$$



$$\frac{V_1 - 8}{R_1} = 1/4$$

$$V_1 = 16.5$$

At node 1

$$\frac{V_1 - V_2}{R_1} + \frac{V_1 - V_2}{R_5} + \frac{V_1 - V_2}{R_2} = 0$$

$$\frac{V_1 - V_2}{R_1} = 1/4$$

$$V_1 = 16.5$$

$$3V_1 + 3V_2 - 3V_2 + 4V_1 - 4V_3 + 8 = 0$$

$$7V_1 - 3V_2 - 4V_3 + 11 = 0 \quad \text{--- (1)}$$

At node 2 :

$$\frac{V_2 - 1 - V_3}{R_2} + \frac{V_2}{R_3} + \frac{V_2 - V_3}{R_4} = 0$$

$$3V_2 + 3V_3 - 3V_2 - 2V_3 - V_3 = 0$$

$$3V_3 - 3V_2 = 0 \quad \text{--- (2)}$$

$$\frac{V_3 - V_1}{R_3} + \frac{V_3 - V_2}{R_4} + \frac{V_3 - V_2}{R_5} = 0$$

$$3V_3 + 3V_2 - 3V_1 - 2V_2 - V_2 = 0$$

$$3V_3 - 3V_1 - 2V_2 = 0 \quad \text{--- (3)}$$

$$\frac{V_2 - V_1}{R_2} + \frac{V_2 - V_2}{R_4} = 4$$

$$\frac{2V_2 - 2V_1 + V_2 - 2}{4} = 4 \Rightarrow 3V_2 - 2V_1 = 18 \quad \text{--- (2)}$$

$$V_2 = \frac{18 + 2V_1}{3}$$

$$3V_1 - \frac{1}{3} \left( \frac{18 + 2V_1}{3} \right) = 24.2$$

$$3V_1 - 90 - 10V_1 = 24.2$$

$$21V_1 = 332$$

$$V_1 = \frac{332}{21} = 15.8$$

$$14V_1 - 3 \left( \frac{3V_1 + 2V_3 + 3}{4} \right) - 4V_3 + 11 = 0$$

$$14V_1 - \frac{9}{4} (3V_1 + 2V_3 + 3) - 4V_3 + 11 = 0$$

$$14V_1 - 3V_1 - 2V_3 - 3 - 8V_3 + 22 = 0$$

$$11V_1 - 10V_3 = -19 \quad \text{--- (4)}$$

from eqn - (3)  
 $\frac{1}{2}V_3 - 4V_1 - 25 = 2V_2$

$$7V_1 - 3\left(\frac{11V_3 - 4V_1 - 25}{2}\right) - 4V_3 + 11 = 0$$

$$\begin{aligned} 14V_1 - 33V_3 + 12V_1 + 75 - 8V_3 + 22 &= 0 \\ 26V_1 - 41V_3 &= -97 \quad \text{---(5)} \\ 41V_3 - 26V_1 &= 97 \end{aligned}$$

$$410V_3 - 260V_1 = 970$$

$$(eqn-4) \quad \frac{-410V_3 + 451V_1}{-410} = -779$$

$$19V_1 = 191$$

$$\boxed{V_1 = 1}$$

$$\begin{aligned} V_3 &= \frac{-19 - 11}{-10} = 3 \quad \boxed{V_3 = 3} \\ \frac{11}{10} & \\ \frac{15}{10} & \\ \frac{15}{10} & \\ \frac{15}{10} & \end{aligned}$$

$$7 - 3V_2 - 12 + 11 = 0$$


$$\boxed{V_2 = 2}$$

\* Mesh current method  $\Rightarrow$  This method is based

method instead of assuming branch current mesh currents are assumed with do which do not split but complete their path around the mesh.

Step to solve current using mesh analysis  
 i) Identify all the mesh and assume mesh current in any direction.

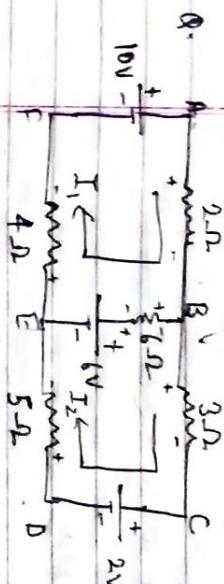2/1 Write KVL eqn for each mesh and solve it.  
 Note  $\rightarrow$  This method is not applicable in a mesh containing current source.



In mesh ABFA

$$\begin{aligned} -2I_1 - 6I_1 - 6 - 4I_1 + 10 + 6I_2 &= 0 \\ 6I_2 - 12I_1 + 4 &= 0 \quad \text{---(1)} = 3I_2 - 6I_1 - 2 = 0 \\ 6I_1 - 14I_2 + 4 &= 0 \\ 3I_1 - 7I_2 &= -2 \quad \text{---(2)} \times 4 \end{aligned}$$


In mesh BCDEB

$$\begin{aligned} 2I_2 - 4I_1 &= 9I_2 - 18I_1 = -6 \\ 4I_2 + 18I_1 &= 12 \\ -33I_1 &= -18 \quad \text{---(3)} \end{aligned}$$

$$2I_1 - 2I_2 = -8$$

$$\begin{aligned} 12I_1 - 6I_2 &= 4 \\ -2I_2 &= -12 \quad \boxed{I_2 = \frac{6}{11}} \end{aligned}$$

$$I_1 = \boxed{\frac{20}{33}}$$

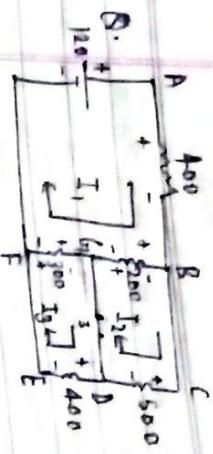

In mesh ABCDA

$$120 - 400I_1 - 200I_2 - 300I_3 + 200I_2 + 300I_3$$

$$\text{In } \Delta \text{ of } I_3 - I_2 = -0.048 + 0.072 = 0.024$$

(node method)

$$120 + 200I_2 + 300I_3 = 300I_1 \quad \text{--- (1)}$$

In mesh BCDEF

$$-500I_2 - 200I_3 + 200I_1$$

$$200I_1 = 700I_2 \quad \text{--- (2)}$$

In mesh CDEF

$$-400I_3 - 300I_2 + 300I_1 = 0$$

$$3I_1 = 7I_3 \quad \text{--- (3)}$$

$$I_1 = \frac{7}{3}I_3 \quad \text{--- (4)}$$

$$120 + 200I_2 + 300 \times \frac{2}{3}I_2 = 300 \times \frac{7}{3}I_3$$

$$120 + 400I_2 + 900I_2 = 6300I_3$$

$$I_1 = 0.048$$

$$5000 \cdot I_1 = \frac{6065}{160} = 37.90625$$

$$I_1 = \frac{7}{2} \times 0.048 = 7 \times 0.025 = 15.75$$

$$|I_1| = 0.168$$

$$I_3 = \frac{3}{2} \times 0.048 = 3 \times 0.024 = 0.072$$

$$I_3 = \frac{3}{2} \times 0.048 = 3 \times 0.024 = 0.072 = I_3$$

(node method)



In mesh ABCFDA

$$144 - 3I_1 - 4I_2 - 2I_3 + 4I_2 + 2I_3$$

$$144 + 2I_3 = 9I_1 + 4I_2 \quad \text{--- (1)}$$

In mesh CDEF

$$-2I_2 - 2I_3 - 12I_3 + 2I_1 + 4I_2$$

$$8I_2 + 2I_1 = 22I_3 \quad \text{--- (2)}$$

In mesh BCDEA

$$-4I_3 - 4I_2 - 8I_3 + 4I_1 + 2I_2 = 0$$

$$-4I_3 - 4I_2 - 4I_1 + 8I_3 = 16I_2 \quad \text{--- (3)}$$

$$\text{in eqn (1)} \quad I_1 + 2I_2 + 4I_3$$

$$144 + 4I_3 - I_1 = 3I_1 + 4I_2 \quad (\text{from eqn (2) } - 2I_2)$$

$$10I_1 = 144$$

$$I_1 = 14.4$$

$$(2I_1 = \frac{16I_2 - 4I_3}{2})$$

$$I_3 = 4I_2 - 4I_1 = 22I_2 + 8I_1$$

$$I_3 = 4I_2 - 4I_1 = 22I_2 + 8I_1$$

$$\text{from eqn } ② + ③ \\ 2I_1 + 4I_3 = 22I_3 - 2I_1 \\ I_1 = \frac{18}{4} I_3 = \frac{9}{2} I_3 \quad (4)$$

$$\text{from eqn } ① + ③ \\ 14V_1 - 11I_1 + 11I_3 - I_1 + 2I_3 = 0$$

$$14V_1 + 13I_3 = 10I_1 \Rightarrow 288 = (90 - 26)I_3 \\ 14V_1 + 13I_3 = 90I_3$$


$$I_3 = 4.5 \quad I_1 = \frac{9}{2} \times 4.5 = 20.25 \\ I_1 = 20.25$$

In eqn ③

$$2I_1 + 4I_3 = 8I_2 \\ 2(20.25) + 4(4.5) = 8I_2 \\ 40.5 + 18 = 8I_2 \\ \frac{58.5}{8} = I_2 \Rightarrow I_2 = 7.31$$

$$\text{In 'E3' Branch} \\ V = I_3 \times R = 4.5 \times 12 = 54 \text{ Volt}$$

node method :-

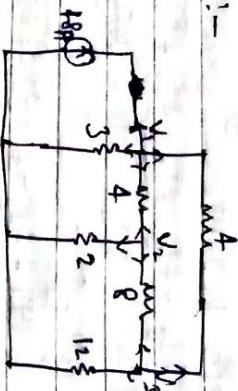

At node 1

$$\frac{V_1 - V_2}{4} + \frac{V_1 - V_3}{4} + \frac{V_1}{3} = 4.8$$

$$3V_1 - 3V_3 + 3V_1 - 3V_2 + 4V_1 = 576 \\ 10V_1 - 3V_2 - 3V_3 = 576 - ①$$

At node 2

$$\frac{V_2 - V_1}{4} + \frac{V_2 - V_3}{8} + \frac{V_2}{2} = 0$$

$$2V_2 - 2V_1 + V_2 - V_3 + 4V_2 = 0 \Rightarrow 7V_2 = 2V_1 + V_3 - ②$$

At node 3

$$\frac{V_3}{12} + \frac{V_3 - V_2}{8} + \frac{V_3 - V_1}{4} = 0$$

$$2V_3 + 3V_3 - 3V_2 + 6V_3 - 8V_1 = 0 \Rightarrow 11V_3 = 3V_2 + 6V_1 - ③$$

$$\text{In eqn } ②, ③ \\ 2V_2 - 6V_1 = 3V_3 \\ 3V_2 + 6V_1 = 11V_3$$

$$\frac{9V_2}{14} = V_3 \Rightarrow \frac{12}{7}V_2 = V_3 \\ \Rightarrow V_2 = \frac{7}{12}V_3$$

$$10V_1 - 3V_2 - \frac{3V_2}{4} = 576 \\ 10V_1 - 3V_2 - \frac{3V_2}{4} = 576 \\ 10V_1 - \frac{15}{4}V_2 = 576 \\ 40V_1 - 15V_2 = 2304$$

$$40V_1 - 19V_3 = 2304 - ④ \\ \frac{12}{7}V_2 V_3 = 24V_1 + V_3$$

$$(49 - 12)V_3 = 24V_1$$

$$37V_3 = 24V_1 \quad V_1 = \frac{37}{24}V_3$$

$$\frac{12V_5}{40 \times 37} - 19V_3 = 2304$$

$$\left(\frac{3V_5}{12} - 19V_3\right) V_3 = 2304$$

$$V_3 = \frac{2304}{128}$$

31/8/18

Network Theorem  
Superposition theorem  $\Rightarrow$

In a linear resistor network containing two or more energy sources, the total current in

any part of a circuit is equal to the algebraic sum of all the currents produced by each source separately


Steps for solving superposition theorem  $\Rightarrow$

- Take any one of the independent voltage or current source. Replace the other energy sources by their internal resistances that is voltage sources become short circuited and current sources become open circuited.


- Obtain various branch current.
- Repeat the above two step for each of the independent energy sources.

- At all the currents obtain in each branch for individual energy source.

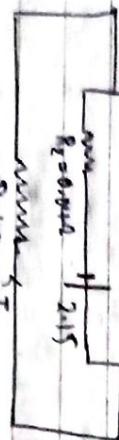Q.  $\frac{V}{R_1} = \frac{V}{0.04} = \frac{V}{2.05}$



Ay.

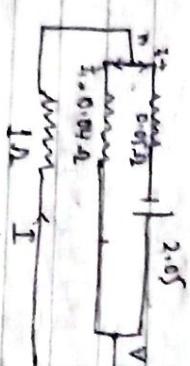

$$\frac{V}{R_1} = \frac{V}{0.04}$$

$$120V = 820 \\ V = \frac{820}{920} = \frac{4}{46} = 0.891 \\ I = 0.891A$$

$$920V = 820$$

$$V = \frac{820}{920} = \frac{4}{46} = 0.891$$

~~I = 0.891A~~

- Take any one of the independent voltage or current source. Replace the other energy sources by their internal resistances that is voltage sources become short circuited and current sources become open circuited.
- Repeat the above two step for each of the independent energy sources.
- At all the currents obtain in each branch for individual energy source.


$$\frac{V}{R_1} + \frac{V}{1} + \frac{V - 2.05}{0.04} = 0 \\ \frac{100}{5} + \frac{V}{1} + \frac{100 - 2.05}{4} = 0 \\ 20V + 20V + 25V = 0 \\ 65V = 0 \\ V = 0$$

$$920V = 1075 \\ V = \frac{1075}{920} = 1.16 \\ I_{total} = 1.16 = 2.051$$

$$V_{total} = 0.891 + 1.16 = 2.051$$



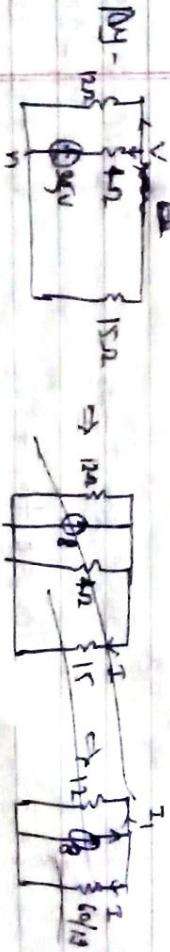
Q.  $\frac{V}{R_1} = \frac{V}{0.04} = \frac{V}{2.05}$



$$\frac{V}{R_1} = \frac{V}{0.04} + \frac{V}{1} + \frac{V}{2.05} = 0$$

$$120(V - 2.05) + \frac{V(100 - 2.05)}{4} + \frac{V(100 - 2.05 + 2.05)}{920} = 0 \\ 90V - 243 + 24.75 + 2.05 = 0 \\ 94.75 = 243 \\ V = 2.05$$

$$V = 2.05$$

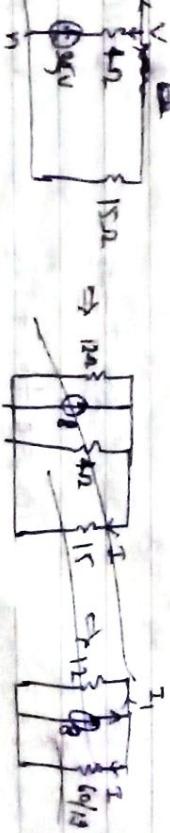


$$\frac{V}{R_1} = \frac{V}{0.04} + \frac{V}{1} + \frac{V}{2.05} = 0$$

$$120(V - 2.05) + \frac{V(100 - 2.05)}{4} + \frac{V(100 - 2.05 + 2.05)}{920} = 0 \\ 90V - 243 + 24.75 + 2.05 = 0 \\ 94.75 = 243 \\ V = 2.05$$

$$V = 2.05$$

$$I = 0.891A$$
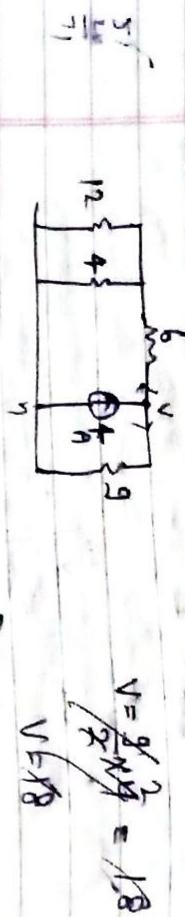
$$V = IR \Rightarrow \frac{20}{15} = I \Rightarrow I = \frac{4}{3} A$$




$$\frac{V}{9} + \frac{V}{9} = 4 \Rightarrow V = \frac{9}{2} \times 4 = 18$$

$$I = \frac{V}{R} = \frac{18}{9} = 2$$

$$I_{10} = \frac{V}{3} + 2 = 1.33 + 2 = 3.33$$

dependent

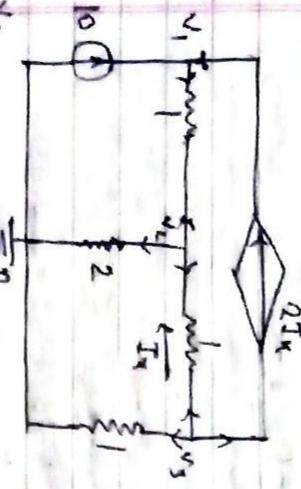

$$5V_3 - V_1 + V_2 + 2V_3 - V_3 = 0$$

$$5V_3 - 2V_1 + V_2 + V_3 = 0 \quad \text{eqn } -\textcircled{1}$$

$$5V_3 - 2V_1 + 10 = V_1 - V_2 \quad \text{eqn } -\textcircled{4}$$

$$I_A = V_2 - V_1$$

$$\begin{aligned} V_3 - V_2 + 2I_A + V_3 \\ 2V_3 + 2I_A = V_2 \\ 2V_3 + 2V_3 - 2V_1 = V_2 \\ 4V_3 = 3V_2 - \textcircled{3} \end{aligned}$$

eqn -\textcircled{2}

$$5V_2 = 2V_1 + \frac{3}{2}V_2$$

$$3V_2 + 10 = 2V_1 + 2V_2$$

$$V_2 = 2V_1 - 20$$

$$10V_2 = 4V_1 + 3V_2$$

$$V_1 = \frac{5V_2 - 3V_2}{4} = 14$$

$$\frac{14V_2}{4} = V_1$$

$$V_1 = 14$$

$$V_2 = \frac{7}{2}V_2 - 20$$


$$V_2 = 8$$

DATE : / /


PAGE NO. :

$$4V_3 = \frac{3 \times 8}{6} \quad I_A = V_3 - V_2 = 6 - 8 = -2 \quad \boxed{I_A = -2A}$$

Q.

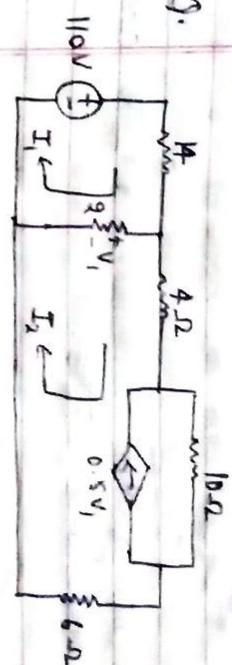

$$V = (I_1 - I_2) \times 2$$

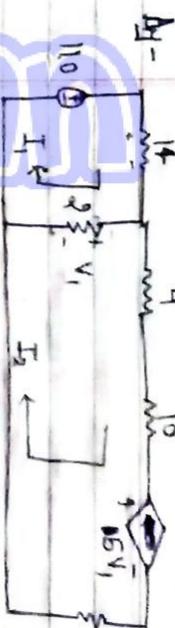

$$110 - 14I_1 - 2I_1 + 2I_2 = 0$$

$$110 - 16I_1 + 2I_2 = 0 \quad \text{--- } \textcircled{1}$$

$$-2I_2 - 14I_1 - 6I_1 + 2I_1 - 5(V_1 - V_2) = 0$$

$$-2I_1 - 22I_2 - 10I_1 + 10I_2 = 0$$

$$-8I_1 - \frac{1}{3}12I_2 = 0$$

$$-16I_2 = 24I_1$$

$$-3I_2 = 2I_1$$

eqn -\textcircled{1}

$$110 + 24I_2 + 2I_2 = 0$$

$$26I_2 = -110$$

$$I_2 = -\frac{55}{13} = -4.23$$

$$-3(-4.23) = 2I_1$$


$$I_1 = \frac{12.69}{2} = 6.34$$

$$V_1 = 10.57 \quad \boxed{V_1 = 21.149}$$

Thevenin Theorem:— Any linear resistive network with current & voltage sources can be replaced by an equivalent circuit containing of a single independent voltage source  $V_{TH}$  and series resistance  $R_{TH}$ .


Step for solving thevenin theorem →

- 1] Open the load resistor
- 2] Calculate the open circuit voltage or thevenin Voltage that is  $V_{TH}$ .
- 3] Replace the sources by their internal resistances i.e. current source become open circuited and voltage become a short circuited.
- 4] Calculate the thevenin resistance i.e.  $R_{TH}$ . Now re-draw the circuit with majored value of  $V_{TH}$  &  $R_{TH}$  and connect the load resistor. This is the equivalent thevenin circuit.
- 5] Find out the total current  $I_L$  flowing through the load resistor.

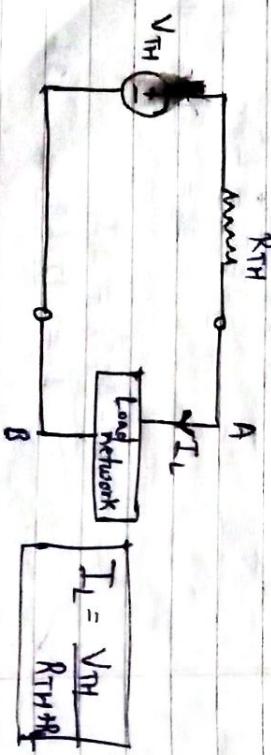


Step for solving Norton's theorem →


- 1] Short the load resistor.
- 2] Calculate the norton's current i.e.  $I_N$
- 3] Replace the source by their internal resistance i.e. current source becomes open circuited and voltage source become short circuited.
- 4] Calculate the norton's resistance i.e.  $R_N$ . Now re-draw the circuit with majored value of  $I_N$  &  $R_N$  and connect the load resistor. This is the equivalent norton's circuit
- 5] Find out the total load current flowing through the load resistor.

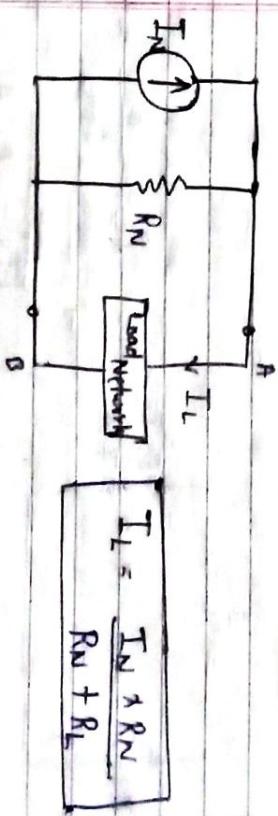

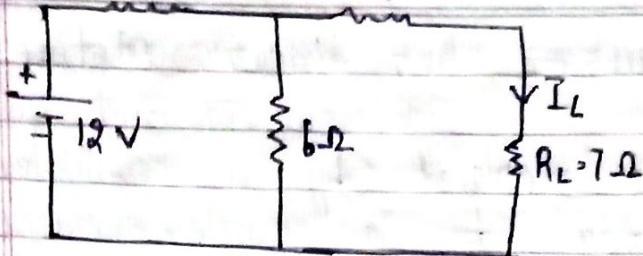Q. 3.  $\frac{3\Omega}{12V}$   $\frac{7\Omega}{R_L=7\Omega}$



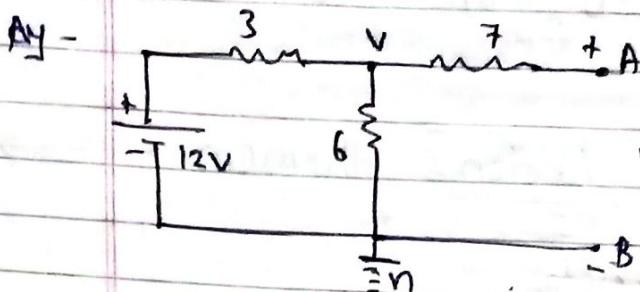Find  $I_L = ?$  using  
thevenin theorem




$$V_{TH} = ?$$

By nodal theorem:-

$$\frac{V-12}{3} + \frac{V}{6} = 0$$

$$\frac{2V-24+V}{6} = 3V = 24$$

$$V = 8 \text{ Volt}$$

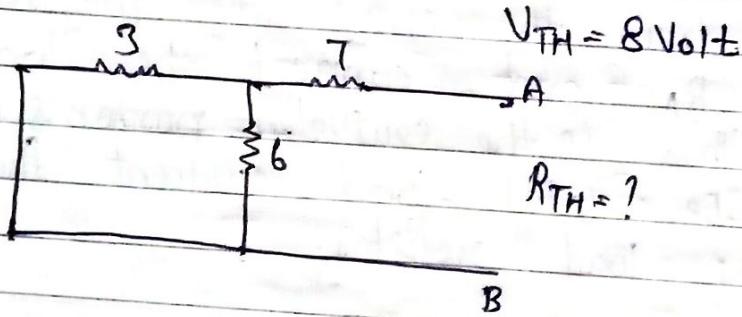


$$V_{TH} = 8 \text{ Volt}$$

$$R_{TH} = ?$$



$$R_{TH} = 2 + 7$$

$$R_{TH} = 9 \Omega$$

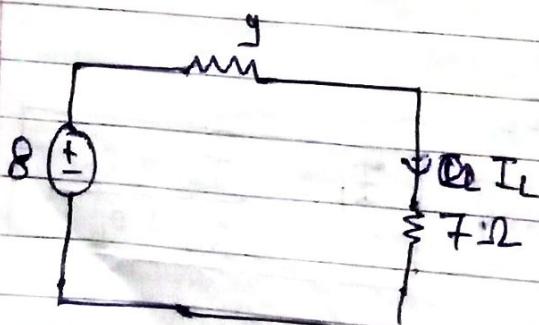


$$I_L = \frac{8}{9+7} = \frac{8}{16} = \frac{1}{2}$$

$$I_L = 0.5 \text{ A}$$


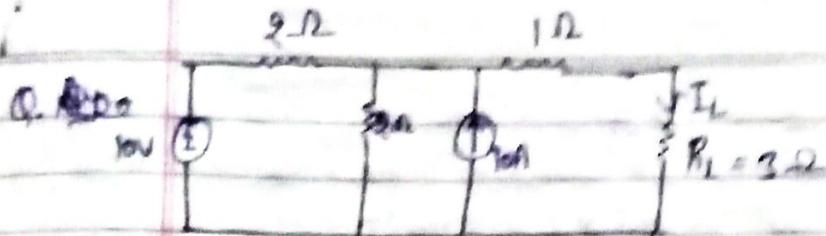
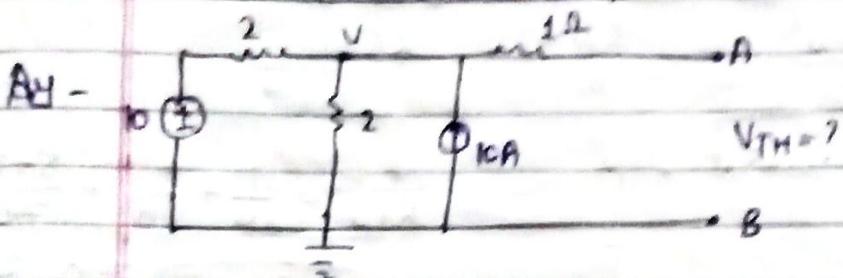
find  $I_L = ?$ 

$$\frac{V-10}{2} + \frac{V}{2} = 10$$
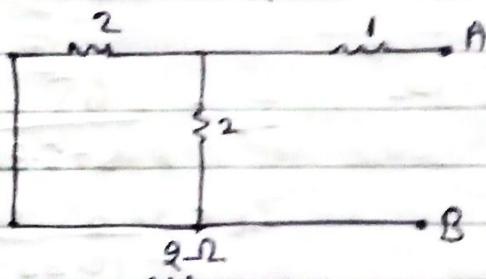
$$2V = 30 \Rightarrow V = 15\text{V} \text{ at } V_{TH} = 15\text{V}$$




$$R_{TH} = 2\Omega$$

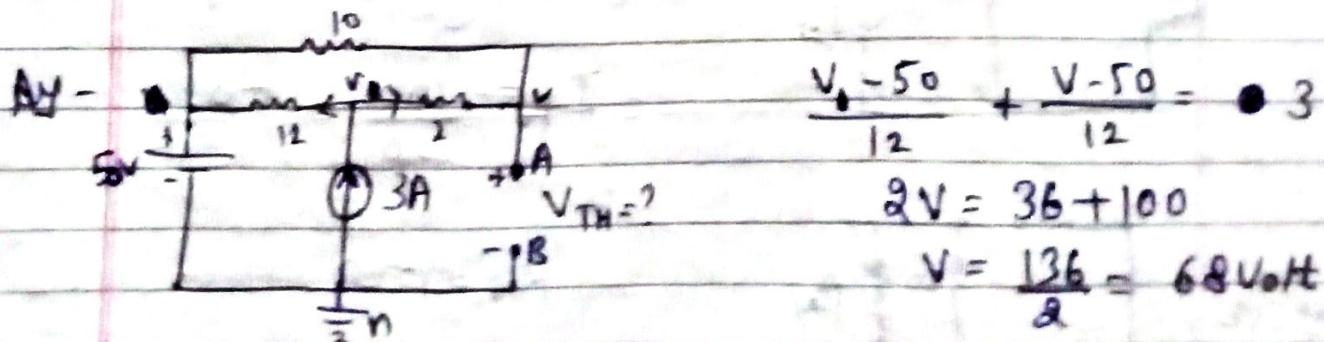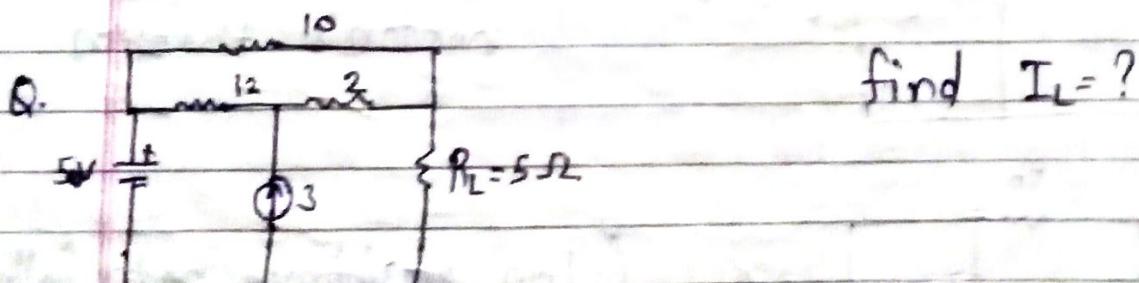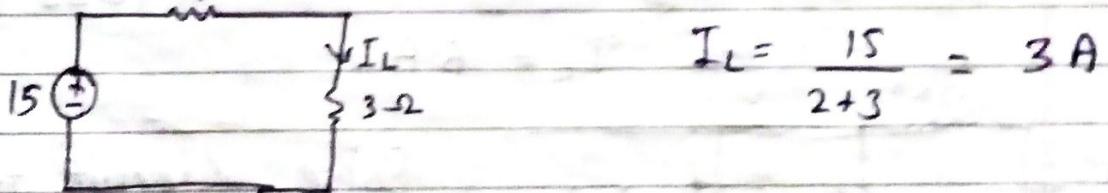

$$I = \frac{68 - 50}{12} = \frac{18}{12} = 1.5 \text{ A}$$

$$V' = 1.5 \times 2 = 3 \text{ Volt}$$


$$V_{TH} = V - V' = 68 - 3 = 65$$

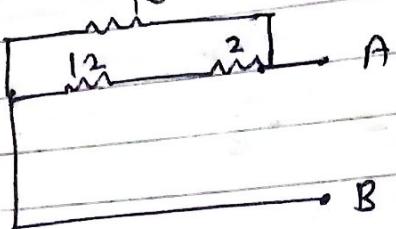

$$\frac{1}{R_{TH}} = \frac{1}{12} + \frac{1}{10} = \frac{5+7}{70}$$

$$R_{TH} = \frac{70}{12} = 5.83 \Omega$$


$$R_{TH} = 5.83 \Omega$$

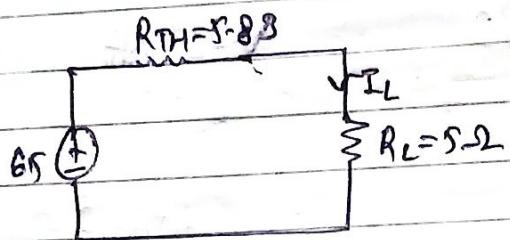

$$I_L = \frac{65}{5 + 5.83}$$


$$I_L = \frac{65}{10.83} = \frac{6500}{1083}$$

$$I_L = 6 \text{ A}$$

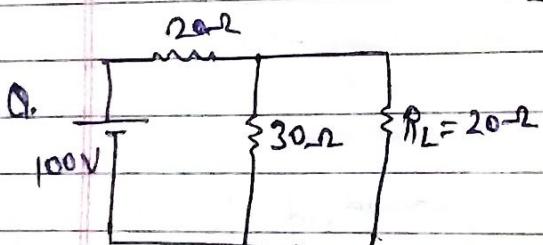


Solve circuit to  
norton's theorem

Ans

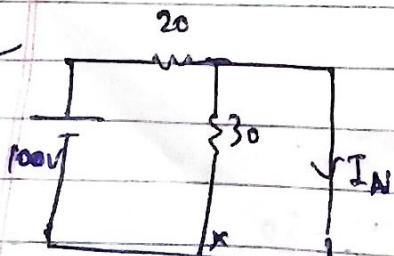

(Low resistance path follow)


$$I_N = \frac{100}{20} = 5 \text{ A}$$

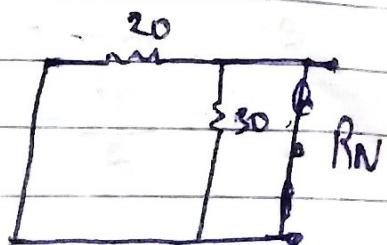

$$R_N = 12 \Omega$$


$$\frac{60}{5} = 12$$
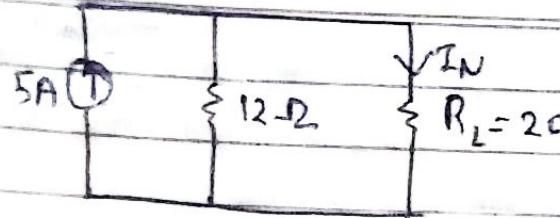
$$\frac{1}{2} + \frac{1}{3} = \frac{5}{6}$$




$$I_L = \frac{5 \times 12}{12 + 20} = \frac{60}{32} = \frac{15}{8} = 1.875$$

$$= \frac{15}{8} = 1.875$$

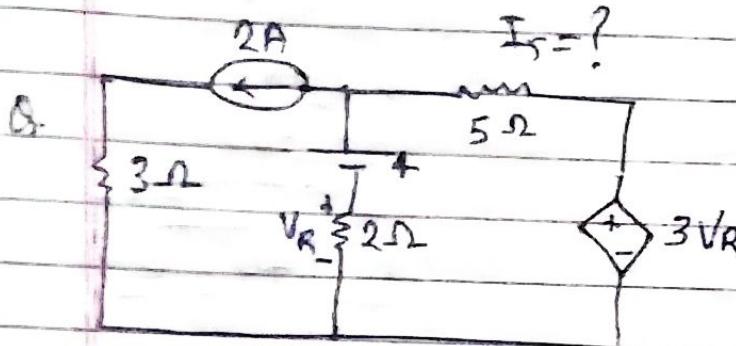

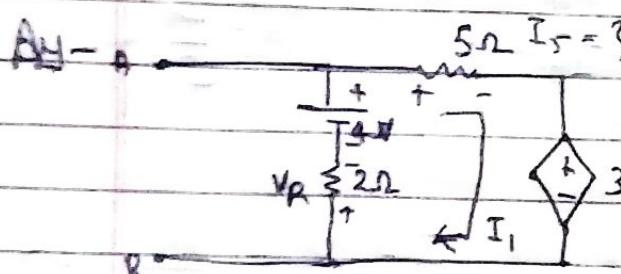find out at  
5 ohm Resistance  
Using superposition  
theorem




By Mesh :-

$$-5I_1 - 3VR - 2I_1 + 4 = 0$$

$$\begin{aligned} V_R &= 2I_1 \\ V &= -2I_1 \end{aligned}$$

$$-5I_1 + 6I_1 - 2I_1 + 4 = 0$$

$$I_1 = 4A$$

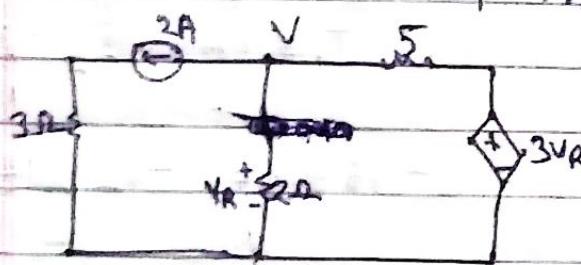

$$2 + \frac{V}{2} + \frac{V - 3VR}{5} = 0$$

$$2 + \frac{VR}{2} + \frac{VR - 3VR}{5} = 0$$

$$\frac{20 + 5VR - 4VR}{10} = 0$$

$$VR = -20 \text{ Volt}$$

$$I_2 = \frac{V - 3VR}{5} = \frac{-2VR}{5} = \frac{-2(-20)}{5} = 8A$$

$$I = 8 + 4 \Rightarrow 12A = I_{\text{total}}$$




find  $I_L$ ? using  
Thermin theorem?

$$R_{TH} = \frac{18+24}{5} = \frac{42}{5} = 8.4 \Omega$$



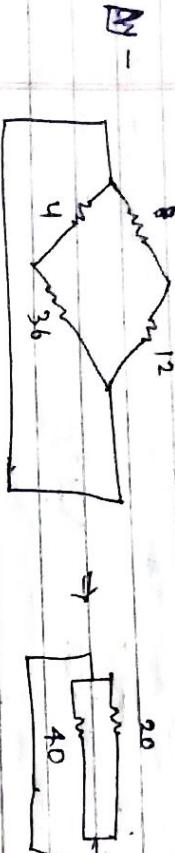
$$I_L = \frac{-12}{8.4 + 36} = -\frac{12}{44.4} = -\frac{30}{111}$$



$$\frac{1}{R_H} = \frac{1}{20} + \frac{1}{36} = \frac{2+1}{40} = \frac{3}{40} \Rightarrow R_H = \frac{40}{3} \Omega$$
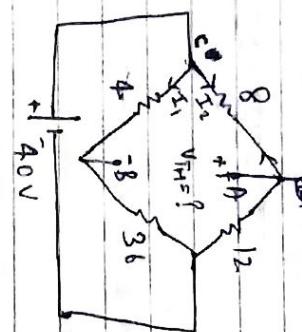
$$I = \frac{V}{R} = \frac{40}{40/3} = 3A$$



$$I_1 = 1A, I_2 = 2A$$

$$I_2 = 3 \times \frac{20}{60} = 1$$

$$V_{TH} = \sqrt{V_{AC}^2 + V_{BC}^2} = -16 + 4 = -12 \text{ Volt}$$

$$I_L = \frac{V_{TH}}{R_H + R_L} = \frac{-12}{\frac{40}{3} + 36} = \frac{-12 \times 3}{40 + 108}$$

$$I_L = -\frac{36}{148} = -\frac{18}{74} = -\frac{9}{37}$$




$$\frac{1}{R_H} = \frac{1}{20} + \frac{1}{36} = \frac{1}{12} + \frac{1}{36} = \frac{1}{12}$$

$$\frac{1}{R_H} = \frac{1}{12} + \frac{1}{36} = \frac{3+1}{36} = \frac{4}{36} = \frac{1}{9}$$

$$\frac{1}{R_H} = \frac{1}{12} + \frac{1}{36} = \frac{1}{12} + \frac{1}{36} = \frac{1}{12}$$

$$P_L = \frac{V^2}{R_L}$$

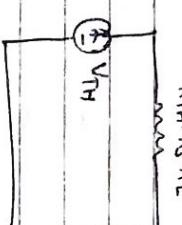

$$[R_S = R_L]$$

$$I_L = \frac{V}{R_S + R_L}$$

Power transfer.

$$P_L = I_L^2 R_L$$

$$P_L = \frac{V^2}{(R_S + R_L)^2} \times R_L$$

$$P_L = \frac{V^2}{R_S^2 + R_L^2 + 2R_S R_L} \times R_L$$

Maximum Power Transfer Theorem:-

DATE :  
PAGE NO.:

$$P_L = \frac{(R_S^2 + R_L^2 + 2R_S R_L)}{R_L} \times R_L \quad \text{for max. power}$$



$$P_{max.} = \frac{dP_L}{dR_L} = 0$$

$$\frac{-2R_S^2}{R_L^2} + 1 = 0$$

$$R_S = R_L$$

The max. power transfer theorem is used to determine the condition under which max. power can be transferred from a source network to load. According to this theorem max. power will be transferred from a source network to a load. If the

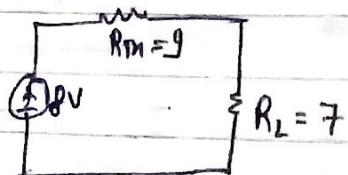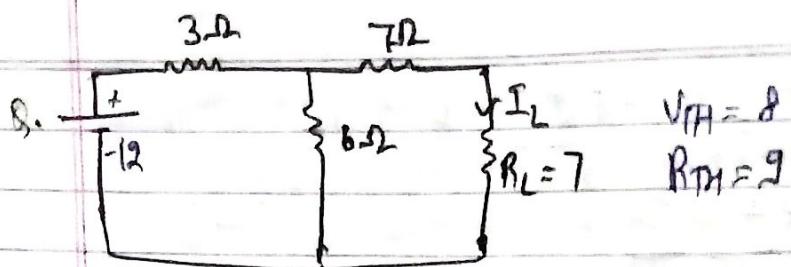load resistance  $R_L$  equal to the equivalent resistance  $R_S$  of the source network  
i.e.  $R_S = R_L$



$$I_L = \frac{V_{TH}}{(2R_S)}$$

$$P = I_L^2 R$$

$$P = \frac{V^2}{4R^2} \times R = \frac{8 \times 8}{4 \times 9} = \frac{64}{36}$$


$$P = \frac{16}{9} = 1.77$$

## Unit - 2

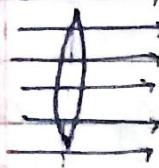
### AC Circuits

$$\theta = \omega t$$


Generation of AC Voltage or EMF  $\Rightarrow$



$$\theta = 0^\circ$$

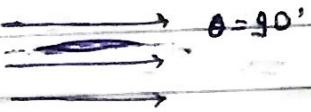

$$\theta = 90^\circ$$

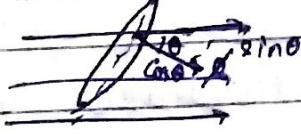

$$\theta = \omega t$$

$$e = -\frac{d(N\phi)}{dt} = N \frac{d(-\phi \cos \theta)}{dt} = N\phi \sin \theta \omega t$$

$$e = N\phi \omega \sin \omega t$$

$$e = E_{\max} \sin \omega t$$

According to the Faraday's Law of electro-magnetic induction when a moving conductor is placed in a magnetic field emf is generated.

It is important to note that max. of flux is linked with the conductor when the plane of the conductor is  $\perp$  to the flux lines. And it is zero when the plane of the coil is in parallel. At any other angle say  $\theta$  the flux linked with the conductor is equal to the component of  $\phi$  which is  $\perp$  to the coil.

1. Alternating Quantity

2. Waveform

3. Cycle

4. Time period

5. Frequency

6. Phase angle

7. Phase difference

8. Instantaneous Value

9. Average Value

10. Peak value

11. Alternating Quantity  $\Rightarrow$  It is the quantity which changes periodically in magnitude and indirection w.r.t. time.

2. Instantaneous Value  $\Rightarrow$  The value of alternating quantity at any particular instant & is called instantaneous value.

3. Average value  $\Rightarrow$  It is the average of all the instantaneous value

over one complete cycle.

4. Time period  $\Rightarrow$  Time taken by an alternating quantity to complete one cycle is called time period and it is denoted by 'T'.

5. Frequency  $\Rightarrow$  The number of cycles completed first, second by an alternating quantity is called 'Frequency' and denoted by 'f'.

6. Peak value  $\Rightarrow$  It is the maximum magnitude of an alternating quantity. Note:-

7. Wave form  $\Rightarrow$  The curve obtained by plotting instantaneous value wrt. time. is called 'wave form'

8. Cycle  $\Rightarrow$  One complete set of positive and negative values of an alternating wave is called cycle.

Average Value and RMS Value  $\Rightarrow$

Average value:- It is the average of all the instantaneous value of an alternating quantity over one complete cycle.

$$I_{av} = \frac{1}{2\pi} \int_0^{2\pi} i dt$$



RMS Value:- It is the square root of mean of square instantaneous value. The RMS value of an alternating quantity is given by that steady voltage or current which when flow through a resistor for a given period time

produced the same amount of heat. When the alternating current or voltage is applied to the same resistor for the same period of time.

$$I_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2(t) dt}$$

From vector ( $k_f$ )  $\Rightarrow I_f$  is the ratio of effective value on rms value to the average value.

$$\boxed{k_f = \frac{I_{\text{rms}}}{I_{\text{av}}}}$$


Note:- for sinusoidal wave  $k_f = 1.11$   
 for square wave  $k_f = 1$   
 for triangular wave  $k_f = 1.547$

Peak vector ( $k_p$ )  $\Rightarrow I_f$  is the ratio of max. value to the RMS value.

$$\boxed{k_p = \frac{I_{\text{max}}}{I_{\text{rms}}}}$$

Note:- For sin wave  $k_p = 1.414$   
 for square wave  $k_p = 1$   
 for triangular wave  $k_p = 1.732$

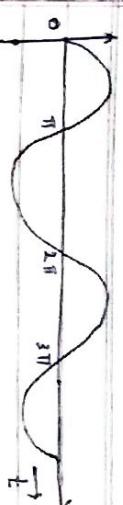Q. Find out average value, RMS value, peak value and peak value for sin wave.



$$I_{\text{av.}} = \frac{1}{\pi} \int_0^\pi i dt = \frac{1}{\pi} \int_0^\pi I_{\text{max}} \sin \omega t dt$$

$$= \frac{I_{\text{max}}}{\pi} [-\cos \omega t]_0^\pi = \frac{I_{\text{max}}}{\pi} [-\cos \pi + \cos 0]$$

$$\boxed{I_{\text{av.}} = \frac{2I_{\text{max}}}{\pi}}$$


$$I_{\text{rms}}^2 = \frac{1}{2\pi} \int_0^{2\pi} I_{\text{max}}^2 \sin^2 \omega t dt$$

$$I_{\text{rms}}^2 = \frac{I_{\text{max}}^2}{2\pi} \left[ t - \frac{\sin 2\omega t}{2} \right]_0^\pi = \frac{I_{\text{max}}^2}{2\pi} (\pi)$$

$$\boxed{I_{\text{rms}} = \frac{I_{\text{max}}}{\sqrt{2}}}$$

$$k_f = \frac{I_{\text{rms}}}{I_{\text{av}}} = \frac{I_{\text{max}}}{I_{\text{av}}} \times \frac{\sqrt{2}}{\pi} = \frac{\pi}{2\sqrt{2}} \times \frac{3.14}{2.89} = 1.11$$
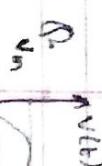
$$k_p = \frac{I_{\text{max}}}{I_{\text{rms}}} = \frac{I_{\text{max}}}{I_{\text{rms}}} \times \sqrt{2} = \sqrt{2} = 1.414$$



$$V_{\text{av.}} = \frac{1}{\pi} \int_0^\pi V(t) dt = \frac{1}{\pi} \left[ \int_0^{\pi/2} V_m \sin t dt + \int_{\pi/2}^{\pi} 0 dt \right]$$

$$V_{\text{av.}} = \frac{V_m}{2\pi} [-\cos \omega t]_0^\pi = \frac{V_m}{\pi}$$

$$V_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V^2 dt$$

$$V_{avg} = \frac{1}{2\pi} \left[ \int_0^\pi V_m^2 \sin^2 t dt + 0 \right]$$

$$V_{avg} = \frac{1}{2\pi} V_m^2 \int_0^\pi \left( 1 - \cos 2t \right) dt$$

$$V_{avg} = \frac{k_p^2}{4\pi} (\pi - 0) = \frac{V_m^2}{4}$$

$$\boxed{V_{avg} = \frac{V_m^2}{4}}$$

$$k_p = \frac{V_{avg}}{V_m} = \frac{V_m \times \frac{\pi}{2}}{V_m} = \frac{3.14}{2} = 1.57$$

$$k_p = \frac{V_{avg}}{V_m} = \frac{V_m}{V_m} \times 2 = 2$$

i(t)



$$I_{av} = \frac{1}{T} \int_0^T I_m \sin \omega t dt$$

$$I_{av} = \frac{1}{T} \int_0^T I_m \sin \omega t dt$$

$$I_{av} = \frac{1}{\pi} \int_0^\pi I_m \sin^2 t dt$$

$$I_{av} = \frac{I_m}{\pi}$$

$$k_p = \frac{I_{av}}{I_m} = \frac{V_m}{I_m} = \frac{T}{2\pi}$$

$$k_p = \frac{I_{av}}{I_m} = \frac{V_m}{I_m} = \frac{T}{2\pi}$$

Q.



$$i(t) = \begin{cases} 0 & 0 \leq t < \frac{T}{4} \\ 100 \sin t & \frac{T}{4} \leq t < \frac{T}{2} \\ 0 & \frac{T}{2} \leq t < T \end{cases}$$

$$I_{av} = \frac{1}{T} \left[ \int_0^{\frac{T}{4}} 0 + \int_{\frac{T}{4}}^{\frac{T}{2}} 100 \sin t dt + \int_{\frac{T}{2}}^T 0 \right]$$

$$I_{av} = \frac{1}{2\pi} \left[ -100 \left[ -1 - \frac{1}{2} \right] \right] = \frac{50}{\pi} \times \frac{1}{\sqrt{2}}$$

$$I_{av} = \frac{50}{3.14} \times \frac{2.41}{1.41} = \frac{12.05}{4.4274} = 2.747$$

$$I_{avg}^2 = \frac{100^2}{2\pi} \left[ \int_0^{\frac{T}{4}} \sin^2 t dt + 0 \right]$$


$$I_{avg}^2 = \frac{50000}{\pi} \left[ \int_{\frac{T}{4}}^{\frac{T}{2}} 1 - \cos 2t dt \right]$$

$$= \frac{5000}{\pi \times 2} \left[ t - \frac{\sin 2t}{2} \right]_{\frac{T}{4}}^{\frac{T}{2}}$$

$$= \frac{5000}{2 \times \pi} \left( \frac{3\pi}{4} - \left( 0 - \frac{1}{2} \right) \right)$$

$$I_{avg} = \frac{5000 \times 1}{8} + \frac{5000}{4\pi \pi} = 5000 \left( \frac{3}{8} + \frac{10}{1256} \right)$$
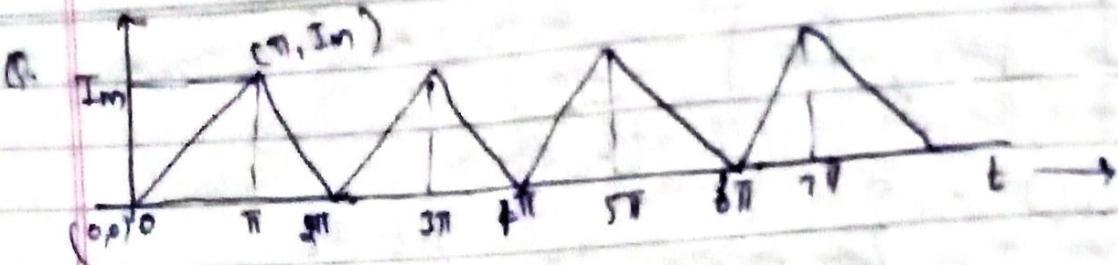
$$I_{avg} = \sqrt{5000^2 + \left( \frac{5000}{4\pi \pi} \right)^2} = \frac{2455000}{1256} = 2273.08$$



$$I_{av} = \frac{\frac{1}{2} \times \pi \times Im}{\pi} = \frac{Im}{2}$$

$$y = mx + c$$

$$i(t) = \frac{y_2 - y_1}{x_2 - x_1} \cdot x + c$$

$$i(t) = \frac{Im \times t}{\pi}$$

$$I_{av} = \frac{1}{2\pi} \int_0^{2\pi} \frac{Im}{\pi} \cdot t \cdot dt$$

$$I_{av} = \frac{1}{2\pi} \times \frac{Im}{\pi} \times \frac{\pi^2}{2} = \frac{Im}{2}$$

$$I_{av} = \frac{Im}{2}$$

$$I_{rms}^2 = \frac{1}{2\pi} \int_0^{2\pi} \frac{Im^2}{\pi^2} \times t^2 \cdot dt$$

$$I_{rms}^2 = \frac{Im^2}{\pi^2} \times \frac{4\pi^3}{3} =$$

$$\frac{Im^2}{\pi^2} \times \frac{4\pi^3}{3} = 0.25 Im^2$$

$$I_{rms} = \frac{2}{\sqrt{3}} Im$$

$$I_{rms} = \frac{2}{\sqrt{3}} Im$$


$$I_{rms}^2 = \frac{1}{\pi^2} Im^2$$

$$I_{rms}^2 = \frac{1}{\pi} \int_0^{\pi} \frac{Im^2}{\pi^2} t^2 \cdot dt$$

$$I_{rms}^2 = \frac{1}{\pi^3} \times Im^2 \left( \frac{\pi^3}{3} \right) = \frac{Im^2}{3}$$

$$I_{rms} = \frac{Im}{\sqrt{3}}$$

## Representation of Phasor:-

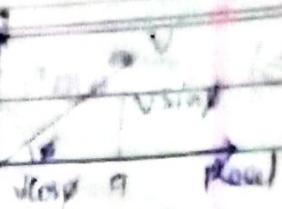

(i) Rectangular form:-

$$V = a + jb$$

Magnitude,  $V = \sqrt{a^2 + b^2}$

phase angle  $\phi = \tan^{-1} \left( \frac{b}{a} \right)$

(ii) Triangular form:-

$$a = V \cos \phi$$

$$b = V \sin \phi$$


$$V = \sqrt{[ \cos \phi + j \sin \phi ]}$$

magnitude

(iii) Polar form:-

$$V = V \angle \phi$$

↓  
magnitude

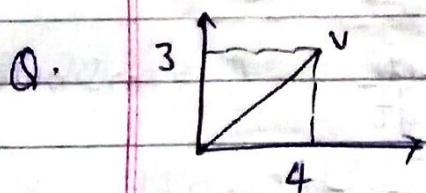

$$a = 4, b = 3$$

magnitude  $V = \sqrt{a^2 + b^2} = \sqrt{4^2 + 3^2} = 5$

Rectangular form

$$V = 4 + jb$$

$$\phi = \tan^{-1} \left( \frac{3}{4} \right) = 37^\circ$$

$$\cos \phi = \frac{4}{5}, \sin \phi = \frac{3}{5}$$

(ii) Triangular form

$$V = 5 \left[ \frac{4}{5} + j \frac{3}{5} \right] = 5 [\cos \phi + j \sin \phi]$$

$$V = 5 [\cos 37^\circ + j \sin 37^\circ]$$

Phase factor  $N = 5 \angle 31^\circ$        $V = 5 \angle 31^\circ$

$$V = 5 \tan^{-1} \left( \frac{3}{4} \right)$$

Analysis of AC circuit  $\Rightarrow$

(i) Purely Resistance circuit :-

$$V = V_m \sin \omega t$$

$$i = \frac{V}{R} = \frac{V_m \sin \omega t}{R}$$

$$\text{Graph: } i = I_m \sin \omega t$$



$$\text{Active power } P = VI \cos \phi$$

$$P = VI$$

(ii) Purely inductive circuit :-

$$e = -L \frac{di}{dt} \quad i = I_m \sin \omega t$$

$$\text{Graph: } e = -L I_m \frac{d(\sin \omega t)}{dt}$$

$$V = -L I_m \omega \cos \omega t = V_m \sin(\omega t + 90^\circ)$$

$$(iii) \quad V = V_m \sin(\omega t + 90^\circ)$$

$$\text{Time value } \downarrow \quad \text{Frequency } \downarrow \quad \text{Phase angle } \downarrow$$

Q.  $V = 75 \sin(200\pi t - 0.25)$  find (i) amplitude and

time value

(ii) Time & frequency (iii) Phase angle  $\phi$

$$\text{Ans: } (i) 75 \quad , \quad V_{\text{rms}} = \frac{75}{\sqrt{2}}$$

$$(ii) f = 100 \text{ Hz}$$

$$(iii) T = \frac{1}{f} = 0.01 \text{ sec} = T$$

$$\text{Graph: } V_m = L I_m \omega \sin \omega t = \omega L I_m$$

$$X_L = \omega L = 2\pi f L$$

$$\pi = 180^\circ$$

$$P = VI \cos \phi = VI (\cos 90^\circ)$$

$$\text{Graph: } i = \frac{C}{R} \frac{dV}{dt}$$

$$\text{Where } V = V_m \sin \omega t$$

$$i = C \frac{d(V_m \sin \omega t)}{dt}$$

$$j = C V_m \omega \cos \omega t = I_m \cos \omega t = I_m \sin(\omega t + 90^\circ)$$

$$\text{Graph: } j = I_m \sin(\omega t + 90^\circ)$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$X_C = \frac{V_m}{I_m}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

• R-L series circuit:— Apply KVL in the loop.

$$V = V_R + V_L$$

$$V = IR + jX_L I$$

$$V = I(R + jX_L)$$

$$V = IL$$

Applying KVL

$$V = V_R + V_L + V_C$$

$$V = IR + jIX_L - jIX_C$$

$$V = IL$$

$$Z = R + jX_L - jX_C$$


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

R-C series circuit:—

$$V = V_R + V_C$$

$$V = IR + jIX_C$$

Case - I When  $X_L > X_C$

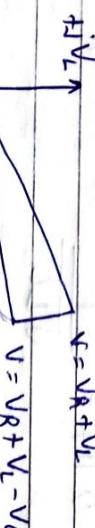


$$V = IZ$$


$$Z = R + j\frac{1}{\omega C}$$

$$\phi = \tan^{-1} \left( \frac{1}{\omega CR} \right)$$

$$\cos \phi = \frac{VR}{V}$$

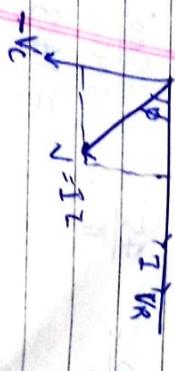


Case - II when  $X_C > X_L$

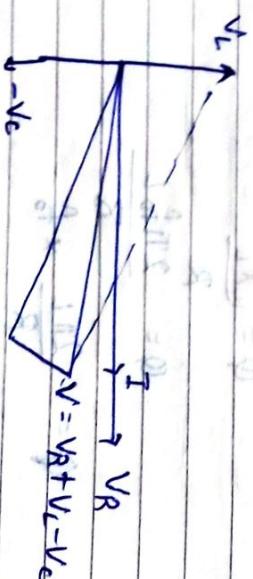

$$Z = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}$$

$$\phi = \tan^{-1} \left( \frac{1}{\omega CR} \right)$$

Series RLC circuit  $\Rightarrow$

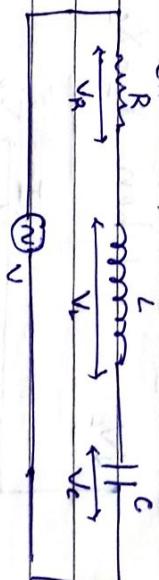

Applying KVL

$$V = V_R + V_L + V_C$$

$$V = IC(R + jX_L - jX_C)$$

$$V = IL$$

$$Z = R + jX_L - jX_C$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

DATE : / /  
PAGE NO. :

DATE : / /  
PAGE NO. :

Case - III When  $X_L = X_C$

$$Q = \frac{2\pi f L}{R} \times \frac{1}{2\pi f C}$$



$$\downarrow -jV_C$$

At resonance

$$X_L = X_C$$

$$WL = \frac{1}{WC}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi \sqrt{LC}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$Q$  factor

$$Q = \frac{X_L}{R}$$

$$Q = \frac{2\pi f_b L}{R}$$

$$Q = \frac{2\pi L}{R} \times f_b$$

FORMULA

$$V_R = IR, \quad V_L = jIX_L, \quad V_C = jIX_C, \quad I = \frac{V_L 0^\circ}{Z \mid Z \mid},$$

$$X_L = 2\pi f L, \quad X_C = \frac{1}{2\pi f C}, \quad V = \sqrt{I^2 R^2 + (V_L - V_C)^2}$$

$$A) \quad Z = \sqrt{(X_L X_C)^2 + R^2}$$

$$Z = \sqrt{(0.2 - 0.00015)^2}$$

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right), \quad \phi = \tan^{-1} \frac{X_L}{R}$$

$$X_C = \frac{1}{1000000 \cdot 2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 150} = \frac{1}{314 \times 150} = 0.000006366$$

$$\phi = \tan^{-1} \frac{X_C}{R}, \quad P = \sqrt{I \cos \phi}, \quad Q = \sqrt{I \sin \phi}$$

$$X_C = \frac{1}{1000000 \cdot 471} = \frac{1}{471} = 21.23$$

$$Z = R + j(X_L - X_C)$$

$$Z = \frac{20 + j(62.8 - 21.2)}{\sqrt{400 + 1730.56}} = \frac{20 + j16.6}{\sqrt{2130.56}} = 21.23$$

$$Z = 21.23$$

$$\phi = \tan^{-1} (62.8 - 21.2) = \frac{61.6}{20} = 3.08^\circ$$

$$\phi = 64.32^\circ$$

$$\text{Ques. } I = \frac{V_L 0^\circ}{Z \mid Z \mid} = \frac{400}{471} = 0.85 \text{ A}$$

$$I = \frac{400 \cdot 0^\circ}{46.15 \cdot 164.3^\circ} = \frac{8.66 \cdot 164.3^\circ}{8.66 \cdot 164.3^\circ} = 1$$

$$V_R = IR = 173.2 \angle -64.3^\circ$$

$$V_L = jIX_L = (8.66 \angle -64.3^\circ)(62.8 \angle -64.3^\circ) = 544 \angle 285.6^\circ$$

$$V_C = IX_C = -j(8.66 \angle -64.3^\circ)(21.23) = 183.8 \angle 154.3^\circ$$

$$20 \text{ mm} \quad 15 \text{ mm} \quad 0.2 \text{ H}$$

Find  $Z = ?$ ,  $I = ?$ ,  $V_R, V_L, V_C$ ,  $\cos \phi$ ,  $P + Q$

DATE: / /  
PAGE NO.:

$$\cos \phi = \cos(-64.3^\circ) = 0.43$$

$$P = V I \cos \phi$$

$$V \text{ Icos} \phi$$

$$400 \times 8.66 \cancel{\times 643} \times 0.43$$

$$\rho = 1489.5 \cancel{\times 643} \text{ Wt Wt}$$

$$Q = \sqrt{I} \sin \phi$$

$$Q = 400 \times 8.66 \times (-0.9)$$

$$Q = -3117 \cdot 6 \frac{\text{V}}{\text{Amm}}$$

Toto power unit

20

$$X_L = 1\omega = 3.18 \times 10^{-3} \times 314 = 9.98 \text{ S} \approx 10 \text{ S}$$

$$X_C = \frac{1}{C\omega} = \frac{1}{6.415 \times 10^{-6} \times 314} = 50 \Omega$$

$$Z = \sqrt{(10)^2 + (10 - 50)^2} = 10\sqrt{17} = 41.23\Omega$$


$$\phi = \tan^{-1}\left(\frac{-40}{10}\right) = -75.96^\circ = -76^\circ$$

1 = ✓20 ✓200  
2 Lb

$$\overline{I} = 4.85 \angle 76^\circ \text{ Amsf}$$

$$\cos \phi = \cos(76^\circ) = 0.24$$

9

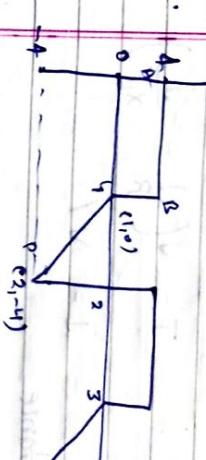

$$\text{Var}_y = \frac{1}{2} \left\{ \int_0^2 (4+4t)dt + \int_0^2 (-4t+4)dt \right\} = \frac{1}{2} \left\{ [4t]_0^2 + \left[ -\frac{4}{3}t^2 + 4t \right]_0^2 \right\}$$

$$\text{Voms} = \frac{1}{2} \left[ 16 \int_0^1 dt + 16 \int_1^2 (t^2 + 1 - 2t) \cdot dt \right]$$

$$V_{max} = 8 \left[ [t]_0 + \left[ \frac{t^3}{3} + t - t^2 \right]_0 \right]$$

$$V_{\text{rms}} = \sqrt{g} \left[ 1 + \frac{g}{3} - 2 \left( \frac{1}{3} \right) \right]$$

$$\text{Volume} = \frac{32}{3} \text{ Volume}$$

$$\text{Jms} = \sqrt{10.6}$$

$$V_{\text{rms}} = 3.2 \text{ Volt}$$

DATE : / /  
PAGE NO. : 8-8

Parallel  $RL$  circuit: →

Apply KCL

$$\begin{aligned} I &= \frac{V}{R} + \frac{V}{jX_L} \\ I &= \frac{V}{R} + j\frac{V}{X_L} \\ I &= \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{V}{X_L}\right)^2} \end{aligned}$$

$$I = \sqrt{Y}$$


where  $Y$  is admittance

$$Y = \frac{1}{Z} = \frac{1}{R} - \frac{j}{X_L}$$

$$Y = G + jB \quad \rightarrow \text{Susceptance}$$

Conductance
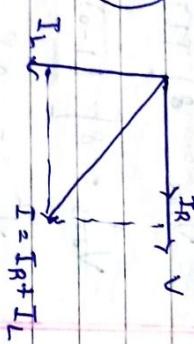
$$\begin{aligned} G &= \frac{1}{R} \\ B &= \frac{-1}{\omega L} \quad \phi = \tan^{-1}\left(\frac{B}{G}\right) \end{aligned}$$



Parallel  $RC$  circuit: →

Ans.

$$\begin{aligned} I &= I_R - I_C \\ I &= \frac{V}{R} - \frac{jV}{jX_C} \\ I &= \frac{V}{R} + \frac{jV}{X_C} \end{aligned}$$

$$I = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{V}{X_C}\right)^2}$$

Parallel  $RLC$  circuit: →

Apply KCL

$$\begin{aligned} I &= \frac{V}{R} - \frac{V}{jX_C} + \frac{V}{jX_L} \\ I &= \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{V}{X_C}\right)^2 - \left(\frac{V}{X_L}\right)^2} \end{aligned}$$

$$\begin{aligned} I &= \sqrt{Y} \\ Y &= \frac{1}{Z} = \frac{1}{R} + j\omega C - \frac{j}{\omega L} \\ Y &= G + j(B - \gamma_L) \end{aligned}$$

$$\begin{aligned} \phi &= \tan^{-1}\left(\frac{Y_L - Y_C}{G}\right) \\ \text{Ans.} & \quad \begin{array}{c} \text{Given} \\ \text{values} \\ \text{from} \\ \text{Q.} \end{array} \end{aligned}$$

$$\begin{array}{c} \text{Ans.} \\ \text{values} \\ \text{from} \\ \text{Q.} \end{array}$$

Calculate ①  $V_1, R_1 V_2$  (ii)  $I_1, R_1 I_2$

$$V_1 = \Sigma Z_1 \quad I = \frac{V_L 10^\circ}{Z_{L\phi}}, \quad Z_{23} = \frac{Z_2 \times Z_3}{Z_2 + Z_3}$$

A)

$$Z_1 = 2 + j3 = 3.6 \angle 56.3^\circ$$

$$Z_2 = 3 + j4 = 5 \angle 53.1^\circ$$

$$Z_3 = 6 - j8 = 10 \angle -53.1^\circ$$

$$Z_{23} = \frac{5 \angle 53.1^\circ \times 10 \angle -53.1^\circ}{5 \angle 53.1^\circ + 10 \angle -53.1^\circ} = 3 + j4 + 6 - j8$$

$$Z_{23} = \frac{50 \angle 0^\circ}{9 - j4} = 50 \angle 10^\circ = 5.1 \angle 23.9^\circ$$


$$Z_{23} = 5.1 \angle 23.9^\circ = 5.1 [0.9 + j0.4] = 4.59 + j2.05$$

$$Z = Z_1 + Z_{23} = 2 + j3 + 4.59 + j2.05$$

$$Z = 6.59 + j5.05 = 8.30 \angle 37.3^\circ$$

$$I = \frac{V_L 10^\circ}{Z_{L\phi}} = \frac{100 \angle 0^\circ}{8.30 \angle 37.3^\circ}$$

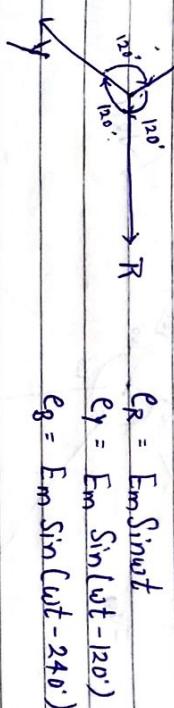Phase sequence :— It is the order in which attain their maximum +ve value.



### Generation of 3 phase EMF :-

Star connection :— In star connection the ends of 3 windings are connected to a common point called "neutral point". And the 3 line conductors are run from the remaining three terminals called line conductor. The current flowing in through each phase is called phase current  $I_P$ , and the current flowing through each conductor is called line current  $I_L$ .

$$V_1 = I Z_1 = 12 \angle -37.3^\circ \times 3.6 \angle 56.3^\circ$$


$$V_1 = 43.2 \angle 19^\circ$$

$$V_2 = I Z_2 = 12 \angle -37.3^\circ \times 5.1 \angle 23.9^\circ$$


$$V_2 = 61.2 \angle -13.4^\circ$$

$$I_1 = \frac{V_2}{Z_1} = 61.2 \angle -13.4^\circ \times \frac{1}{5 \angle 53.1^\circ} = 12.2 \angle -46.5^\circ$$
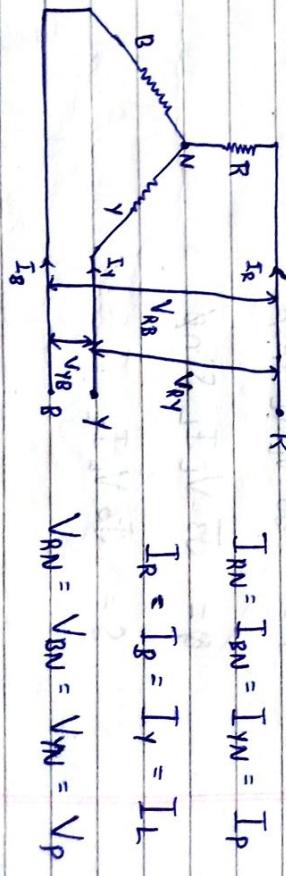
$$I_2 = \frac{V_2}{Z_3} = \frac{61.2}{10} \angle -13.4^\circ = 6.12 \angle 89.7^\circ$$



$$V_{AY} = V_{BY} = V_{RN} = V_P$$

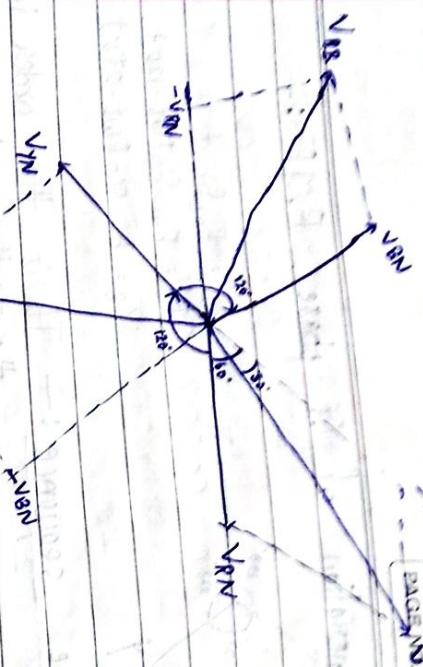

- A 3 phase star connected generator has a terminal voltage of 415 volt & delivers a full load current of 200 Amp at 0.8 power factor lagging. find  
 (i) Voltage per phase (ii) full load current per phase  
 (iii) KVA rating (iv) Real power delivered  
 (v) Load impedance (apparent)  $\angle 36.8^\circ$

$$\text{Ans} \quad \text{(i)} \quad V_p = 415 \quad \text{(ii)} \quad I_L = I_p = 200 \text{ Amp}$$

$$V_p = \frac{415}{\sqrt{3}} = 239.6$$

$$\text{(iii)} \quad S = \sqrt{3} V_L I_L = \sqrt{3} \times 415 \times 200 = 14380 \text{ VA}$$

$$\text{(iv)} \quad P = .\sqrt{3} \times 415 \times 200 \times 0.8 = 115.88 \text{ kW}$$

$$\text{(v)} \quad V_L^2 = V_p^2 + V_{ph}^2 + 2V_{ph}I_p \angle 36.8^\circ$$

$$V_L^2 = V_p^2 + V_{ph}^2 + 2V_{ph}I_p \angle 36.8^\circ$$

$$V_L^2 = V_p^2 + V_{ph}^2 + 2V_{ph}I_p \angle 36.8^\circ$$

$$V_L^2 = \frac{3V_p^2}{2} \quad \boxed{I_L = I_p}$$

$$Z = 1.19 \angle 36.8^\circ$$

$$Z = \frac{V_L^2}{P} = \frac{239.6^2}{115.88} = 52 \Omega$$

$$Z = \frac{V_L^2}{P} = \frac{239.6^2}{115.88} = 52 \Omega$$

$$Z = \frac{V_L^2}{P} = \frac{239.6^2}{115.88} = 52 \Omega$$

$$P = 3 V_p I_p \cos \phi$$

$$P = \sqrt{3} \times \sqrt{3} V_p I_p \cos \phi$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$Q = \sqrt{3} V_L I_L \sin \phi$$

$$S = \sqrt{3} V_L I_L$$

$$A - I_p = \frac{400}{\sqrt{3} \times 10} = 23.09 \angle 36.8^\circ \quad V_p = 230.9 \text{ Volt}$$

$$\sqrt{L} = 400$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$P = \sqrt{3} \times 400 \times 23.09 \times \frac{4}{5}$$

$$P = 368^\circ$$

power factor

$$T_p = 23.09 \angle -36.8^\circ$$

$$\cos\phi = 0.8$$

$$V_p = 230.9$$

$$P = \sqrt{3} \times 400 \times 23.09 \times 0.8$$

$$P = 12.797.77 \text{ Watt}$$

$$\text{real power } P = 12.79 \text{ kWatt}$$

$$Q = -9.59 \text{ kVar}$$

$$Q = -\sqrt{3} \times 400 \times 23.09 \times \frac{3}{5}$$

$$\theta = -9.59^\circ$$

$$\theta = -9.59^\circ$$

$$Z = \frac{V_p}{I_{pp}} = \frac{230.9}{23.09 \angle 36.8^\circ}$$

$$S = \sqrt{3} \times 400 \times 23.09 = 16.08 \text{ kVA}$$

$$I_L^2 = I_p^2 + I_p^2 + \frac{2 \times 1}{2} \times I_p^2$$

$$I_R^2 = 3 I_p^2$$

$$N_L = V_p$$

$$I_L = \sqrt{3} I_p$$

Power :-


$$P = 3 \sqrt{3} \rho I_p \cos\theta = \sqrt{3} \times \sqrt{3} I_p \rho \cos\theta$$

$$P = \sqrt{3} V_L I_L \cos\theta$$

Delta connection :

$$Q = \sqrt{3} V_L I_L \sin\theta$$

$$S = \sqrt{3} V_L I_L$$

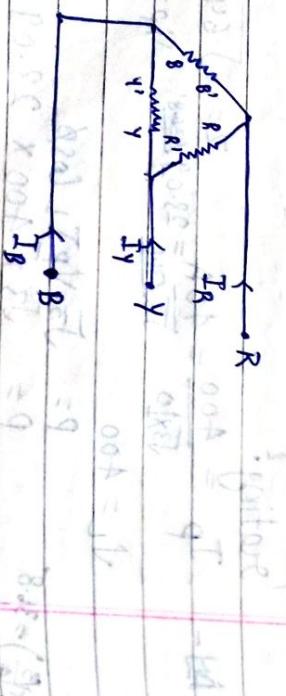

- Q. 3 coil of equal impedances of  $4 + j3 \Omega$  are connected in Delta across 400 volt, 50Hz supply. Find the phase current of each coil, line current, active, reactive &

apparent power?

$$\text{Ques} \quad V_L = 400 \text{ volt} = V_p, \quad f = 50 \text{ Hz}$$

$$Z = 4 + j3$$

$$Z = 5$$

$$\theta = \tan^{-1} \left( \frac{3}{4} \right) = 36.86^\circ$$

$$I_p = \frac{V_p / 0^\circ}{Z / 36.86^\circ} = \frac{400}{5 / 36.86^\circ} = 80 / -36.86^\circ$$

$$I_L = \sqrt{3} \times 80 / -36.86^\circ$$

$$I_L = 138.56 / -36.86^\circ$$

$$P = \sqrt{3} V_L I_L \cos \theta$$

$$P = \sqrt{3} \times 400 \times 138.56 \times 0.8$$

$$P = 76.81 \text{ kWatt}$$

$$Q = \sqrt{3} \times 400 \times 138.56 \times \sin(-36.86^\circ)$$

$$Q = -\sqrt{3} \times 400 \times 138.56 \times 0.59$$

$$Q = -57.80 \text{ kVAR}$$

$$S = \sqrt{3} \times 400 \times 138.56$$


$$S = 96 \text{ KVA}$$

$$I_{RR'} = 80 / -36.86^\circ$$

$$I_{PP'} = 80 / -156.86^\circ$$

$$I_{BB'} = 80 / -276.86^\circ$$

# Transformers

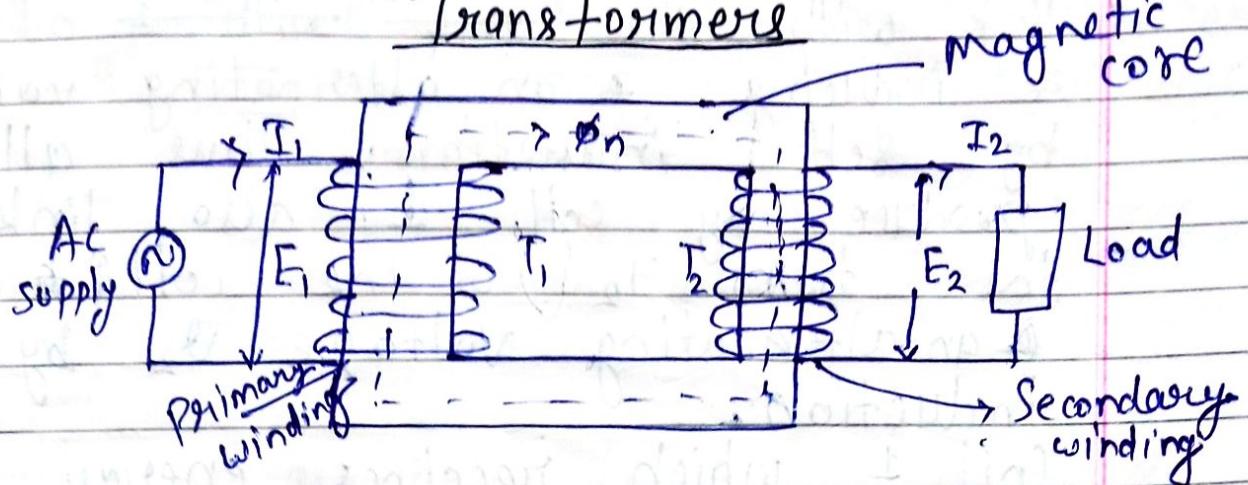


Transformer  $\Rightarrow$  A transformer is a static device which consists of two or more stationary electric circuit interlinked by a common magnetic circuit for the purpose of transferring electric energy b/w them. The transfer of energy from one circuit to another takes place without a change in the frequency.

## Construction & working of transformer $\Rightarrow$

Consider two coils 1 & 2 wound over on a simple magnetic circuit as shown in the figure about. These two coils are insulated from each other and there is no electrical connection b/w them. Let  $T_1$  &  $T_2$  be the no. of turn in coils 1 & 2. Now when a source of alternating voltage  $v$ , is applied to the coil 1 and alternating current  $I_1$  flows in it. This alternating current producing an alternating flux  $\phi_n$  in the magnetic circuit. This alternating flux

from with 1 of coil 1  
link with the ~~turn~~ turn with 2 of coil 2  
inducing induction. Thus all the flux  
is self produced by coil 1 also links with  
the turn  $T_2$  of the coil 2 and induces  
an alternating voltage  $v_2$  by mutual  
induction.

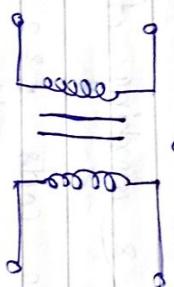coil 1 which receives energy from the  
source of AC supply is called the  
"primary" winding or simply the primary  
(coil 1) which is connected to the load  
and delivers energy to the load is  
called the "secondary" winding or simply  
the secondary. Thus electric energy  
is transferred from coil 1 to 2 by  
a common magnetic circuit.




Ideal transformer  $\Rightarrow$

An Ideal transformer is an imaginary  
transformer which has the following  
properties :-

1) Its primary winding & secondary winding  
resistances are negligible.  
2) The core has infinite permeability.

QUESTION)

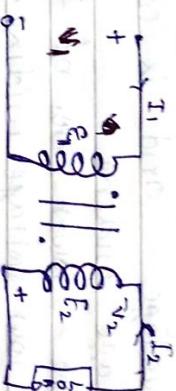3.1 The leakage flux and leakage inductance are zero.  
So the entire flux is confined to the core  
and links with both the ~~turns~~ windings.  
Their are no losses due to resistance,  
hysterisis and eddy currents. So  
the efficiency is 100%.



EMF Equation of transformer  $\Rightarrow$

Let at any instant, the flux  $\phi$  is .

$\phi = \Phi \sin \omega t$

The instantaneous emf is

$$e = -T \frac{d\phi}{dt}$$

$$e = -T \frac{d(\Phi \sin \omega t)}{dt} = -T \Phi m \omega \cos \omega t$$

$$e = T \Phi m \omega \sin(\omega t - \frac{\pi}{2})$$

$$e = E_m \sin(\omega t - \frac{\pi}{2})$$

$$\text{for Sin wave } E_{mfs} = \frac{E_m}{\sqrt{2}} = \frac{T \Phi m \omega}{\sqrt{2}}$$

1) Its primary winding & secondary winding  
resistances are negligible.  
2) The core has infinite permeability.

$$\boxed{E = 4.44 T \text{ mmf}}$$

PAGE NO.: / /  
DATE: / /

$$\boxed{E_1 = E_2}$$

$$\boxed{T_1 = T_2}$$

Voltage ratio & Turns ratio:-

$$E_1 = 4.44 \Phi_m f T_1$$

$$E_2 = 4.44 \Phi_m f T_2$$

$$\frac{E_1}{E_2} = \frac{\Phi_m}{\Phi_m} \frac{f T_1}{f T_2}$$


$$\boxed{\frac{E_1}{E_2} = \frac{T_1}{T_2} = q = \text{Transformation ratio}}$$

$$\text{mmf} = I_1 T_1 = I_2 T_2$$

$$\frac{I_1}{I_2} = \frac{T_2}{T_1}$$

$$\boxed{\frac{E_1}{E_2} = \frac{T_2}{T_1} = \frac{I_2}{I_1}}$$

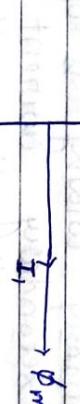No-load phasor diagram of Ideal transformer  
 $\Rightarrow$   
 $E_1, E_2$



Note:- The winding with higher no. of turns will have a high voltage and is called "the high voltage winding". The winding with the lower no. of turns is called the low voltage winding.

Stepup transformer:- A transformer in


which the output voltage is greater than its input voltage is called a "stepup transformer".

Stepdown transformer:- A transformer in which the output voltage is less than its input voltage is called a "stepdown transformer".


Note:- A transformer may receive energy at

some voltage and deliver it at the same voltage such a transformer is called one to one transformer.

For a one to one transformer

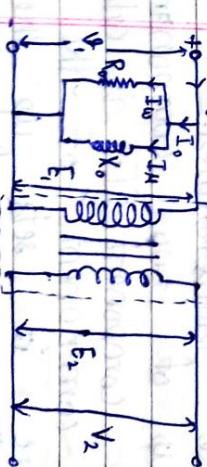

Transformer on No-Load  $\Rightarrow$

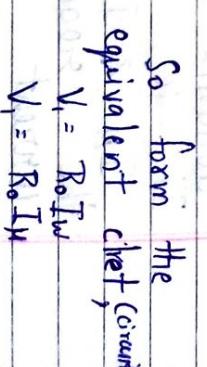

So form the equivalent circuit,

$$V_1 = R_1 I_{1n}$$

$$V_2 = R_2 I_{2n}$$

Ideal transformer

$$\boxed{I_{1n} = I_{2n}}$$

DATE: / /  
PAGE NO.: / /

where  $I_0$  is the no-load current.

三

$$I_w = I_0 \sin \phi$$

$$I_w = I_o \sin \phi$$

$E_1, E_2$

$$T_0 = \sqrt{T_w^2 + T_H^2}$$

$$\begin{aligned} P &= \sqrt{V_i I_o} \cos \phi && \text{(active power)} \\ Q &= \sqrt{V_i I_o} \sin \phi && \text{(reactive power)} \end{aligned}$$

$$\cos \phi_0 = \frac{I_w}{T}$$

A transformer is said to be on no-load when the secondary winding is open circuited. So the secondary current becomes

zero. When set on a alternating voltage, is applied to the primary a small current flows in the primary. This

current  $I_0$  is called the no-load current of the transformer.

In 4. I<sub>4</sub>. The component I<sub>4</sub> is called the reactive component of the no-

would because it sets up the flux in one. So the  $I_x$  is far in the face with  $\phi_m$ . The component  $I_w$  supply the hysteresis and eddy current losses.

in the core and known as active component off the no-load current. It is in fact ~~is with~~ the applied voltage  $V_1$ .

For a no-load transformer  $E_1$  &  $E_2$  are induced by the same flux by so they will be in face with each other and lags behind  $\phi$  by  $90^\circ$ . According to Lenz Law  $E_1$  is equal & opposite to  $V_s$ .  $I_H$  is in face with  $P_m$  and  $I_{Hw}$  is in face with  $V_s$ . The phasor sum of  $I_H$  &  $I_{Hw}$  is  $I_o$ .  $\cos \phi$  is the power factor on no load and  $\phi$  is the phase angle on no load.

Find the active & reactive component of no load current and no-load current of a  $440/220$  volt single phase transformer. is the input

The low voltage winding is given power factor of the current is 0.3 lagging

$$P_0 = \frac{V_1}{V_0} I_0 \cos \phi$$

$$\cos \phi_0 = 0.3 \quad , \quad V_1 = 4.80 \text{ V}$$

$$L_{40} = 80 \times T_0 \times 0.5$$

$$\frac{2 \times 10}{8 \times 3} = \frac{I_0}{24} = I_0 \Rightarrow I_0 = \frac{12}{24} = 0.083 A$$

$$I_{\text{B}} = I_{\text{O}} \cos \phi = P_0 / V_i I_o \cos \phi$$

$$I_0 = \frac{8 \times 10}{41x^2} = \frac{80}{132} = \frac{20}{33} = 0.60$$

$$I_{\omega} = I_0 \cos \phi = 0.60 \times 0.3 = 0.18 \text{ A}$$

$$I_{\omega} = 0.18 \text{ A}$$

$$\boxed{[(I_0)^2 - (I_{\omega})^2] = I_H}$$

$$0.36 - 0.032 = I_H$$

$$I_H = 0.2$$

$$\boxed{I_H = 0.578 \text{ A}}$$

Equivalent circuit of a transformer :-

Referred value  $\Rightarrow$

$$R_2 \rightarrow R_2'$$

$$T_2'^2 R_2' = T_2^2 R_2$$

$$R_2' = \frac{T_2^2}{T_2'^2} R_2 = \left(\frac{T_2}{T_2'}\right)^2 R_2$$

$$0.360 \\ 0.032 \\ \hline 0.298$$

$$\boxed{R_2' = 0^2 R_2}$$

$$R_2 \left( \frac{T_2}{T_2'} \right)^2 = R_1 \left( \frac{T_2}{T_2'} \right)^2 + R_2$$

from eqn - ①

$$\boxed{R_2 = R_2 + \frac{R_1}{q^2}} \quad \boxed{X_{e2} = X_2 + \frac{X_1}{q^2}}$$

$$X_{e2} = R_{e2} + j \frac{X_{e2}}{q^2}$$

$$Z_{e2} = \sqrt{R_{e2}^2 + X_{e2}^2}$$

Equivalent values referred to the secondary  $\Rightarrow$   
Let  $R_{e2}$ ,  $X_{e2}$  &  $Z_{e2}$  be the effective resistance  
reactance & impedance of the whole trans-  
former referred to the secondary.

$$\boxed{\begin{aligned} I_1^2 R_1 &= I_2^2 R_2 \\ R_1' &= \left[ \frac{R_1}{q^2} \right] R_1 = \frac{R_1}{q^2} \end{aligned}}$$

$$R_{e2} = R_2 + R_1$$

$$\boxed{R_{e2} = R_2 + \frac{R_1}{q^2}} \quad \boxed{X_{e2} = X_2 + \frac{X_1}{q^2}}$$

$$Z_{e2} = \sqrt{R_{e2}^2 + X_{e2}^2}$$

$$R_1 \left( \frac{T_2}{T_2'} \right)^2 = R_1 \left( \frac{T_2}{T_2'} \right)^2 + R_2$$

from eqn - ②

$$\boxed{\frac{R_1}{q^2} = R_{e2}}$$

$$\boxed{X_{e2} = \frac{X_1}{q^2}}$$

$$\boxed{Z_{e2} = \frac{Z_1}{q^2}}$$


ideal transformer

Let  $R_{e1}$ ,  $X_{e1}$  and  $Z_{e1}$  be the effective resistance  
reactance & Impedance of the whole  
transformer referred to the primary


$$R_{e1} = R_1 + R_2'$$

$$\boxed{R_{e1} = R_1 + 0^2 R_2} \quad \text{--- ①}$$

$$\boxed{X_{e1} = X_1 + 0^2 X_2}$$

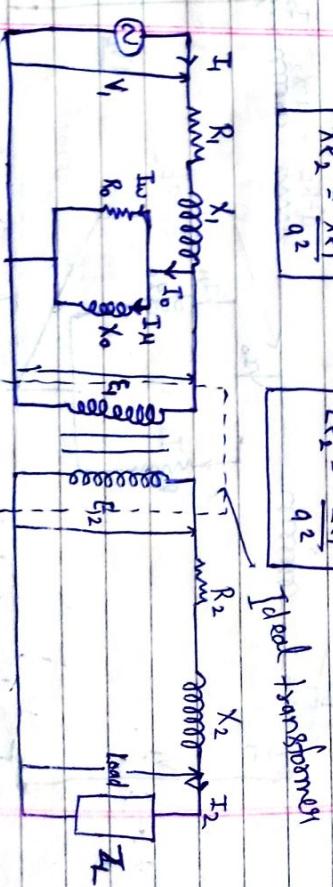

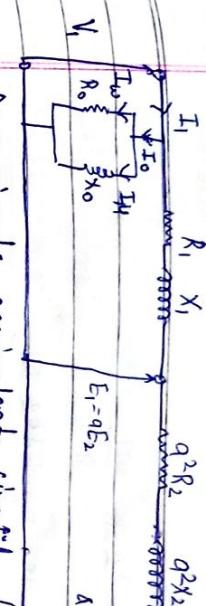The above figure shows the complete equivalent circuit of a transformer and exact equivalent circuit referred to the primary can be deduced as follows:—



Approximate equivalent circuit of a transformer referred to primary

This approximation gives the following advantages:-

The primary & secondary impedances reflected to the primary can be added easily. The calculations for voltage regulation of the transformer become easier.


The following result are obtain from the approximate equivalent circuit.

$$x_1 = x_1 + a_2 x_2$$

$$I_1 = \frac{V_1}{R_1 + jX_1}$$

$$I_1 = \frac{V_1}{Z_L + j\omega Z_L} \quad \text{where } Z_L \text{ is the load impedance.}$$

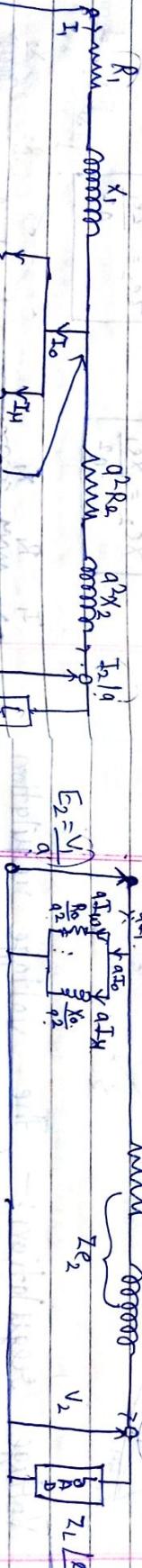Approximate equivalent circuit referred to the secondary  $\Rightarrow$



The following results are obtain from this

Exact equivalent circuit of a transformer is as follows:

$$X_{L2} = X_2 + \frac{X'_1}{a_2}$$

$$Z_{L2} = R_{L2} + jX_{L2}$$


$$I_2 = \frac{V_2}{Z_L}$$

$$I_2 = \frac{E_2}{Z_L + Z_L}$$

$$E_2 = \frac{V_1}{a}$$

$$E_2 = \frac{V_2}{a} = V_2 + I_2 Z_L$$

Phasor Diagram  $\Rightarrow$

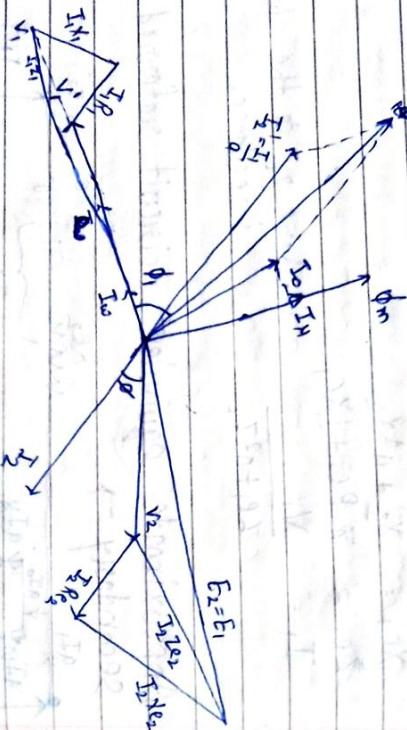

Value of primary voltage for both no load & 'rated load': It is expressed as either per unit or a percentage of the rated load voltage.

Per-unit voltage regulation at full load

$$= \left| \frac{|V_{2no}| - |V_{2f}|}{|V_{2f}|} \right| \times 100$$

Percentage voltage regulation at full load

$$= \left| \frac{|V_{2no}| - |V_{2f}|}{|V_{2f}|} \right| \times 100$$

$|V_{2f}| = \text{constant}$

Where  $V_{2no}$  is the no load secondary terminal voltage &  $V_{2f}$  is the rated secondary terminal voltage.

Voltage regulation in terms of primary

$$V_{2no} = \frac{V_1}{a}$$

$$= \left| \frac{|V_1| - |V_{2f}|}{|V_{2f}|} \right| \times 100$$

Transformer efficiency  $\Rightarrow$  The ratio of the output power to input power in a transformer is known as transformer efficiency.

$$\eta = \frac{\text{Output Power}}{\text{Input Power}}$$

Voltage regulation:- The voltage regulation of a transformer is defined as the percentage difference in the secondary (no load & full rated load) voltage at a given power factor with a given

$$\eta = \frac{\text{Output power}}{\text{Output power} + \text{Losses}}$$

$$\eta = \frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + I_2^2 R_2 + \text{iron loss}}$$

$$\eta = \frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + I_2^2 R_2 + P_i} \quad (\text{Rounding})$$

Losses in transformer  $\Rightarrow$  The losses which occur in a time

formation are

Iron loss or core loss ( $P_i$ )

Copper loss or  $I^2 R$  loss ( $P_e$ )

$f$  is the frequency of the alternating flux and the exponent ' $x$ ' is called 'Steinmetz constant'. Its value varies from 1.5 to 2.5 depending upon the magnetic properties of the core material. So the total core loss can be written as  $P_i = k_h f B_m^x + k_e f^2 B_m^2$

$$V_1 - E_1 = 4.44 A_m f I_1$$

$$B_m = \frac{V_1}{A_m}$$

$$P_h = k_h f B_m^x$$

$$P_h = k_h f \frac{V_1^x}{(4.44 A_m f I_1)^x}$$

$$P_h = \frac{k_h V_1^x}{4.44 A_m^x f^x} \frac{f^x}{f^x} \quad k_h = k_h \left(\frac{1}{4.44 A_m f I_1}\right)^x$$

This relation shows that the hysteresis loss depends upon both the applied voltage and frequency. Similarly  $P_e = k_e f^2 \frac{V_1^2}{(4.44 A_m f I_1)^2}$

$$\text{where } P_h = k_h f B_m^x$$

$$P_e = k_e f^2 B_m^2$$

$k_h$  = constant of proportionality which depends upon the volume and quality of the core material.

$k_e$  = constant of proportionality which depends upon the volume & resistivity of the core material.

$B_m$  = max. flux density in the core.

$$P_e = k_e \frac{V_1^2}{(4.44 A_m f I_1)^2} \frac{f^2}{f^2} \quad \left\{ k_e = \frac{k_e}{(4.44 A_m f I_1)^2} \right\}$$

$$[P_e = k_e V_1^2]$$

This relation shows that the eddy current loss depends on the square of the applied voltage and independent to frequency.

The total core loss is

$$P_i = K_h V^x f^{1-x} + K_e V^2$$

2.1 Copper loss  $\Rightarrow$  Copper loss is the  $I^2 R$  loss which takes place in the primary and secondary windings because of the winding resistances.

Total copper loss in a transformer


$$= \text{primary winding copper loss} + \text{secondary winding copper loss}$$

or

$$P_c = I_1^2 R_1 + I_2^2 R_2$$

$$P_c = I_1^2 R_{e1}, \quad P_c = I_2^2 R_{e2}$$

# ROTATING ELECTRICAL MACHINES

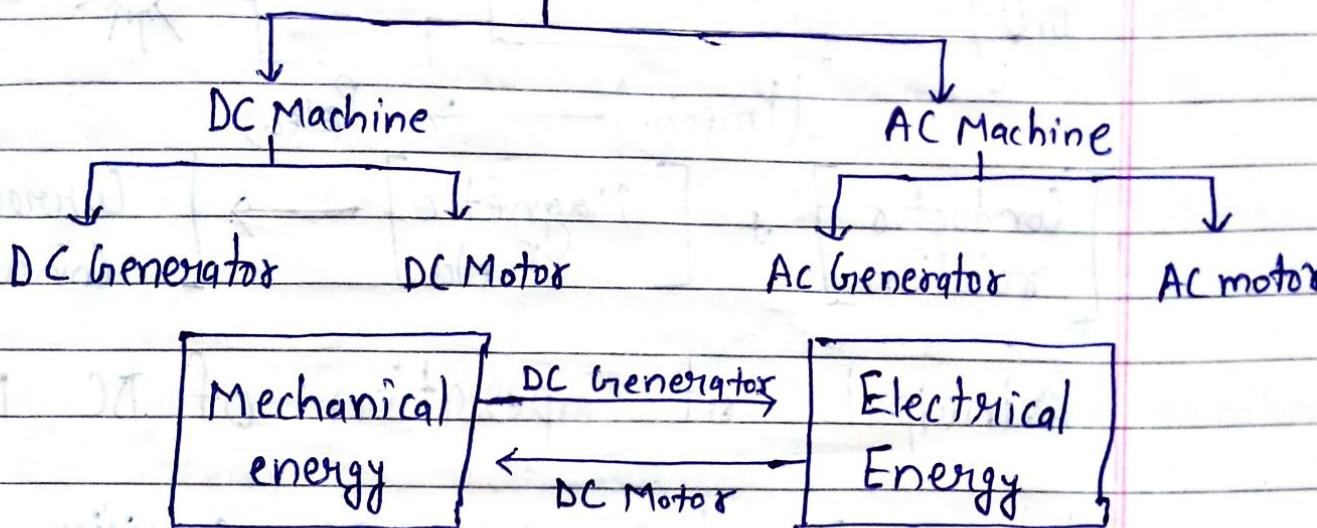

The rotating electrical machines are the electro mechanical energy conversion devices that converts mechanical energy into electrical energy and electrical energy into mechanical energy. There are two types of electrical machine -

1) DC Machine

2) AC Machine

The DC Machine is further divided into two parts the 1<sup>st</sup> one the 'DC Generator' & 2<sup>nd</sup> 'DC Motor'.


Principal of operation of a DC Generator  
→ If an externally applied force makes the conductor to move into the magnetic field. The current starts to flow in the conductor. Thus, converting mechanical energy into electrical energy. The figure shows the operating principle of the DC Generator.



$\left[ \text{Conductor} \right] + \left[ \text{Magnetic Field} \right] \rightarrow \left[ \text{Current in Conductor} \right]$

Principal of operation of DC Motor  $\Rightarrow$

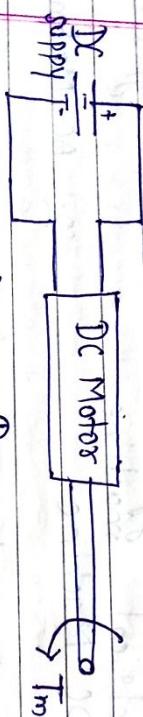When ever the current carrying conductor placed in the magnetic field it experiences a force that tends to oppose it. Therefore converting the electric energy into mechanical energy.



Pole  $\rightarrow$  P\_mech.

$\left[ \text{Current Carrying Conductor} \right] + \left[ \text{Magnetic Field} \right] \rightarrow \left[ \text{Rotation of Rotatable shaft} \right]$

$$\text{e} = \frac{P\phi N}{60} \text{ Volts}$$

If the number of armature conductor per parallel path is equal to  $\frac{Z}{A}$ . so the total emf in one conduction is equal to

$$E = \frac{P\phi N}{60} \text{ Volt}$$

**NOTE**  $\Rightarrow$  1) DC Motor follows the Fleming's left hand.

2) DC Generator follows the Fleming's Right hand Rule.

EMF Eq<sup>n</sup> of DC Machine  $\Rightarrow$  In general

the armature rotates an emf is generated across its conductor and

this emf is called generating emf. ( $E_g$ ).

Similarly Motor due to the armature rotation and emf is induced which is known as back emf. ( $E_b$ )


Let us consider  $\phi$  = Flux per pole (Wobens)

$$Z = \frac{\text{No. of poles}}{\text{Total no. of armature conductors}} \quad A = \frac{\text{No. of parallel paths through armature}}{\text{Speed of armature (rps)}}$$

$$\frac{P = A}{A = 2}$$

Lap winding  $\Rightarrow$   
Wave winding  $\Rightarrow$

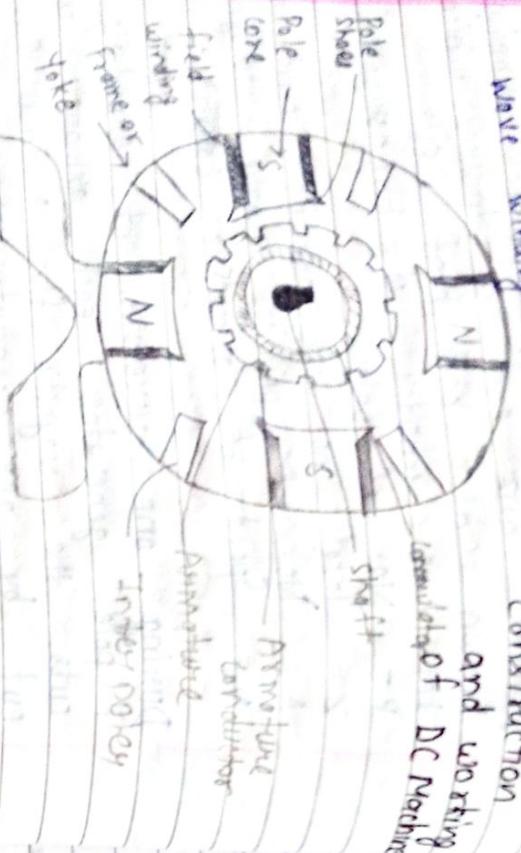Construction  
and working  
principle of DC Machine



(2.) Its pole forms a part of magnetic circuit.

(b) Pole core :— An even no. of pole cores are bolted to the yoke. Since the poles project inwards they are called salient poles.

(c) Pole shoes :— Each pole core has pole shoes having occurred surface and serves the following two purposes :—  
(i) It supports the field windings.  
(ii) It increases the cross sectional area of the magnetic circuit and reduces its reluctance.

(d) Field windings :— Each pole core have one or more field windings placed over it to produce the magnetic field in the machine.

(2) Armature  $\Rightarrow$  The rotating part of the DC Machine

(i) Magnetic field system  $\Rightarrow$  The magnetic field system is the stationary part of the machine. The magnetic field system consists of different parts :—  
(a) Frame or yoke :— The outer frame or yoke is a hollow cylinder made up of cast steel. The yoke serves the following two purposes  
(i) It supports the pole core and acts as a protecting cover for machine.



(ii) It provides the slot for the armature commutator & brush gear.

ii) Commutator and brush gear  $\Rightarrow$  Alternating voltage is produced in the windings rotating in a magnetic field. To obtain the direct current in the external circuit a commutator is needed. This commutator is required in the system to convert the AC into DC & DC into AC supply. It is made up of no. of insulated shape, copper bars insulator from each other and from the shaft.

**Brushes:-** Current is collected from the armature winding by means of two or more carbon brushes mounted on the commutator. Each brush is supported in a metal box called the brush box or brush holder.

**Equivalent circuit of a DC Machine:-** The armature of a DC Machine can be represented by an equivalent electric circuit: It can be represented by 3 series connected elements  $e$ ,  $r_a$  &  $V_b$ . The element ' $e$ ' is generated voltage.  $r_a$  is armature resistance &  $V_b$  is the brush contact voltage drop. The equivalent circuit of the armature of a generator or of a DC motor is shown by the figure below. In case of the DC motor  $e$  is the back emf.

DC generator

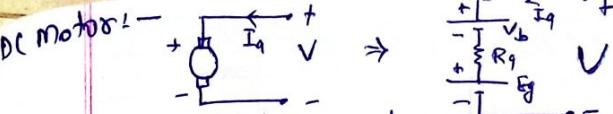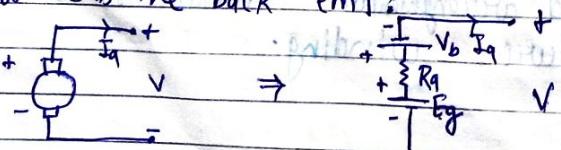

In case of generator, current flows from armature to line  
 $V = E_g - I_a R_a - V_b \Rightarrow V = E_g - I_a R_a$  [eqn "fundamental generator"]

In case of motor, current flows from line to armature  
 $V = E_g + I_a R_a + V_b \Rightarrow V = E_g + I_a R_a$  [eqn "fundamental motor"]

**Back emf:-** When the motor armature rotates its conductor cut the magnetic flux therefore the emf of rotation  $E_g$  is induced in them and in case of the motor this emf of rotation is known as "back emf" or "counter emf" because it opposes the apply voltage.

**Types of DC Machine  $\Rightarrow$**

**DC Machine**

Separately excited

Self excited

Shunt wound


Series wound

Compound wound

Short shunt


Long shunt

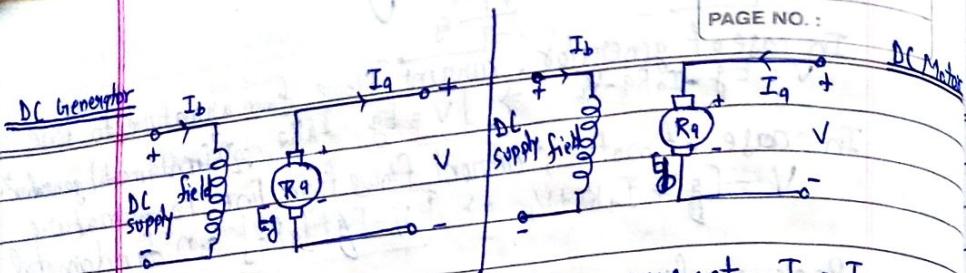i) Separately excited DC Machine  $\Rightarrow$  When the field windings are energized by a separate DC source the connection is called separately excited DC Machine.



Line current  $I_L = I_a$   
Generated EMF:—  
 $E_g = V + I_a R_a$   
Terminal voltage:—  
 $V = E_g - I_a R_a$


Shunt (parallel) wound DC Machine:—

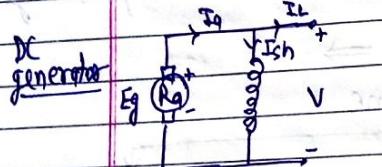

$$I_a = I_{sh} + I_L$$

$$-V + E_g - I_a R_a = 0$$

$$E_g = V + I_a R_a$$

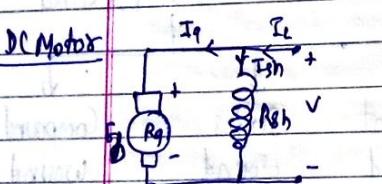

$$I_L = I_{sh} + I_a$$


$$E_f = V - I_a R_a$$

A machine in which the field coils are connected in parallel with armature called a shunt wound dc machine. Since the shunt field receives the full output voltage of a generator or the supply voltage of a motor it is generally made up of large no. of turns of a fine wire.

Line current  $I_L = I_a$   
generated emf:—  
 $E_f = V - I_a R_a$   
Terminal voltage:—  
 $V = E_f + I_a R_a$


Series wound DC Machine  $\Rightarrow$  A DC machine in which the field coils are connected in series with the armature is called series wound DC machine.

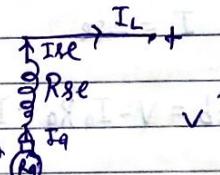The series to field winding consists of few turns of wire of large cross sectional area because it has to carry the large armature current.



$$I_a = I_{se} = I_L$$

$$V = E_g + I_a R_a + I_{se} R_{se}$$

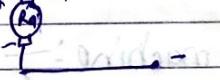



$$I_a = I_{se} = I_L$$

$$E_b = V - I_a R_a - I_{se} R_{se}$$



Compound wound DC machine  $\Rightarrow$  A DC machine having both shunt & series field is called a compound DC machine. The compound machine may be connected into two ways.

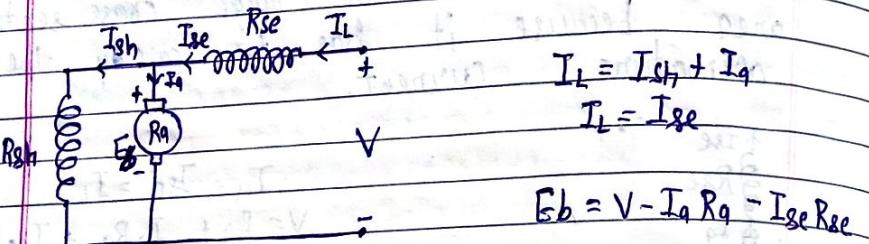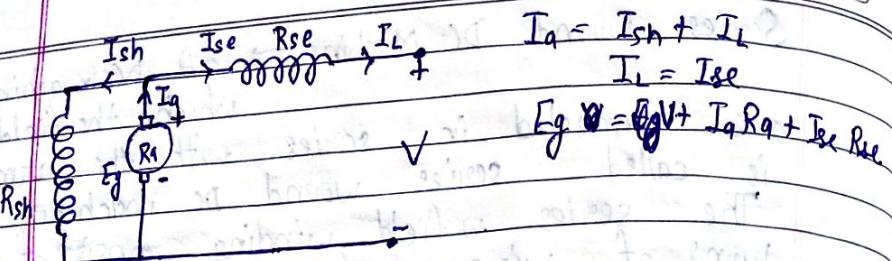1) Short shunt compound machine:—

If the shunt field is connected in parallel with armature along the machine is called short shunt compound machine.



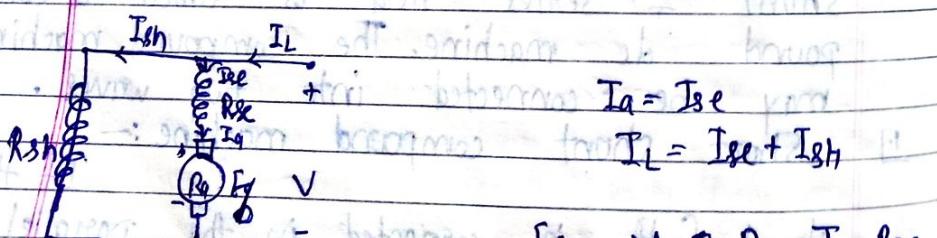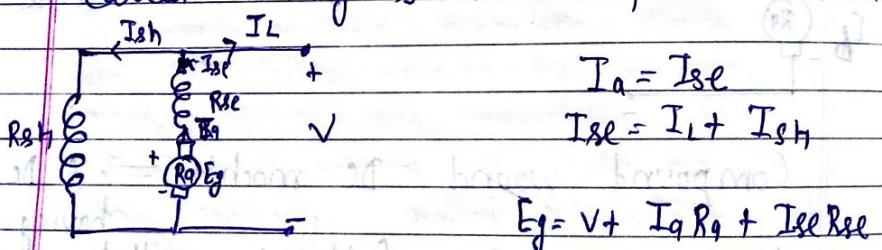3.1 Long shunt compound DC machine:— If the shunt field is connected in parallel with both armature & series field winding the dc is called long shunt compound DC machine.



Q. A 4 pole 900 rpm dc machine has a terminal voltage of 220 Volt & induced voltage of 240 Volt. At rated speed the armature resistance is 0.2 Ω. Is the machine operating as a generator or a motor? Compute the armature current & the no. of armature conductor if the flux per pole is 10 mWb & the armature wave wound.

Note— When induce voltage is greater than the terminal voltage the machine working as generator and vice versa.

Ans—  $V_T < V_I$  so generator

$$\begin{aligned} E_g &= V + I_a R_q \\ 240 &= 220 + I_a (0.2) \\ \frac{20}{0.2} &= I_a \Rightarrow I_a = 100 \text{ A} \end{aligned}$$

$$E = \frac{P \phi N}{60} \times \frac{Z}{A}$$

$$240 = \frac{4 \times 10 \times 10^6 \times 900}{60} \times \frac{Z}{2} \quad (c = \text{wave winding } A=2)$$

$$\frac{24 \times 8 \times 100 \times Z}{2} = Z \times 10^7$$

$$Z = 8 \times 10^7$$

Speed of a DC Machine → The emf equation of a DC machine is given by

$$E = \frac{NP\phi Z}{60 \times A}$$

$$\text{Now, solving } \frac{E}{N} = \frac{EZ}{\phi Z} \Rightarrow N = \frac{EZ}{\phi}$$

$$N = \frac{E}{k\phi}$$

$k$  = machine const.  
 $E$  = induce emf  
 $\phi$  = flux per pole

$$\text{where } k = \frac{PZ}{60\pi A}, \quad E = \text{induce emf} \\ \phi = \text{flux per pole} \\ & \text{Z} = \text{field flux}$$



In case of generator

$$N = \frac{V + I_a R_g}{k\phi}$$

motor:

$$N = \frac{V - I_a R_g}{k\phi}$$

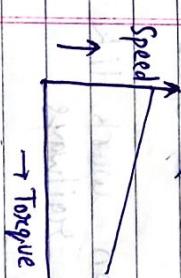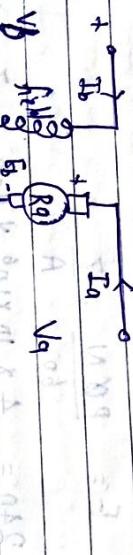Torque speed characteristic of a DC Motor  $\Rightarrow$



The torque speed characteristic is shown below:

Now if we plot the torque speed characteristic we found that as the torque developed is increased the speed will fall with the gradient of  $\frac{(k\phi)^2}{R_g}$ .

In separately excited DC motor the field windings are excited from a separate DC source. So the motor back emf or speed voltage is given by  $E_b = V_a - I_a R_g$  by applying KVL, we got  $E_b = V_a - I_a R_g$

And the armature induced voltage with motor rotating at a speed  $\omega$  is given by

$$E_b = k_e \omega$$

where  $\phi$  is the field flux &  $k_e$  is machine constant. Similarly the motor torque is given by

$$T = k_e \phi I_a$$

A 4 pole generator having wave wound armature winding has 5 slots and each slot containing 20 conductor. What will be the generated voltage when the machine is rotated at 1500 rpm & flux per pole is 7 millivolt.

$$\Delta V = \frac{E}{N} = \frac{NP\phi}{60} \times \frac{Z}{A}$$

$$E = 5000 \times 2 \times 7 \times 10^{-3} \times \frac{1020}{60} = 3570 \text{ V}$$

## Application of DC machine :-

DC generator :- (i) DC generators are used for light and power supply purpose.

(ii) It is used for charging batteries & lighting &

(iii) It is used for dc loco motive for

the braking for dc breaking.

DC Motors :- (i) It is used for the products of high starting torque.

(ii) It is used in steel rolling mills, paper mills, etc.

(iii) It is used where very accurate speed is required.

(iv) It is used for traction work like lifts, trains & in electric railways.

Speed control of a DC Motor  $\Rightarrow$  The speed of a DC motor is given by the relationship

$$N = \frac{V - I_a R_a}{K_f}$$

The above eqn shows that the speed is dependent upon the supply voltage  $V$ , the armature resistance  $R_a$  & the field

flux  $\Phi$  in practice the variation of these three factors is used for speed control. Thus, there are 3

DATE : / /  
PAGE NO. :

DATE : / /  
PAGE NO. :

general method of speed control of DC motor :-

(i) Variation of resistance in the armature circuit  $\Rightarrow$  This method is called armature resistance control.


(ii) Variation of field flux  $\phi \Rightarrow$  This method is called field flux control.

(iii) Variation of applied voltage  $\Rightarrow$  This method is called armature voltage control.

Armature resistance control :- In this method a variable series resistor  $R_a$  is put in the armature circuit.

In this case the field is directly connected across the supply and flux  $\phi$  is not affected by variation of  $R_a$ .

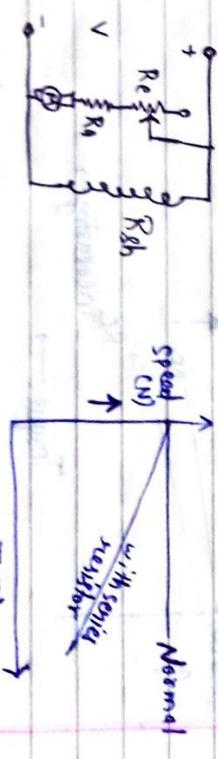The voltage drop in  $R_a$  reduces the voltage applied to the armature & therefore the speed is reduced. This method is only used for small motors.



(ii) Field flux control  $\Rightarrow$  Since the flux is produced by the field current the control of speed by this method is obtained by controlling the field current. In th-

Shunt motor this is done by connecting shunt resistor  $R_c$  in series with the variable resistor  $R_b$ . The resistor  $R_b$  is called the shunt field regulator.

$$I_{sh} = \frac{V}{R_{sh} + R_c}$$

The connection of  $R_c$  in the field reduces the field current and hence the flux is also reduced. The reduction in the flux will result in an increase in the speed. Consequently the motor runs at a speed higher than the normal speed. For this reason the method of speed control is used to give motor speed above the normal.



Q. DC shunt machine connected to 250 volt supply

has an armature resistance of 0.2 ohm and the field circuit resistance is 100 ohm.

Find the ratio of speed as a generator to the speed as a motor, the line current in each case is 80A.

$$N_1 = \frac{V + I_a R_a}{K_p} = \frac{250 + 80 \times 0.2}{0.12} = 2000$$

$$N_2 = \frac{V}{K_p}$$

$$N_2 = \frac{V - I_a R_a}{K_p}$$

$$\frac{N_1}{N_2} = \frac{V + I_a R_a}{V - I_a R_a}$$

Torque  $\rightarrow$

$$T_{sh} = \frac{V}{R_{sh} + R_c} = \frac{250}{0.12 + 100} = 2.49 \text{ A}$$

(iii) Armature voltage control  $\Rightarrow$  Speed control of DC motor can

also be obtained by varying the applied voltage to the armature. This method

of speed control is based on the principal of Ward-Leonard system. Since the speed control is carried out with the started current  $I_a$  with constant motor field flux  $\Phi_m$ . A constant torque upto the base speed is obtain. Hence, with the armature voltage control method constant torque is obtained from the speed below the base speed.

where  $N_0 = \text{no load speed}$

$N_F = \text{full load speed of the motor}$

- Q. A long shunt compound generator delivers a load current of  $50A$  at  $500V$  & a load current of  $0.05A$  and short circuit current of  $0.003A$  and short circuit current of  $0.05A$ . calculate the generator voltage & the armature current.

$$\text{Ans. } I_a = I_{se} - I_L = 50A$$

$$I_a = I_L + I_{sh} \quad \sqrt{= 500V + 1}$$

$$I_a = 50 + 2 = 52A \quad R_a = 0.05\Omega$$

$$R_{se} = 0.003\Omega$$

$$R_{sh} = 250\Omega$$

$$E_g = V + I_a R_a + I_{se} R_{se}$$

$$T_{sh} = \frac{V}{R_{sh}} = \frac{500}{250} = 2$$

(i) Single phase induction motor  $\Rightarrow$

$$E_g = 500 + 52 \times 0.05 + 52 \times 0.003$$

$$E_g = 500 + 2.6 + 0.156$$

$$E_g = 502.756 \text{ V.A.F}$$

260


Speed regulation  $\Rightarrow$  It is defined as the change in speed from full load to the no-load and it is expressed as a percentage of the full load speed

$$\% \text{ Speed regulation} = \frac{N_0 - N_F}{N_F} \times 100$$

$\phi_A = \phi_m \sin \omega t$

$$\frac{53}{156} \quad \phi_B = \phi_m \sin(30^\circ + \omega t)$$


figure (i)

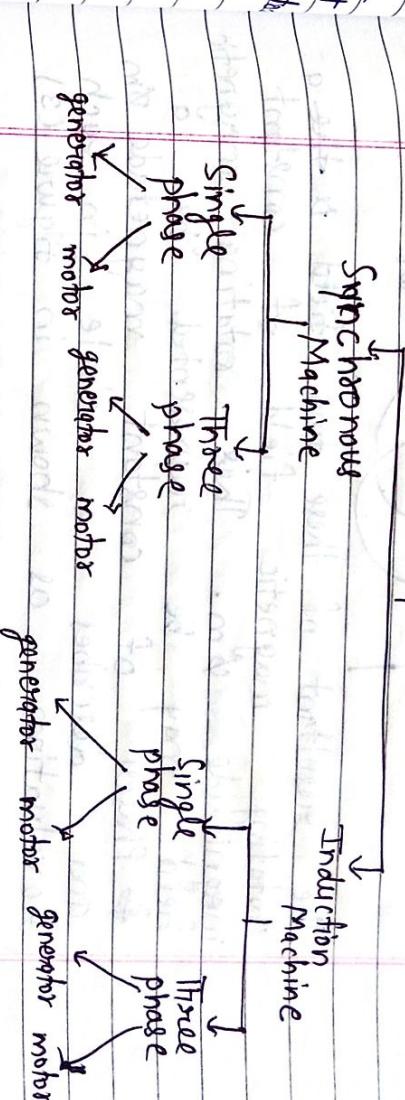

The waveforms of the field are shown in the figure (2).



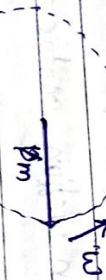The resultant of these two fields is the rotating magnetic field of constant magnitude  $\phi_m$ . This rotating magnetic field may be represented by a rotating field of constant magnitude  $\phi_m$  and described as shown in figure (3) and evaluation.




### single phase induction motor principle

A single phase induction motor consists of a single phase winding mounted on the stator and a cage winding on the rotor when a single phase supply is connected to the stator winding a pulsating magnetic field. Under these conditions the rotor doesn't rotate due to the inertia there from a single phase induction motor is inherently not self starting and requires some special starting means. If however the single phase stator winding is

excited and the rotor of the motor is started by an auxiliary means and the starting device is then removed, the motor continues to rotate in the direction in which it is started.
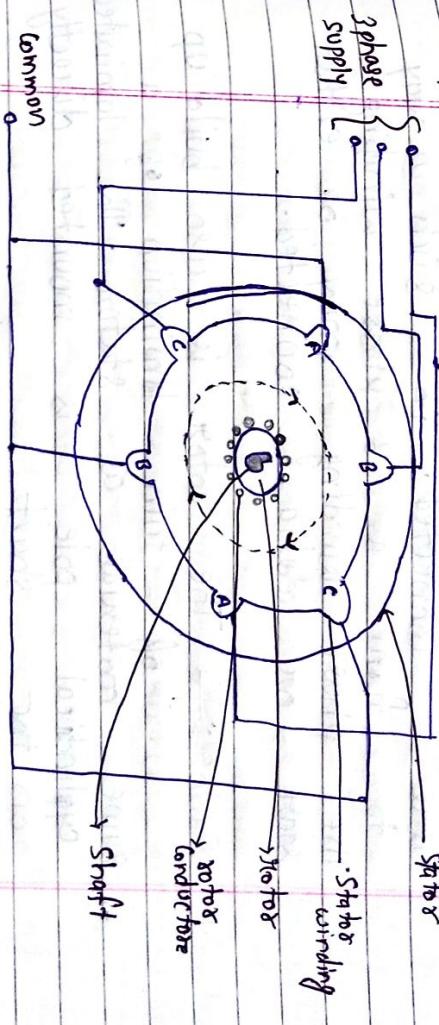
### Construction of a 3 phase induction motor:-



3 phase induction motor is the most popular type of AC motor. An induction motor doesn't require any starting device. So it is called self started. An induction motor is very commonly used for industrial drive since it is cheap, efficient, reliable and robust. It has good speed regulation and high starting torque and requires little maintenance. A 3 phase induction motor essentially consists of 2 parts. The stator & the rotor.

1.1) **Stator** :- The stator is the stationary part build up of high grade laminations. The laminations are made of steel and are insulated from each other. The laminations are placed in such a way to form a 3 phase winding. The phase winding may be either star or delta connected.

2.1)

**Rotor** :- The rotor is also build up of thin laminations of a cylindrical pole mounted directly on the shaft. These laminations are slotted on their outer periphery to receive the rotor conductor. There are two types of induction motor rotors.

1.1) **Squirrel cage rotor**  
Phase wound or slip ring rotor

1.1) **Cage rotor** :- It consists of a cylindrical laminated core with slots parallel to the shaft axis. Each slot contains bars of aluminum or copper at each end of

rotor. The rotor bars conductors are short circuited by heavy and rings to form a cage of the tire.

2.1)

**Slip ring rotor** :- The wound rotor consists of a slotted armature. Slotted conductors are placed in the slots and connected to form a 3-phase double layer distributed winding similar to the stator winding. The rotor winding are connected in star. And brought outside of the rotor & connected to the 3 insulated slip rings. Which are mounted on the shaft with brushes resting on them.

**Synchronous speed**  $\Rightarrow$  It is the speed of rotation of the magnetic field in the stator winding of the motor at which emf is produced by the AC machine. And it is given by

$$N_S = \frac{120f}{P}$$

where  $f$  is frequency &  $P$  = No. of pole

**Cogging** or magnetic locking  $\Rightarrow$  Sometimes even when full voltage is applied to the stator winding the motor of a 3 phase cage induction motor fails to start this happens when the no. of stator & rotor slotted a

Let us consider a 3 phase induction motor as shown about with stator & rotor wound for 3 phase and having an identical no. of poles. Initially assume that the motor winding is open circuit and the stator is connected to a 3 phase supply.

As we know that when the stator winding carries the 3 phase current a rotating magnetic field is produced in the air gap b/w the stator and the rotor which runs at the synchronous speed.


This rotating magnetic field induces an emf in the stator winding which balances the supply voltage and at the same time this emf (rotating) also induces the emf in the rotor winding. But as the rotor is open circuited so no rotor current flows and the rotor remains stationary. Now if the rotor winding is short circuited so the rotor winding will carry a 3 phase current due to the induced emf in rotor.

Now the motor behave like a current carrying conductor placed in the rotating magnetic field of the stator and experiences a torque. Hence the motor starts rotating.
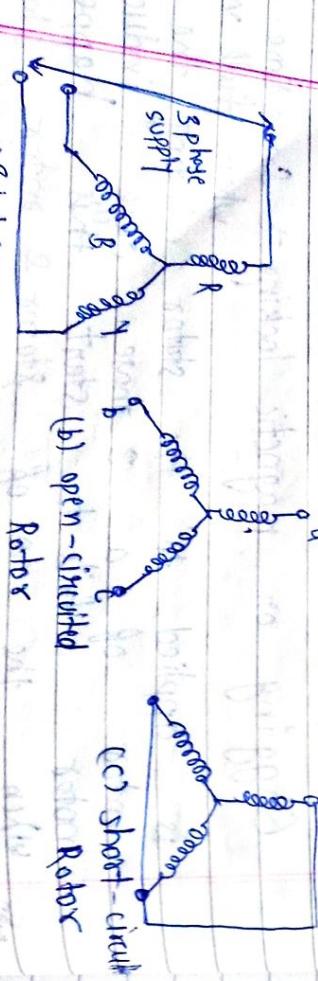
### # Principal of operation of a 3 phase induction motor

$\Rightarrow$

Principal of operation of a 3 phase synchronous generator  $\Rightarrow$  The working principle of these machines are governed by two



Principal of operation of a 3 phase synchronous generator  $\Rightarrow$

The working principle

long:- law of electro magnetic induction

1.1 Faraday's law of interaction

2.1

Faraday's Law of EMI  $\Rightarrow$  According to this law is used as a generator and emf is induced in the armature conductors when ever cut by the magnetic field.

2.1 Law of interaction  $\Rightarrow$  This law relates to the production of force or torque that is when ever a current carrying conductor is placed in the magnetic field produced by the main field producing conductor and the current force is exerted on the conductor producing torque. So the

mechanical power spent in maintaining the relative motion of the conductor is converted into electrical energy.

EMF equation of AC Machines:-

$$N_S = \frac{120f}{P}$$

$$\text{E} = \frac{\rho \phi N}{60} \times Z_{ph}$$

$$T_{ph} = \frac{Z_{ph}}{2}$$

$$e = \frac{\rho \phi N}{60} \times 2 T_{ph} \times \frac{2}{2}$$

$$e = \frac{4 \rho \phi N T_{ph}}{120} = 4 T_{ph} f \times \frac{N}{120}$$

$$(E_{ph})_{\text{ind}} = A_{ph} \times f \times \text{form factor}$$

$$= 4 \rho T_{ph} f \times (1.1)$$

$$E_{ph} = 4.44 \rho T_{ph} f$$

Q. A 3 phase star connected 2 pole alternator run at 3600 rpm if there are 500 conductor per phase and flux per pole is 0.1 weber determine the frequency & magnitude of the generated emf.

$$N_S = \frac{120 \times f}{P}$$

$$\frac{60}{2 \times 2} = f$$

$$f = 60 \text{ Hz}$$

$$E_{ph} = 4 \times 0.1 \times \frac{500}{2} \times 60 = \times 1.1$$

$$E_{ph} = 120 \times 100 = \frac{12000}{2} \times 1.1 = \frac{13200}{2} = 6600$$

$$\frac{V_L}{\sqrt{3}} = V_p$$

$$E_L = \sqrt{3} \times 6600 = 1.73 \times 6600 = 22440$$

$$E_L =$$

**Ammature reaction**  $\Rightarrow$  In DC machine the main field is produced by field windings. In both generating and motoring mode the ammmature current produces a magnetic field called the ammmature flux. which is effect of ammmature flux on the distribution of the main field flux is called the "ammature reaction".

It demagnetizes and cross magnetizes the main field, decrease the value of flux per pole and increase the iron losses in the machine.

Torque Slip characteristic:

$$\text{we have } T = \frac{KS R_2 E_{20}^2}{R_2^2 + (SX_{20})^2}$$

where  $K$  = constant,  $s$  = slip speed

$R_2$  = resistance / phase of motor

$E_{20}$  = Emf induced / phase of motor at standstill

$X_{20}$  = reactance / phase of motor at standstill

if  $R_2$  and  $E_{20}$  are constant then the torque depend upon the slip. So the torque vs. slip characteristic curve can be divided into 3 regions:

PAGE NO. : \_\_\_\_\_  
DATE : / /

PAGE NO. : \_\_\_\_\_  
DATE : / /

1) Low slip region:- At synchronous speed  $s=0$

therefore the torque is also zero. when the speed is very near to synchronous speed the slip is very low and  $(SX_{20})^2$  is negligible in comparison with  $R_2$ . Therefore Torque =  $\frac{k_1 s}{R_2}$  if  $R_2$  is constant the torque is directly proportional to the slip. Hence the torque

slip curve is a straight line in this region.



2) Medium Slip region:- As the slip increase the

so that  $(R_2)^2$  becomes large

torque =  $\frac{k_3 R_2}{(SX_{20})^2}$  Thus the torque is inversely proportional to the slip. The torque

slip characteristic is represented by a rectangular hyperbola in this region. In doing so it passes through the point of maximum torque

where  $R_2 = X_{20}$  The maximum torque developed in an induction motor is called "pullout & breakdown torque".

**High Slip reason:-** The torque decreases beyond the point of max. torque as a result the motor slows down and eventually stop in this reason. At this stage the over load protection must immediately disconnect the motor from the supply to prevent damage due to over heating.

**Slip  $\Rightarrow$**  The difference b/w synchronous speed and actual rotor speed is called slip. And it is expressed as

$$S = \frac{N_s - N}{N_s} \times 100$$


**Starting of Induction Motor  $\Rightarrow$**  The following are the common used starters for induction motor :-

- (i) Direct - on - line starter :-

3 phase supply

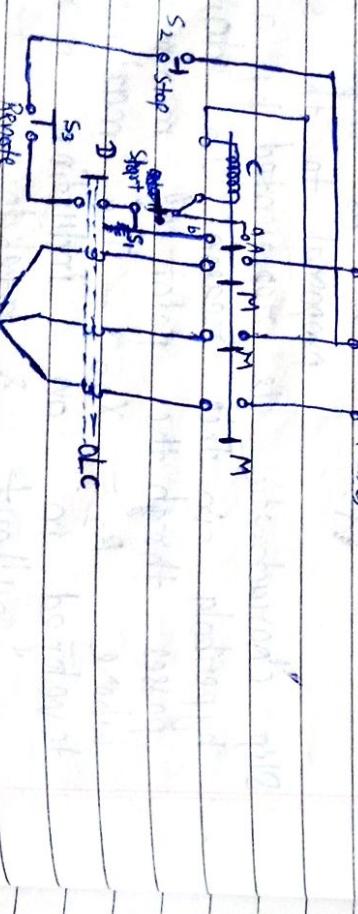
2.1 Auto transformer starter :-

Both star and delta connected motors. In this method the starting current is limited by using a 3 phase auto transformer to reduce the initial starting applied voltage. The auto transformer is provided with a no. of tapping. The Starter is connected on one of the tapping



In this method starting the motor is connected by means of a direct-on-line starter. It consists of coil controlled by start and stop buttons. C is energized from the 2 line conductors  $L_1$  &  $L_2$ . The 3 main connects M & the auxiliary contact A closed and the terminals a & b are short circuited. So the motor is connected to the supply and starts rotating. When the pressure on  $S_1$  is released, even then the coil C remains energized and the contacts M remain closed. When the stop push button  $S_2$  is pressed the supply through the coil C is disconnected and it becomes de-energized and the main contact M and auxiliary contact A become open. So the supply to the motor is disconnected and the motor stops.

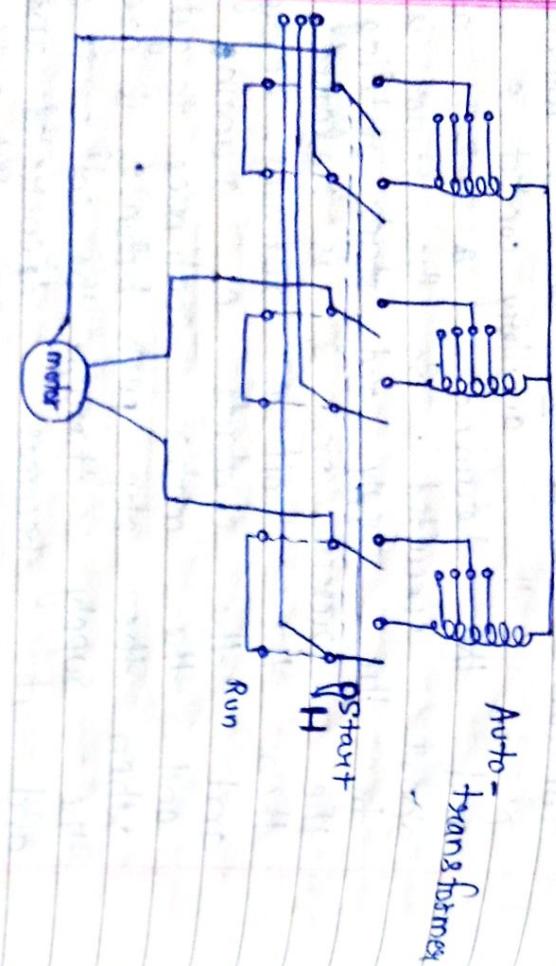To obtain the most suitable starting voltage. A double throw switch is used to connect to auto transformer used in the circuit with the help of the handle H as shown in the figure below




Speed control of induction motor  $\Rightarrow$  The speed of an induction motor is given by

$$N_m = \frac{120f}{P} (1-s)$$

from the above eqn it is seen that the motor speed can be changed by a change in frequency  $f$ , no. of pole  $P$  and

A Star-delta starter is used to run normally on delta connected stator winding. The figure shows the connection of a 3-phase induction motor with a star-delta connection. In the start position, the switch  $S$  is connected in star. When the switch  $S$  is connected in the start position, the motor picks up the speed quickly. To the run position, the switch  $S$  is thrown over. By connecting the stator winding in delta, the line current in star and then in delta is reduced by one third ( $\frac{1}{3}$ )rd. So in this method the starting torque is reduced to ( $\frac{1}{3}$ )rd that obtained by direct delta starting.

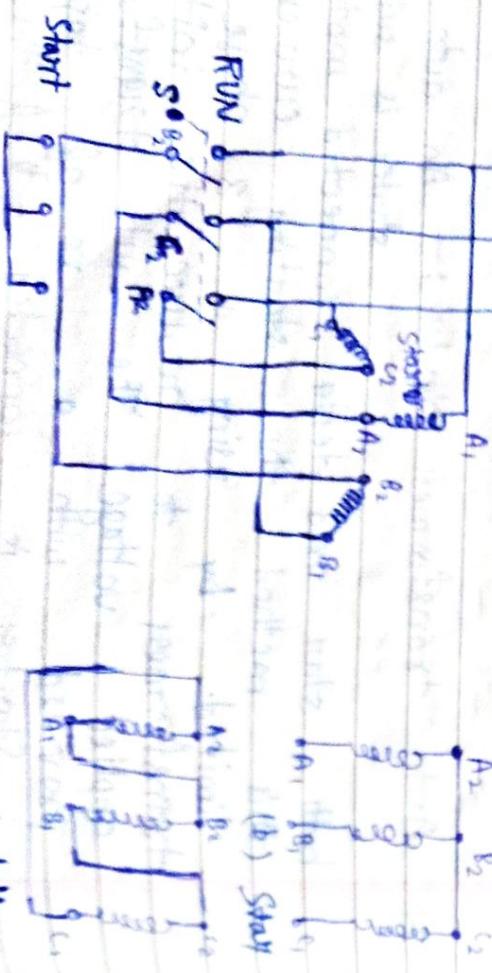

slip 's'. The main method used for speed control of induction motor are as follows :—

- (i) By changing the no. of stator pole.
- (ii) Stator voltage control
- (iii) Supply frequency control
- (iv) Rotor resistance control
- (v) Slip energy recovery

(i) By Pole changing method :— The method of speed control by

pole changing are suitable for cage rotors only because the cage rotor automatically develops no. of poles equal to the poles of the stator winding. So by changing the no. of stator poles we can control the speed of the rotor. The no. of stator poles can be changed by 3 method


- (i) Multiple stator winding method
- (ii) Method of consequent pole amplitude
- (iii) Pole changing method

(ii) Stationary voltage control :— The speed of the 3-phase induction motor

motor can be varied by varying the supply voltage. We know that

$$T = \frac{K_s E_2^2}{R_2^2 + (s\omega_0)^2}$$

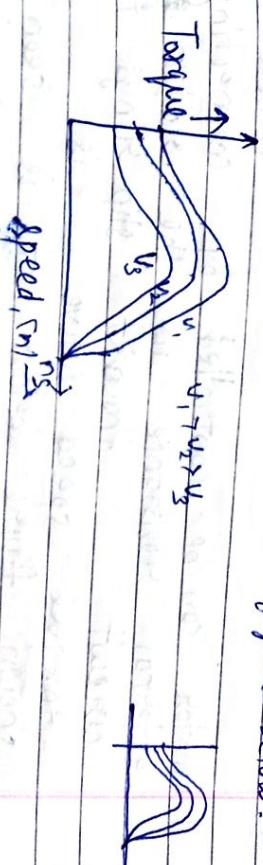From this relation torque developed is directly proportional to the square of the supply voltage. So the speed control obtained by varying the supply voltage



(iii) Variable frequency control  $\Rightarrow$  The synchronous induction motor is given by  $N_s = \frac{120f}{P}$

therefore the synchronous speed and the speed of the motor can be controlled by the varying the supply frequency. The emf induced in the stator of the induction motor is given by  $E = 4.44 T \sin \theta$ . Therefore if the supply frequency is changed by the supply voltage  $E_2$  will also change to maintain the same air gap flux. Consequently the torque is also changed by changing the supply voltage. Thus the speed control of an induction motor can be done by using variable frequency supply. Which requires a variable voltage source. The variable frequency

until the torque required by the load is developed at the desire speed. Therefore as the no. of poles is reduced to reduce the speed reduces. The torque developed by the motor also a 3 phase induction motor for varying supply voltage is shown in the figure below :—

Supply is generally obtained by the following

(i) Voltage source inverter

(ii) Current source inverter

(iii) Cyclo converter

④ Rotor resistance control  $\Rightarrow$  The speed of induction


motor can be controlled by connecting external resistors in the rotor of the circuit through slip rings the

torque speed curve is shown figure below it is seen that when the value of  $R_2$  is increased as a result the slip will also increase and consequently the pull out torque decreases but maximum speed remain constant.

Therefore by this method control is provided to rated speed to low speed.



$$S_m = \frac{X_2}{R_2}$$

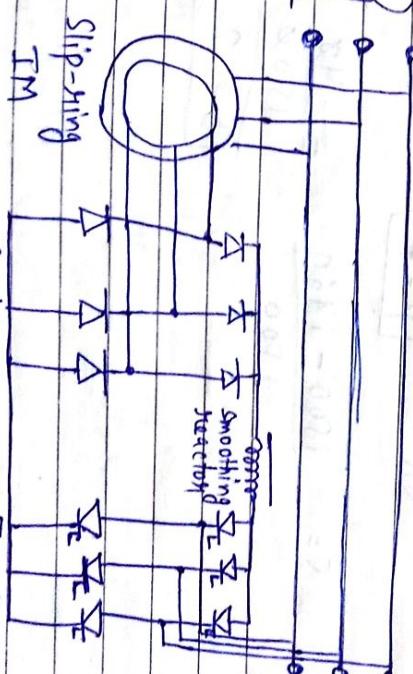

⑤ Slip energy recovery  $\Rightarrow$

In the rotor resistance control the slip power is wasted as  $I^2 R$  loss during the low speed operation.

So the efficiency of the dry system by this method of speed control is reduced. So the slip power from the motor circuit can be recovered and fed back to the AC source thus the over all efficiency can be increased. This method for recovering the slip power is known as static

Scheibeus drive. In this method a position of the rotor AC power is converted into DC. By a diode rectifier. The rectified current is smoothed by the smoothing reactor then the output of the rectifier is fed to the DC terminal of the inverter. Then the output is inverted into AC power as feed its back to the AC source. This method is used large power application.

Q. An induction motor runs at 1460 rpm under fullload condition when supplied by 50 Hz supply find the No. of pole & slip of the motor?

$$\text{Ans. } N = 1460 \text{ rpm}$$

$$f = 50 \text{ Hz}$$

$$N_s = \frac{120f}{P}$$

$$P = \frac{120 \times 50}{1460} = \frac{6000}{1460} = \frac{300}{73}$$

$$N_s = \frac{120f}{P}$$

if  $P=2$

$$N_s = \frac{120 \times 50}{2} = 3000$$

$$N_s = \frac{120 \times 50}{4} = 1500$$

$$N_s = \frac{120 \times 50}{4} = 1500$$

$$S = \frac{1500 - 1460}{1500} = \frac{40}{1500} = 0.026$$

(iii) Single phase full wave rectifier with R-load :-

$$S = 2.6 \text{ v.}$$






Semiconductor

$$0 \quad 0 \quad 0 \quad 0 \quad 0$$

$$J=E$$

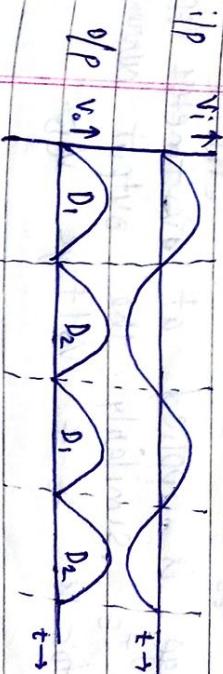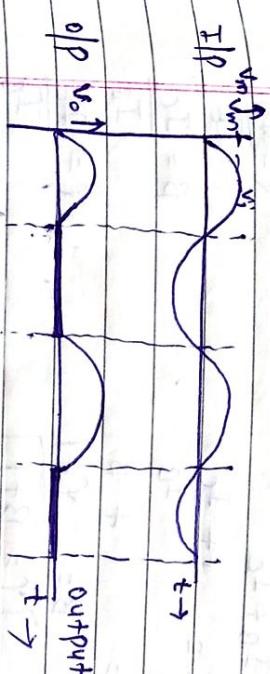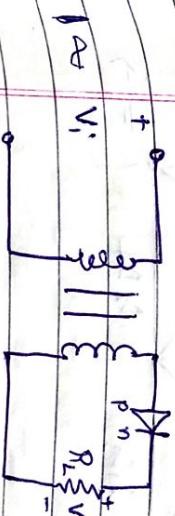
(i) Single phase half wave rectifier with R-load:-



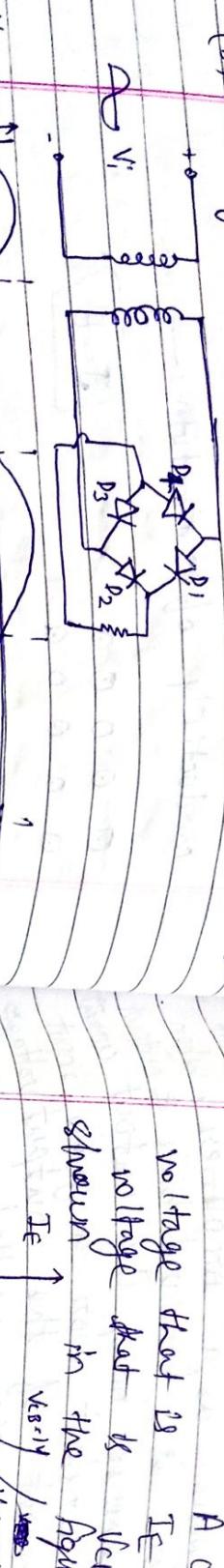(b) Bridge rectifier (In full wave rectifier)

input characteristic:—

A curve is drawn below current  $I_E$  &  $V_{EB}$  at const. output voltage that is  $V_o$ . And the input characteristic shown in the figure below:—



$$I_F = I_B + I_C$$

$$\frac{I_F}{I_B} = 1 + \frac{I_C}{I_B}$$

$$\beta = \frac{I_C}{I_B}$$

$$V = 1 + \beta$$


$$V = \frac{I_F}{I_B}$$

$$r = \beta + 1$$

Transistor configuration:—

i)

CB

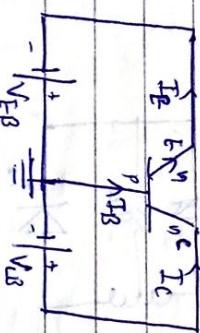

The input voltage  $V_{in}$  is applied at a voltmeter  $V_{EB}$  & current  $I_E$ . Similarly the output current at collector is  $I_C$  & voltage  $V_{CB}$ .

Output characteristic:— The curve of output current  $I_E$  v/s output voltage  $V_{CB}$  are plotted for the constant value of input current  $I_E$ . And the output char. is shown in below:—



The three region of operation of a transistor can be seen on the output characteristic curve.

(i) Active region:— In this region the transistor work as a amplifier when forward bias is applied.

~~forward reverse~~ the input junction is forward bias when junction is reverse bias. The output current  $I_C$  is almost constant for a given input current independent of the output voltage  $V_{CB}$ . That is why BJT is called a current control device.


Cut off region:— When the input junction is in reverse bias and the device is set to be off. This region lie below  $I_E = 0$ .

How ever a small character current flow due to minority carriers lie below  $I_E = 0$ .

(ii) Saturation region:— The output junction is forward biased and the transistor is said to be saturated. This region lie at the left of  $V_{CB} = 0$ . In this region a small change in  $V_E$  will rapidly increase the  $I_C$ .

Note:- Early effect:— As the collector voltage  $V_C$  is made to increase the reverse bias the space charge width of collector of base tends to increase with the result that the effective width of the base decrease. So this dependence of base width on collector to emitter voltage is known as the early effect.

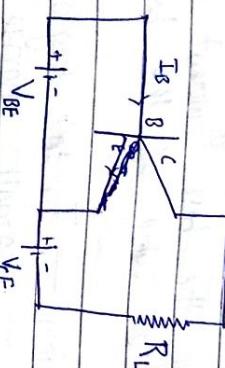(ii) Common emitter configuration:— Transistor in common emitter ~~configuration~~ is shown in figure below.



(a) Input characteristics:— To determine the input char. the collector to emitter voltage  $V_{CE}$  is kept constant and the base current is increased from zero in equal steps by increasing  $V_{BE}$  as shown in figure below.


$$I_B \uparrow$$

$$V_{BE} \uparrow$$

In input char. for a fixed value of  $V_{BE}$  base current reduces for an increase in voltage  $V_E$  due to the early effect.

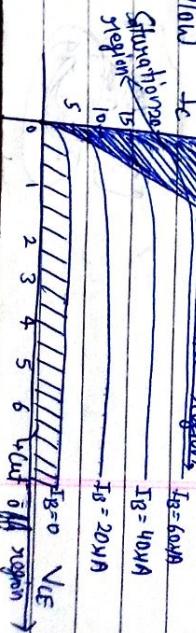(b) Output characteristics:— The curve of the output current  $I_C$  vs output voltage  $V_E$  are plotted for different constant values of input current  $I_B$ .

The output char. curve drawn for the 3 region of a operation of a transistor as shown in figure below.



(i) Active region:— In this region transistor work as an amplifier. In this region the effect of the collector voltage is very small for low value of the base current but increases with the value of the base current.

(ii) Saturation Region:— In this region of operation a small change in  $V_{CE}$  forward bias the output junction and the transistor is said to be saturated. In this region a small change in  $V_{CE}$  will rapidly increase the  $I_C$ .

(iii) Cut off region:— In this region of operation the input junction is reverse biased so the device is said to be off. This region lies below  $I_B = 0$ . However a small collector current flows due to minority carriers.

(iii) Stray loss:— Leakage flux in a transformer produces eddy current in the conductor, transformer oil etc. And these eddy currents are responsible for stray losses.

(iv) Dielectric loss:— It occurs in the insulating material such as in the transformer oil and in solid insulation of transformers. The stray loss & dielectric loss are usually very small so there existance will be negligible in an transformer.

$$15 - 8I_1 - 3I_1 + 3I_2 + 8I_3 = 0$$

$$\text{or } 15 = 11I_1 - 3I_2 - 8I_3 \quad \text{--- (1)}$$

$$5I_3 + 3I_1 = 10I_2 \quad \text{--- (2)}$$

$$5I_2 + 8I_1 = 23I_3 \quad \text{--- (3)}$$

## Unit #4


# BASIC ELECTRONICS

### \* Introduction :
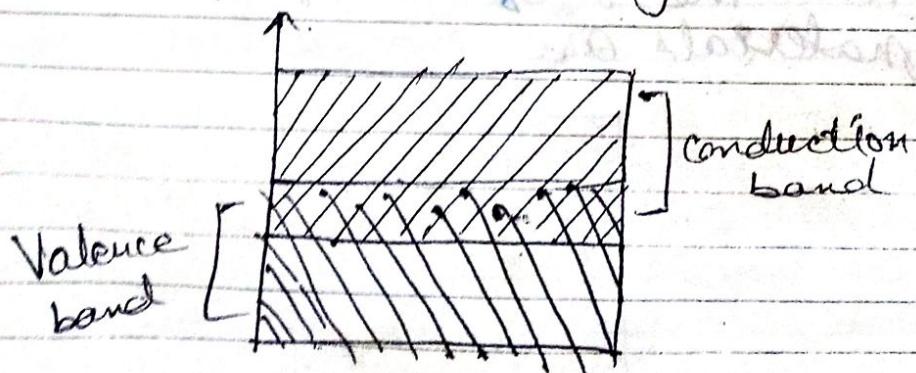
#### Conductivity :


Conductivity refers to the ability of a material to generate free electrons to conduct current. These free electrons are generated by providing excitation energy to the electrons in valence band to move to the conduction band.

Conductors (Metals) : In the absence of the energy gap, a large number of electrons are available for conduction at room temp. So without conduction even at room temp. Such materials conduct easily and hence called as conductor. e.g copper, iron etc.


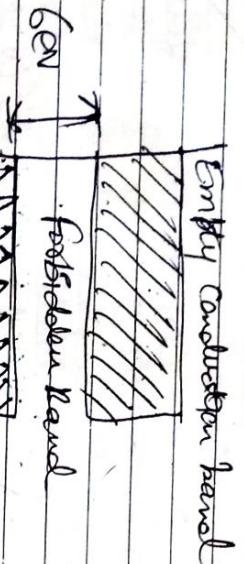
## (b) Insulator :

Large forbidden gap between the energy bands approx.  $E_v$ . So it becomes impossible for an electron to jump from valence to conduction band. So such materials do not conduct called an insulator. Eg Diamond.



## (c) semi-conductor :

The material for which the forbidden gap is relatively very small is called a semi-conductor. Eg. The most important semiconductor materials are Germanium and Silicon.



Now, at room temperature a no. of electrons in valence band absorb the thermal energy from surrounding due to this they break covalent bond and drift to conduction band.

## Semi-conductors :

\* Semi-conductors have resistivity in between that of conductors and insulators. They have negative temp. coefficients of resistance and when suitable metallic impurities are added, the conductivity of semi-conductors change.

Based on the absence and presence of these impurities semi-conductors are classified as intrinsic and extrinsic semi-conductors.

## Intrinsic (pure) semi-conductors :

A piece of semi-conductor in its purest form is known as Intrinsic semi-conductor.

At 0°temp. no free electron is available as the electrons in the valence shell makes bond with share the valence electrons of other neighbouring atoms to attain a certain position in valence shell and get completely filled and stable. So they behave as perfect insulator.

So each electron shifted to conduction band one hole is created in valence band. Thus free electrons and holes are generated in the intrinsic semiconductor.

### \* Extrinsic Semiconductors:

When some impurity generally referred to as dopant is added to intrinsic semiconductor, its conductivity can be increased. These types of semi-conductor are called extrinsic semiconductors.

The process of adding impurity is called doping. The dopant added is generally of two types, either trivalent or pentavalent atoms.

When an extrinsic semiconductor is doped with pentavalent atom i.e. atom having five electrons in its valence shell it is called donor doping. This type of doping creates more number of free electrons and results into N-type of semi-conductor.


When an extrinsic semiconductor is doped with trivalent atom i.e. atom consisting of three electrons in valence shell, it is called acceptor doping. This type of doping creates more number of holes and resulting

extrinsic semiconductor is called as P-type semiconductor.
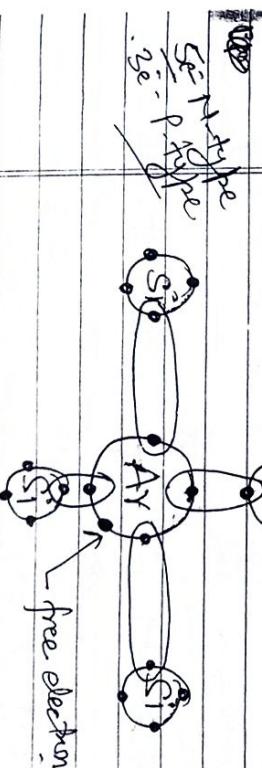
### N-type semi-conductor:

To form N-type semiconductor, pentavalent impurity such as Antimony, phosphorus and arsenic is added to intrinsic semiconductor. After donating one electron, each dopant atom acquires a positive charge.

Conduction in N-type is due to free electrons so they are called majority carriers and the holes are small in number they are called as minority carriers.



so, as the donor impurity is added, energy level, are also introduced just below the conduction band. The donor energy level is 0.05 eV distance below the conduction band.


(2)

(b) P-type semi-conductor:

When a small amount of trivalent impurity such as Boron, Gallium or Indium is added to an intrinsic or pure semi-conductor it is called a P-type semi-conductor.

In this, the three valence electrons of the silicon makes covalent bond with the three adjacent silicon atoms. Due to shortage of one electron the fourth covalent bond remains incomplete. This results in vacant space called as hole.

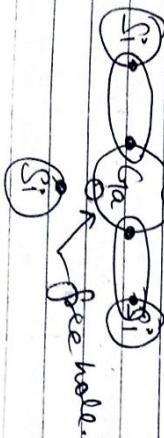In P-type semi-conductors, the carrier conduction is due to holes, hence holes are majority carriers and the free electrons are small in number. They are called as minority carriers.



Si  
Free hole.



$$\begin{aligned} J &= J_n + J_p \\ J &= q \cdot n \cdot v_n E + q \cdot p \cdot v_p E \\ J &= q [n v_n + p v_p] E \end{aligned}$$

\* Conductivity of Semiconductor:

In a pure semiconductor, the no. of holes are equal to the no. of free electrons. Under each electron-hole pair, created two charge-carrying particles are formed. One is negative which is free electron with mobility  $\mu_n$  and other is positive i.e. the hole with mobility  $\mu_p$ .

The mechanism by which hole contributes to conductivity is that when hole exists, the valence electron can jump into it and thus hole leaves its original position. Hole moves in the opposite direction to the electron.

- (a)   
(b)

So, the total current density  $J$  is:

(4)

Depletion region : It is an insulation region within a conductive material. When the mobile charge carriers have been diffused away behind the impurities.

- \* For pure semi-conductor,  $n = p = n_i$  where  $n_i$  is referred to as intrinsic concentration.

$$\text{So } J = n_i^2 (\text{saturation})$$

$$\text{Or } J \propto n_i^2 (\text{saturation})$$

- \* For N-type semiconductor,  $n > p$ .

$$\text{So } J \propto n^2 n_i \text{ etc.}$$

Unit of conductivity is  $\text{S/m}$ .

- \* For P-type semiconductor,  $p > n$ ,

$$\text{So, } J \propto p n_i^2 \text{ etc.}$$

Diode is a one-way device which allows the current to flow in one direction.

- \* Conduction in Semiconductor diode :

If the donor impurities are introduced into one side and acceptors into the other side of a single crystal of a semiconductor, a p-n junction is formed

p-type material and n-type materials have higher concentrations of electrons and holes resp. So at the junction there is a tendency for the free electrons in N-type material to diffuse

from the P-side and holes from P-type to the N-side. This process is called diffusion. When the electrons diffuse to P-type region and holes to N-region, there is a region of charged zones formed at the junction side, the region of the junction is depleted of the mobile charges. It is called depletion region.

And at a result a potential difference is established between the N-type and P-type regions which is called potential barrier. (V<sub>f</sub>).



$$V_f = V_T \ln \frac{N}{n_i^2}$$

$$V_f = V_T \ln \frac{N}{n_i^2}, \text{ where } V_T = T/11600$$

## \* Biasing of a PN Junction:

If voltage is zero, there is no current through the junction.


In order to break current flow through the junction, we need to apply some potential to the P-N diode.

The application of DC voltage across the diode is called biasing.

\* There are two type of biasing:

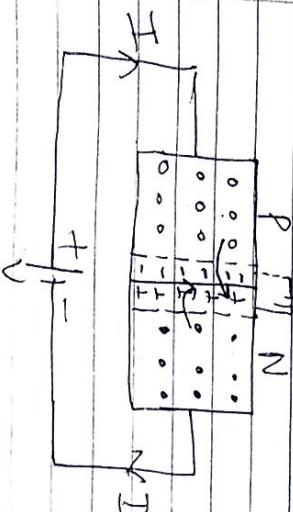(i) Forward biasing:

A diode is said to be forward biased, when an external voltage source is connected with its positive terminal towards the P-side of the diode and negative towards the N-side of the diode.



(ii) Reverse bias:

When the negative terminal of the battery is connected to the P-side and positive terminal of the battery is connected to the N-side of the P-N junction, the bias applied is known as reverse bias.


Due to this the holes of the P-side moves or attracted towards the negative terminal of the battery and electrons from the N-side are at the positive terminal of the battery so as a result the width of the depletion region increases, the potential barrier is increased which prevent the flow of majority carriers.

When the applied voltage is greater than the potential barrier ( $V_b$ ), then

the holes in the P-side are repelled by the positive terminal of the battery and forced to cross the junction.

Similarly the electrons on the N-side are also repelled by the negative of the battery and force to cross the junction so this results in the reduction of the potential barrier and allows large forward current to flow.

(2)

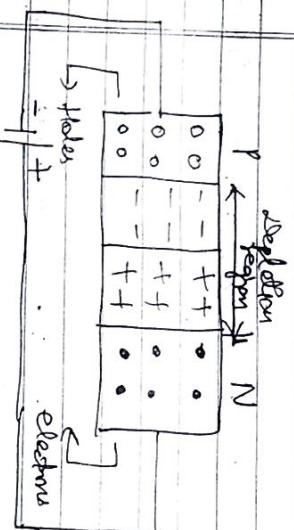

Variation of diode current is given by,

$$I = I_0 \left( e^{\frac{V}{nV_T}} - 1 \right).$$

where  $V_T = \frac{kT}{q} = 11600/T$ ,  $T$  is temp.


$n = 1$  for Ge, 2 for Si

$I =$  Current through diode

$V =$  Applied voltage

$I_0 =$  Reverse saturation current

V-I characteristics:

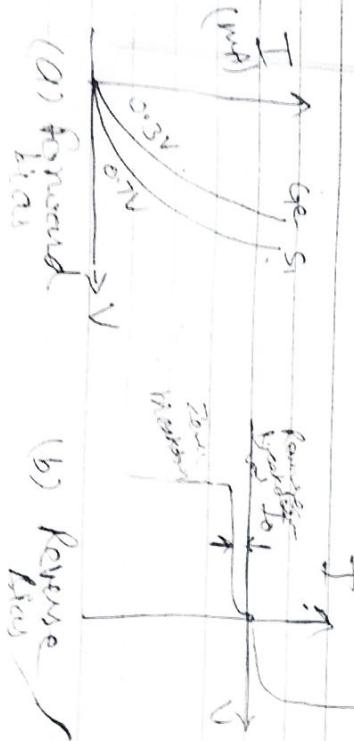

(a) Forward bias

(b) Reverse bias


### Rectification

Rectifier is defined as an electronic device used for converting AC voltage into unidirectional voltage or DC voltage. It uses the conduction diode.

They are classified depending upon the period of conduction:

Half-wave rectification

Ful-wave rectification

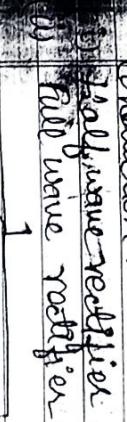

Half wave rectifier:

The basic circuit and waveforms of a half wave rectifier is shown below:



It uses a single diode which conducts in one half of the input AC cycle, thus, pulsating DC voltage is obtained for half cycle of input AC hence, the circuit is called half wave rectifier.

(7)

Let the  $V_i$  be the voltage to the primary of the transformer and given by the eq

$$V_i = V_m \sin \omega t$$

Case 1: During the positive half cycle of the input signal, the p-side of diode becomes more positive with respect to the cathode and hence, diode D conducts. So the whole input voltage will appear across the load resistance  $R_L$ .

Case 2: During negative half cycle of the input signal, the p-side of the diode becomes negative with respect to the Cathode and hence, diode ~~D~~ is reversed biased and so does not conduct. So the voltage across  $R_L$  is zero.

(i) Avg. Value :

$$V_{avg} = \frac{1}{2\pi} \left[ \int_0^{\pi} V_m \sin \omega t d(\omega t) + \int_{\pi}^{2\pi} 0 d(\omega t) \right]$$

$$V_{avg} = \frac{V_m}{2\pi} \left[ -\cos \omega t \right]_0^{\pi}$$


$$\boxed{V_{avg} = \frac{V_m}{\pi} = 0.318 V_m}$$

(ii) Full wave rectifier:

(i) Centre Tap rectifier:

full wave rectifier is an electronic device that converts an A.C voltage into a pulsating Dc voltage using both half cycles of the applied A.C voltage.

It uses two diodes of which one conducts during one half cycle while the other diode conducts during the other half cycle of the AC voltage.

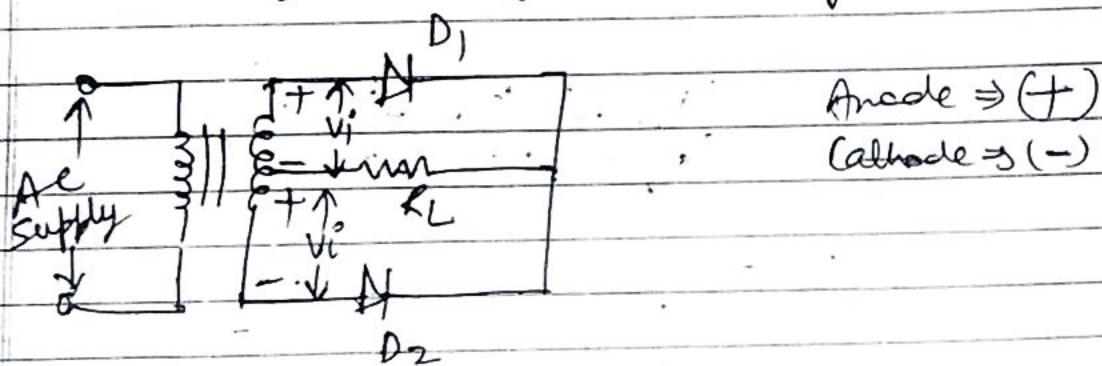


Case I: During positive half cycle, the p side of  $D_1$  becomes positive and at the same time, the anode of diode  $D_2$  is negative so  $D_1$  conducts and  $D_2$  does not conduct.

Case 2: During negative half cycle of the  $D_2$  becomes forward biased and  $D_1$  becomes reversed biased so  $D_1$  does not conduct and  $D_2$  conducts.

(10)

X

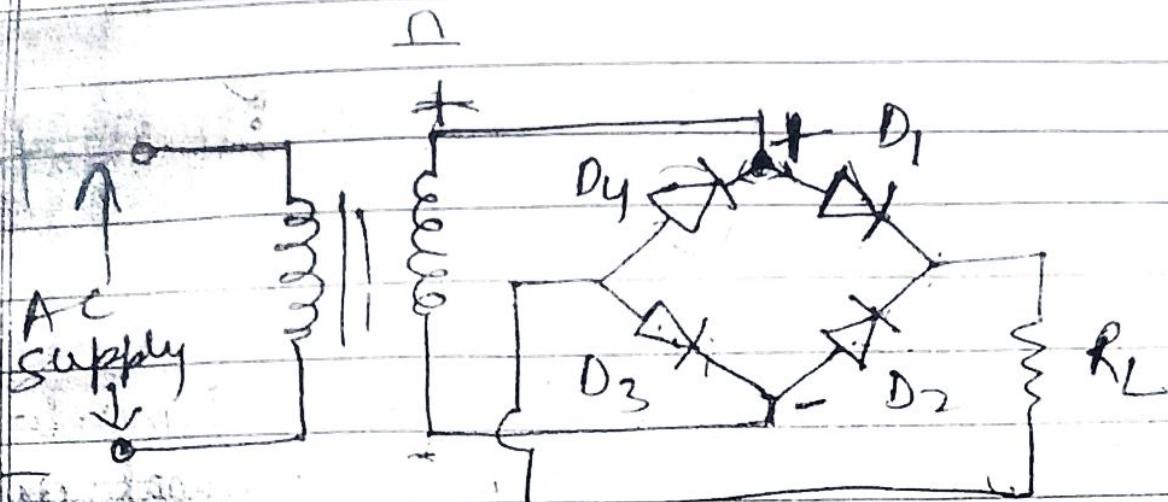

Case I: For positive half cycle of the input AC voltage, diodes  $D_1$  and  $D_3$  conduct whereas  $D_2$  and  $D_4$  do not conduct and load current flows through  $R_L$ .

Case II: For negative half cycle of the input AC voltage, diodes  $D_2$  and  $D_4$  conduct whereas  $D_1$  and  $D_3$  do not conduct and load current flows through  $R_L$ .

\* K

## Bipolar Junction Transistor (BJT) :


A BJT is a three terminal semi-conductor device in which the operation depends on the interaction of both majority and minority carriers and hence the name bipolar). With three terminals, two junctions are present, hence it is a bi-junction device.

Transistor refers to as 'Transfer of power' because it transfers the signal from low resistance input junction to high resistance output junction.
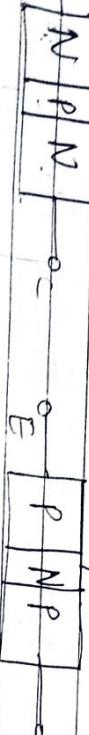
### Construction:

The BJT consists of a silicon crystal in which a thin layer of N-type silicon is sandwiched between two layers of P-type silicon. This transistor is referred to as PNP.

And when a thin layer of P-type is sandwiched between two layers of N-type silicon. This transistor is referred as NPN. And the three terminals are emitter, base and collector.



(a) NPN Symbol      (b) PNP Symbol



(ii) Base: This is the middle terminal of the three terminals which is thinnest of the three and it is more easily doped as it has less resistance.

(iii) Emitter: The main function of this region is to supply majority carriers to the base and it is most heavily doped.

Collector: The main purpose of this terminal is to collect the carriers through base. The majority carrier area through the other two.

### Transistor Biasing:

The application of external voltages is referred to as biasing. After diodes, the functions of BJT can also be forward or reverse biased.

So depending on the nature of biasing transistor works in either of the three regions:

### (i) Active region or (mode):



When emitter-base junction is forward biased and collector-base junction is reverse biased

(a) NPN Symbol      (b) PNP Symbol

i) Emitter current:

$$I_E = I_{PE} + I_{NE}$$

$$\text{As } I_{PE} \gg I_{NE}$$

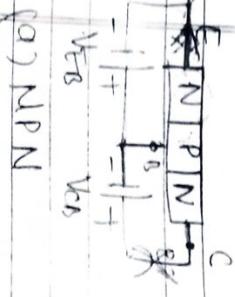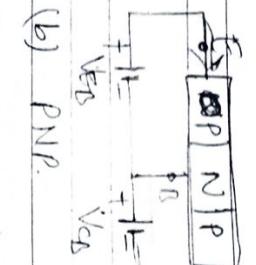

(a) NPN

(b) PNP.

(b)

Cut-off region: When both the junctions are reverse biased.

(c) Saturation region: When both the junctions are forward biased.

Transistor Current Components:

Collector current:

$$I_C = I_{PE} + I_{CO}$$

$$\text{and } I_{CO} = I_{PCO} + I_{NCO}$$

$I_{PCO}$  is due to holes.  
 $I_{NCO}$  is due to electrons.


So, net collector current?

$$I_C = I_E - I_{CO}$$

where  $\alpha > I_{PCO}$  is the large current gain  
and  $I_{CO}$  is the reverse saturation current

(iii) Base current:

$$I_B = I_{NE} + I_{PBE} - I_{CO}$$

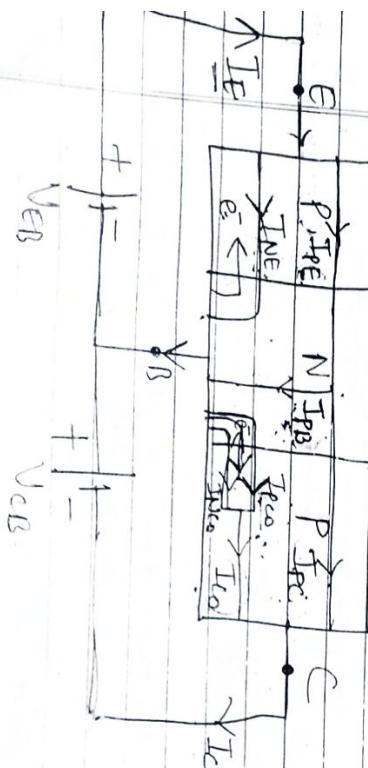

**Ampere Amplification factor:**

(i) The alpha factor ( $\alpha$ ):  $\frac{I_E}{I_C}$  ratio or  $\frac{\Delta I_E}{\Delta I_C}$

$$\alpha = \frac{I_C}{I_E} \text{ "Collector current"} \\ \text{or } \alpha = \frac{I_C}{I_E} \text{ "}$$

(ii) Beta factor ( $\beta$ ): Ratio of collector current to  $I_B$ .

$$\beta = \frac{I_C}{I_B}$$

(iii) Gamma factor ( $\gamma$ ): Ratio of  $I_E$

$$\gamma = \frac{I_E}{I_B}$$

**Relationship between  $\alpha$  and  $\beta$  and  $\gamma$ :**

$$\text{As we know, } I_E = I_B + I_C$$

Now, incremental change in output current

$$\Delta I_E = \Delta I_B + \Delta I_C$$

$$\Delta I_B = \Delta I_E - \Delta I_C$$

$$\therefore \beta = \frac{\Delta I_C}{\Delta I_B} > \frac{\Delta I_C}{\Delta I_E - \Delta I_C}$$

By dividing numerator and denominator by  $\Delta I_E$ , we get,

$$\beta = \frac{\Delta I_C / \Delta I_E}{\Delta I_B / \Delta I_E} = \frac{\alpha}{1 - \alpha}$$

$$\alpha = \frac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B} = \alpha(1 + \alpha)$$

$$\gamma = \frac{I_E}{I_B} = \alpha + 1$$

$$\text{Now, } \gamma = \frac{\Delta I_E}{\Delta I_B}$$

$$\gamma = \frac{\Delta I_E}{\Delta I_E - \Delta I_C}$$

$$\gamma = \frac{1}{1 - \alpha} = \frac{1}{1 - \frac{I_C}{I_E}}$$

use know that,

$$\alpha = \frac{\beta}{1+\beta}$$

$$\gamma = \frac{1}{1-\alpha}$$

$$\gamma = \frac{1-(\beta)}{1+(\beta)}$$

$$\gamma = \frac{1+\beta}{1+\beta-\beta}$$

$$\gamma = 1+\beta$$

### \* Operation of Transistor:

N P N



V\_B

V\_C

As shown in the fig; the forward bias applied to the emitter base junction of an NPN transistor causes a lot of electrons from the emitter region to cross over to the base region. And ~~electrons~~ as the base is lightly doped with P-type impurity, the no. of holes in the base region is very small. And the no. of electrons that combine with the holes in the P-type base region is also very small. Hence, a few electrons combine with holes to constitute a base current  $I_B$ . The remaining electrons cross over into the collector region and move towards the positive terminal of the supply  $V_C$ .

So, the magnitude of the emitter current  $I_E$  is given by,


$$I_E = I_B + I_C$$

### \* Transistor as an Amplifier :

The very first requirement for a transistor to work as an amplifier is that its Emitter junction is forward biased and collector junction is reverse biased i.e. transistor operates in its active region.

How can we increase current without increasing voltage significantly.

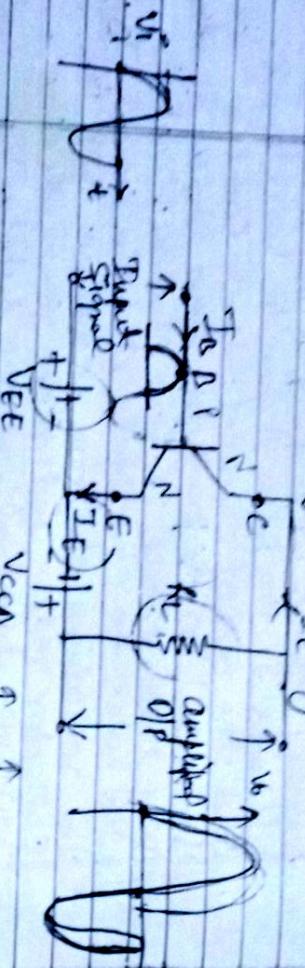The Fig below shows the basic circuit of a Common-Emitter Transistor amplifier. In this the E junction is forward biased by the negative VEE and A is reverse biased by the positive Vcc.



### \* Operation :

When a weak signal is applied between base and emitter during first half cycle, the forward bias across the junction increases and current increases. The flow of electrons from E to C through base and hence increases  $I_c$ . And this increase in  $I_c$  causes more voltage drop across the load resistor  $R_L$ .

During first half cycle, the forward bias voltage across the  $B-E$  decreases and this decreases the  $I_c$  and also the voltage drop across  $R_L$  so an amplified signal appears across  $R_L$ .

### Thyristor (SCR)

It is a Solid State device like Transistor but three terminals.

It is a Unidirectional device.


SCR is a semi-controlled device.

SCR is a charge controlled device.

SCR is a unidirectional device, which block the current from cathode to anode, but unlike diode it also block current flow from anode to cathode.

There two layer of SCR one slightly doped so that strength of junction  $J_2$  is more than strength junction  $J_1$ .

$\uparrow I_A (\text{Anode})$

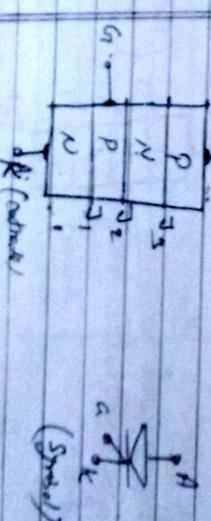

### \* Characteristics of SCR

(a) U-F characteristic  
(b) Gate characteristics

P

17/09

20

Date \_\_\_\_\_  
Page \_\_\_\_\_


b)

Static V-I Characteristics  
It has S-Mode of operation

i.

Reverse Blocking Mode:

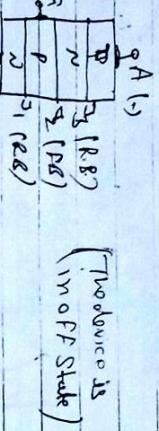Anode  $\rightarrow$  +ve terminal  
Cathode  $\rightarrow$  -ve terminal



Junctions are reverse biased.  
No forward bias.


- For this section only small amount of reverse leakage current is there (due to minority carrier) in this section.

- When the reverse voltage becomes more than Avalanche breakdown occurs at reverse bias junction  $J_1$  &  $J_2$  and device starts conducting at reverse direction.

b. Forward Blocking Mode:


Anode  $\rightarrow$  +ve terminal  
Cathode  $\rightarrow$  -ve terminal

Junctions are F.B.

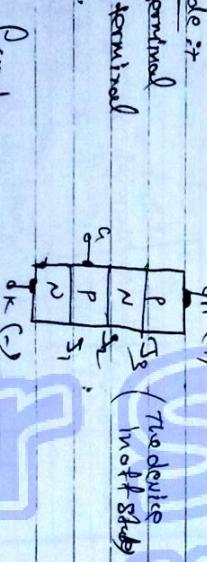

Junctions are forward biased.

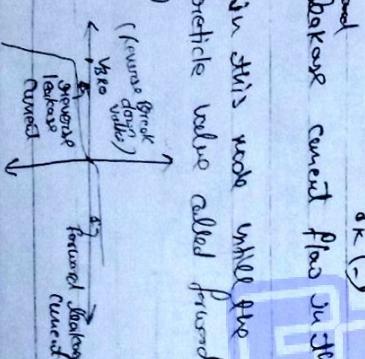- Only small amount of reverse current flows in this region.
- The device remains in this mode until the anode voltage reaches a certain value called forward Breakover voltage ( $V_{FB}$ )




forward blocking mode

reverse blocking mode

forward current

reverse current

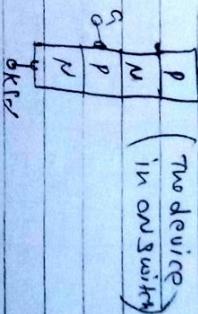- Forward Conducting Mode:
- Anode  $\rightarrow$  +ve terminal  
Cathode  $\rightarrow$  -ve terminal
- Gate pulse available
- Junctions are forward biased.



When anode voltage is greater than the forward Breakdown voltage than Avalanche breakdown occurs at  $J_2$  and device starts conducting.

- SCR starts conducting only if current through the device is greater than a minimum current called holding current during turn on process.

Some important terms in V-I characteristics

(Holding current)  $I_h$  (forward conducting current)

$I_h$   $\leftarrow$   $V_{FB}$

$I_h$   $\leftarrow$   $V_{FBO}$

$I_h$   $\leftarrow$   $V_{FBO}$

$I_h$   $\leftarrow$   $V_{FBO}$

- Locking current  $\rightarrow$  It is the minimum anode current required to turn on the SCR during turning on process. When  $\rightarrow$  Breakdown then large number of carriers are generated so, large current starts flowing. This current is locking current.

## Single-Phase Inverter :-

Page \_\_\_\_\_

• Holding voltage when the device is already in conducting state and if anode current is reduced below a minimum level, the device gets turned off. This minimum current required to turn off device is called holding current.

2) Forward Breakdown voltage :-

• It is the critical or minimum voltage required for breakdown of junction under forward bias condition for turn on device.

- When anode voltage equal to forward breakover voltage the junction  $\rightarrow$  Breakdown due to Avalanche breakdown.

• When the gate current increases the forward breakdown voltage decreases.

a) Rever Breakdown :-

• It depends on voltage and doping level, both higher must be highly doped. Small voltage required for breakdown. It is electrostatic breakdown.

3) Anode avalanche :-


• It depends or occurs due to thermal effect or temperature. It occurs in slightly doped semi-conductor junctions.

There are two types of single-phase inverters :-


- 1) Single-Phase Half-Bridge Inverter.
- 2) Single-Phase Full-Bridge Inverter.
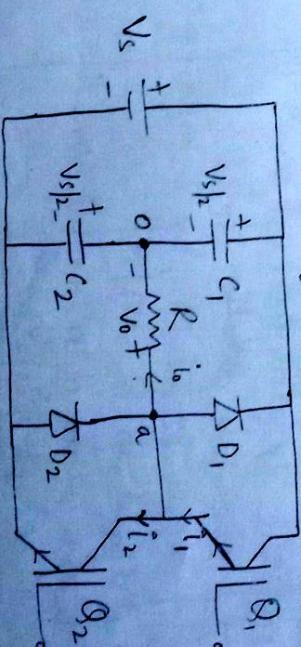
## Single-Phase Half-Bridge Inverter :-

For the half-bridge inverter circuit, the centre-tap of the DC supply is used as one of the load terminals. The centre-tap is created by the two series-connected equal-valued capacitors across the DC supply. The two switches,  $Q_1$  and  $Q_2$ , are switched alternately, at the desired output frequency,  $f_o$ .



(15)

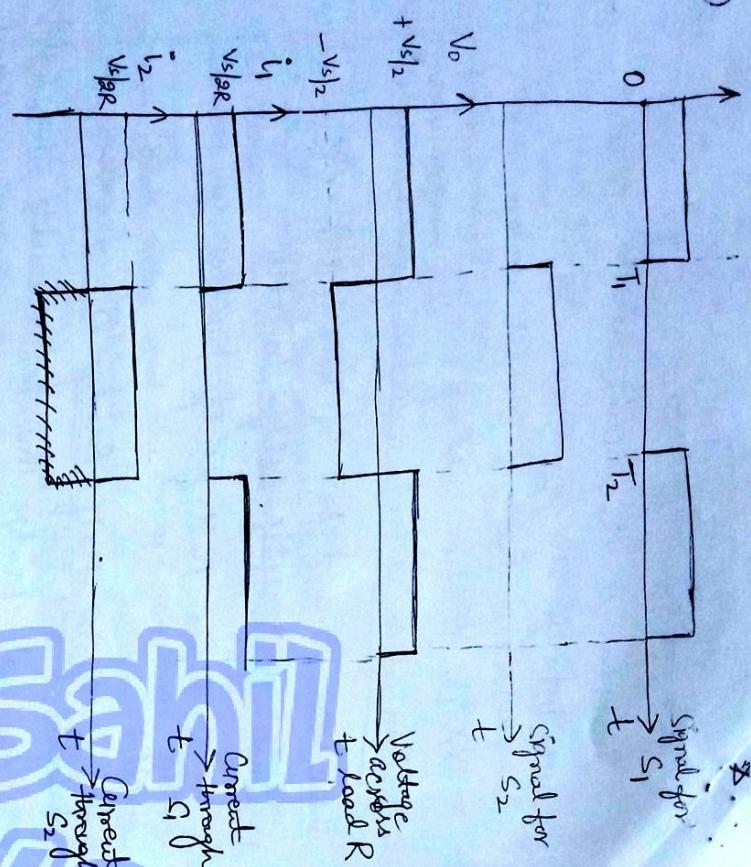

- Working :-
- The current entering node a is considered to be positive.
  - The switches  $S_1$ ,  $S_2$ ,  $S_3$  &  $S_4$  are unidirectional.
  - The switches  $S_1$  and  $S_2$  are turned on simultaneously for a duration  $0 \leq t \leq T_1$ , the voltage across load is  $V_o = V_s$  and the current flows from a to b.
  - The switching sequence is so designed that switch  $S_1$  is on for time duration  $0 \leq t \leq T_1$  and the switch  $S_2$  is on for the time duration  $T_1 \leq t \leq T_2$ .
  - When switch  $S_1$  is turned on, the instantaneous voltage across the load is  $V_o = +V_s/2$ .
  - When switch  $S_2$  is only turned on, the voltage across load is  $V_o = -V_s/2$ .

Sahil

### Single Phase Full-Bridge Inverter :-


A single phase bridge DC-AC inverter is shown in figure below. The analysis of the single phase DC-AC inverter is done by taking the following assumptions into account as :

- The current entering node a in figure is considered to be positive.




$$S_1 - S_2 = \text{ON} ; S_3 - S_4 = \text{OFF} \Rightarrow V_o = V_s.$$

- When the switches  $S_3$  &  $S_4$  are turned on for a duration  $T_1 \leq t \leq T_2$ , the voltage across the load is reversed i.e.  $V_o = -V_s$  and current flows from b to a.
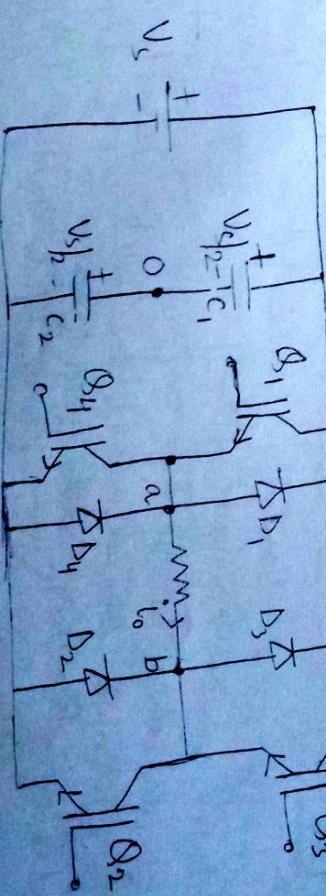
$$S_1 - S_2 = \text{OFF} ; S_3 - S_4 = \text{ON} \Rightarrow V_o = -V_s.$$



(16)

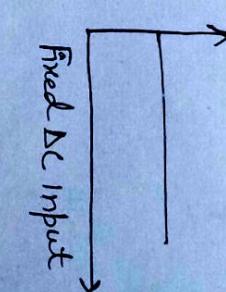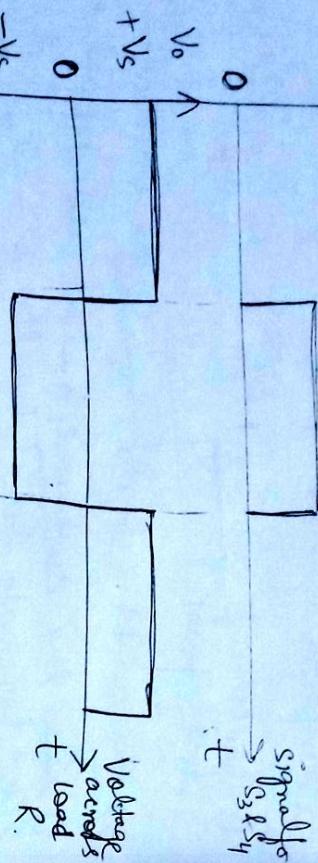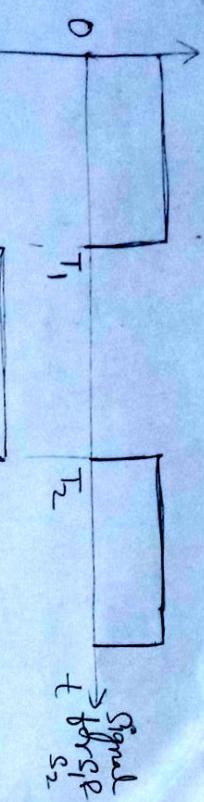


We can control and vary a constant DC voltage

with the help of a chopper. Chopper can increase or decrease the DC voltage level at its opposite side. So, it is also known as DC Transformer.
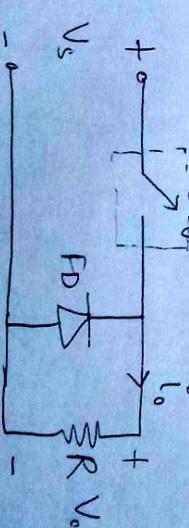
### 1) Step down chopper or Buck converter :-

Step down chopper is used to reduce the input voltage level at the output side as shown in the circuit diagram below :-




When CH is turned ON,  $V_s$  directly appears across the load i.e.  $V_o = V_s$

### DC-DC converter or Chopper :-

Chopper is a basically static power electronics device which converts fixed DC voltage / power to variable DC voltage or power. It is nothing but a high speed switch which connects & disconnects the load from source at a high rate to get variable DC chopped voltage at the output


When  $C_H$  is turned off,  $V_s$  is disconnected from the load i.e.  $V_o = 0$ .

The voltage waveform is shown below:-

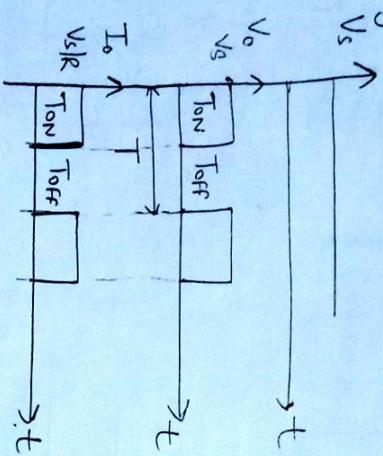
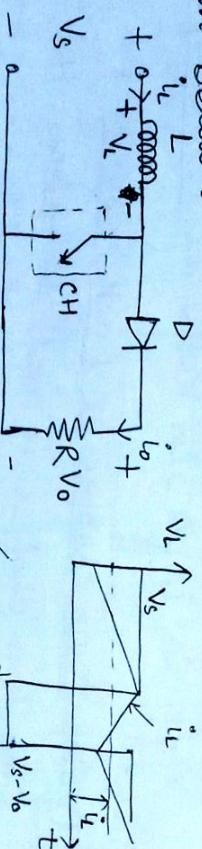
## 2) Step-up chopper or Boost Converter :-


Step-up chopper is used to increase the input voltage level of its output side as shown in the circuit diagram below :-



When the switch  $C_H$  is closed for time duration  $T_1$ , the inductor current rises and the energy is stored in the inductor. If the switch  $C_H$  is opened for time duration  $T_2$ , the energy stored in the inductor is transferred to the load via the diode D and the inductor current falls.

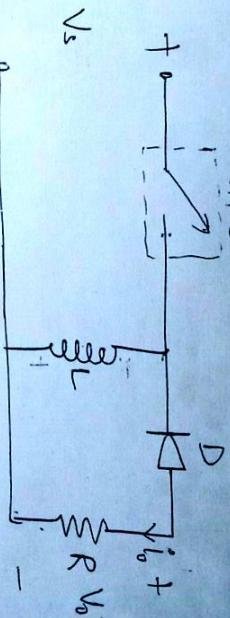(24)


Buck-Boost Converter :-  
With the help of Buck-Boost converter, we can increase or decrease the input voltage level at its output side as per our requirement as shown in the circuit diagram below :-



When  $C_H$  is ON, the source voltage  $V_s$  is applied across the inductor  $L$  and it will be charged and stored energy in the inductor  $\mathcal{Q}_0$ ,  $V_L = V_s$ .

When chopper is OFF, inductor  $L$  reverses its polarity and discharges through load and diode D.

$$\text{So, } V_o = -V_L$$

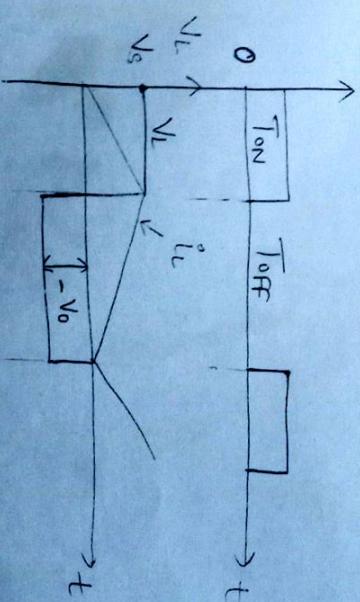

## \* Power Measurement :-

Power is the rate at which work is done.  
In a purely resistive circuit, the voltage & current change direction at the same time.  
So, the formula is :

$$P = V_{rms} I_{rms}$$

## Power meter :-

Power meter is a multi-function device that measures precisely continuous current, alternative current, intensity of DC or AC and power in Watts.


## \* Wattmeter :-

Wattmeter is an instrument used to measure the electrical power. The traditional form of Wattmeter is called as dynamometer Wattmeter.

The Wattmeter has two sets of coils :

1. Current Coil :- One coil is fixed and is made in two identical parts. It is made of heavy gauge copper wire. So, it has low resistance.

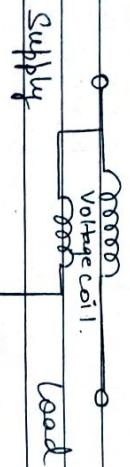d. Voltage coil :- The other coil which is known as Voltage coil is wound from fine gauge wire. So it has relatively high resistance. It is placed between the two parts of the current coil.



→ The current coil is connected in series with the load so that the circuit current flows through it.

→ The voltage coil is connected in parallel with the load.

→ Both the coils will produce magnetic field and these fields interact to each other and produce a deflecting torque on the voltage coil.

→ The interacting fields are proportional to the circuit voltage & current so the produced deflecting torque is proportional to the product of circuit voltage and current  $\propto VI$  which is nothing but a circuit power.


→ A dynamometer wattmeter reads both ac & dc power.

**A**

Measurement of three phase Power :-

Various methods are used for measurement of three-phase power in three phase circuits on the basis of number of wattmeters used.

### 1. Three Wattmeter method :-

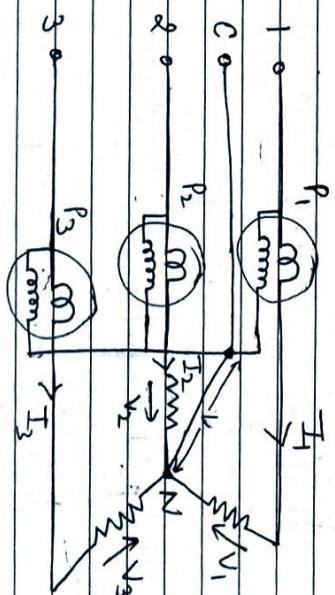

The above figure shows a three phase four wire system having a current coil of all the three wattmeters marked on one, two and three connected to respective phases.

Pressure coils of all the three wattmeters are connected to common point at neutral wire. It is clearly seen that each wattmeter will give reading as product of phase current and line voltage which is a phase power.

The resultant sum of all the readings of wattmeter will give the total power of the circuit.

So,

$$\begin{aligned} P &= P_1 + P_2 + P_3 \\ P &= I_1(V_1 - V) + I_2(V_2 - V) + I_3(V_3 - V) \\ P &= \sqrt{I_1^2 R_1} + \sqrt{I_2^2 R_2} + \sqrt{I_3^2 R_3} \end{aligned}$$

$$\therefore I_1 + I_2 + I_3 = 0$$


2. Measurement of power by two wattmeter method:

In this method, we have two types of connections:-

1. Star connection.

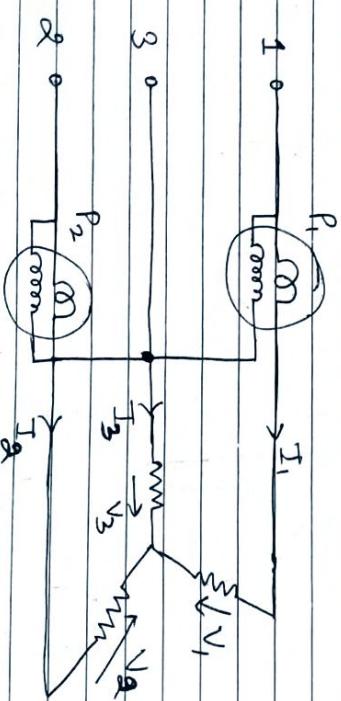2. Delta connection.

When the load is star connected, the diagram is shown below :-



Thus, the total power of the circuit is the sum of the reading of both the wattmeters.

$$P = P_1 + P_2$$

$$P = I_1(V_1 - V) + I_2(V_2 - V)$$

$$P = I_1V_1 - I_1V_3 + I_2V_2 - I_2V_3$$

$$P = I_1V_1 + I_2V_2 - V_3(I_1 + I_2)$$

$$P = I_1V_1 + I_2V_2 + I_3V_3$$

According to Kirchoff's law :-

$$I_1 + I_2 + I_3 = 0$$


$$\therefore I_1 + I_2 = -I_3$$

For star connected load, it is clear that the reading of wattmeter one is product of phase current and voltage difference ( $V_2 - V_3$ ).

Similarly, the reading of wattmeter two is the product of phase current and the voltage difference ( $V_2 - V_3$ )

When the load is connected in delta, the

Diagram is shown below :-

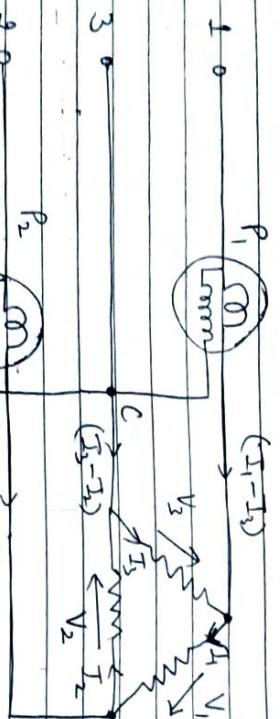

So, the reading of wattmeter one is given by,

$$P_1 = V_1 I_1 - V_3 I_3$$

and the reading of wattmeter two is given by,

$$P_2 = V_2 I_2 - V_1 I_1$$

So, the total power measured by the two wattmeter is the sum of the reading of the both wattmeters.

$$P = P_1 + P_2$$

$$P = V_2 I_2 + V_3 I_3 - V_1 I_1$$

$$P = V_2 I_2 + V_3 I_3 - V_1 I_1$$

$$\text{Express & solve}$$

$$P = V_2 I_2 + V_3 I_3 - V_1 I_1$$

$$P = V_2 I_2 + V_3 I_3 - V_1 I_1$$

Or according to Kirchoff's law :-

$$\begin{cases} V_1 + V_2 + V_3 = 0 \\ V_2 + V_3 = -V_1 \end{cases}$$

### (3) One Wattmeter method :-

The main limitation of this method is it cannot be applied on unbalanced load.

So, in balanced condition,

We have,  $I_1 = I_2 = I_3 = I$

$$\& V_1 = V_2 = V_3 = V$$

As shown in the diagram below, the load is star connected:

$$R \rightarrow P_1 = I^2 R$$

$$P = \sqrt{3} V I \cos \phi$$

A Energy Consumption formula :-

Energy consumption is the consumption of energy or power of a system using supply. The consumption is done in Kilogram of oil equivalent per year (Kgoea), Giga Joule per year and in Watts.

So, the energy consumption formula is given by,

$$E(\text{kwh/day}) = \frac{P \times t}{1000}$$

Where,  $E$  is the energy in kilowatt-hours (kWh).  $P$  is power in Watts.  $t$  is time in hours per day.

In the diagram, we can see there are two switches marked as (1-3) and (1-2). By closing the switch (1-3), we get the reading of voltmeter as:

$$P_1 = \sqrt{3} V I \cos(30 + \phi)$$

$$P_1 = \sqrt{3} V I \cos(30 + \phi)$$

Now by closing the switch (1-2), we get the reading of voltmeter as;



$$V_y$$

$$P_2 = \sqrt{3} V I \cos(30 - \phi)$$

Ques. Calculate the energy consumption in a system that consumes 190 Watts of power and works for 3 hrs a day.

Total power is given by;

$$P_2 = P_1 + P_2$$

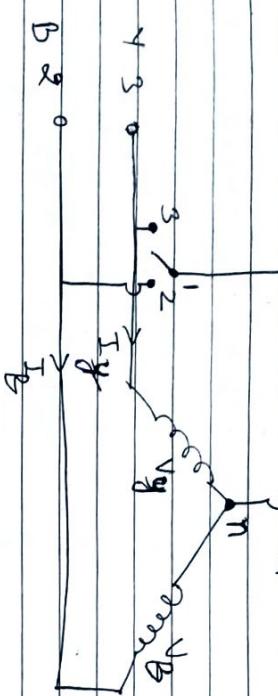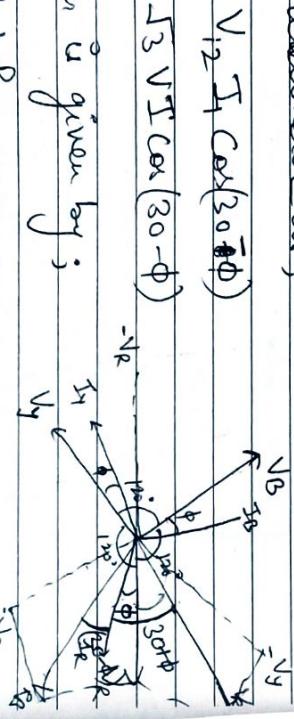

Solution :-

Given :  $P = 190 \text{ W}$   
 $t = 3 \text{ hr/day}$ .

so, The energy consumption is given by :

$$E(\text{kWh/day}) = \frac{P \times t}{1000} \text{ kWh}$$

$$E(\text{kWh/day}) = \frac{190 \times 3}{1000} \text{ kWh}$$

$$E(\text{kWh/day}) = 0.57 \text{ kWh}$$

## \* Introduction :-

An electrical installation is a combination of electrical equipment installed to fulfill a specific purpose.

In dealing with the electrical installation, it is necessary to ensure the safety of personnel as well as the protection of equipment from the electrical faults.

The most popular methods of protection are:

- (1) Earthing or grounding of equipment.
- (2) Use of fuses or Circuit Breakers (ie MCB & MCCB)
- (3) Use of earth leakage and residual current circuit breakers.

## \* Switchgear :-

Switchgear is the combination of electrical disconnect switches, fuses or circuit breakers used to control, protect and isolate electrical equipment.

A switchgear or electrical switchgear is a generic term includes all the switching devices associated with mainly power system protection.

High-voltage switchgear was invented at the end of the 19<sup>th</sup> century for operating motors and other electric machines and now be used with voltage up to 1,100 kV.

Switchgear in substations are located on both the high and low voltage sides of large power transformer.

### \* Features of Switchgear :-

- (1) Complete reliability
- (2) Absolute certain discrimination.
- (3) Quick operation
- (4) Provision for manual control.

### \* Classification of Switchgear :-

Switchgear can be classified on the basis of volt level into the following :-

#### (1) Low Voltage Switchgear :-

The electrical switchgear rated up to 1 kV is termed as low-voltage switchgear. This includes low-voltage circuit breakers, switches, HRC fuse, MCB, ELCB, MCCB etc.

#### (2) Medium-Voltage switchgear :-



The electrical switchgear rated from 3 kV to 36 kV

is termed as medium-voltage switchgear. It includes metal enclosed indoor type, metal enclosed outdoor type, oil CB, SF<sub>6</sub> and vacuum CBs.
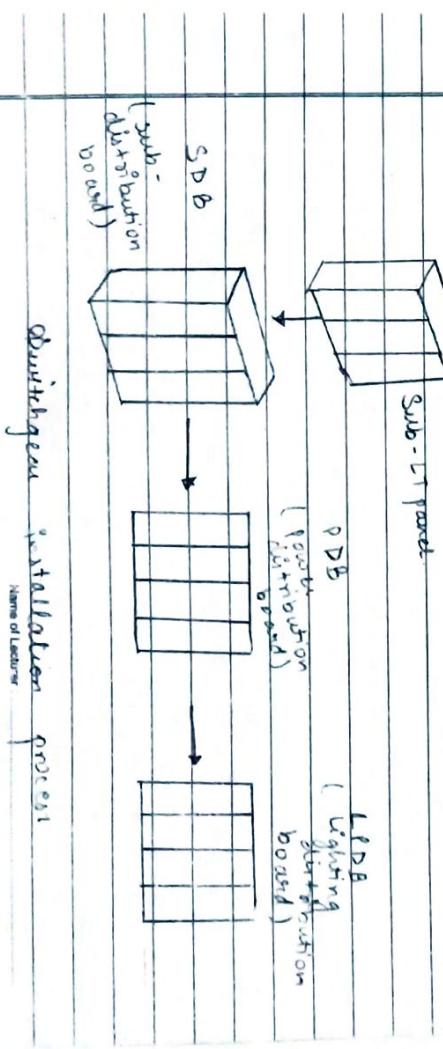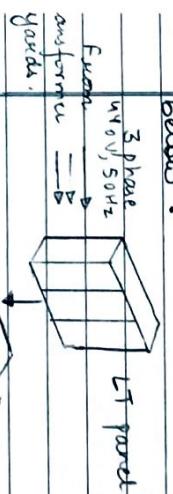
#### (3) High Voltage switchgear :-

The electrical switchgear rated beyond 36 kV is termed as high-voltage switchgear. In this circuit breakers special care is taken during designing as the voltage level is very high.

An installation process of a switchgear is shown below :-



## ★ Switch Fuse Unit (SFU) :-

→ SFU is a switching device having one switch or one fuse unit. When we operate the breaker the contacts will get close through switch and then the supply will pass through the fuse up to the output.

- It is made of power fuse rating (80 - 250 - 400 A) and a switch which can be operated from outside using extended rotary handle to rotate the shaft which is inside it.
- SFU is used for protecting power and control circuit depends on the current rating required.
- It has been used to trip the circuit particularly for high capacity tripping.
- It is used in industrial, residential and commercial buildings for electrical fittings.

Rating current : 16 - 32 - 63 - 100 - 200 Amp.  
Rated Voltage : 240 / 415 V AC.

## ★ Miniature Circuit Breaker (MCB) :-

MCB is an automatically operated electrical switch designed to protect the electrical appliance and human beings from electrical shocks & faults.

These days MCB is more commonly used in low voltage electrical networks than fuse. MCB is used for rating upto 100 Amps in the motor feeders. In domestic sector, its rating is upto 100amps.

## ★ Working of MCB :-

Basically, MCB is operated under two effects of overcurrent.

- (1) Thermal effect
- (2) Short-circuit condition.

The thermal operation is achieved with a bimetallic strip, whenever continuous over-current flows through MCB, the bimetallic strip is heated and deflects by bending. This deflection of bimetallic strip releases mechanical latch. And thus latch is attached with operating lever, it causes to open the MCB contacts.

During short circuit condition, sudden rising of current, causes electromechanical displacement of plunger associated with tripping coil or solenoid of MCB. The plunger strikes the trip lever causing immediate release of latch and consequently opens the MCB contacts.

## \* Construction of MCB :-

MCB construction is very simple, robust and maintenance free. Generally a MCB is not repaired or maintained, it just replaced by new one when required. A MCB has normally three main parts

- (1) Frame
- (2) Operating lever
- (3) Trip unit.
- (4) Bimetallic strip
- (5) Fixed and moving contacts.

During the operation of MCB, the electric current carrying path of a MCB is arranged in series like firstly bimetallic strip — latch mechanism — trip unit — fixed and moving contacts and lastly the operating lever is outside the MCB.

So, whatever may be the condition or effect, may be due to deformation of bi-metallic strip, due to increased or sudden over current by short circuit condition of trip coil or may be due to manual operation, the same latent point is displaced and same spring is released which ultimately responsible for movement of the MCB.

## \* Advantages of MCB over fuse :-

- (1) It automatically switches off the electrical circuit during abnormal condition but fuse does not sense
- (2) MCB is much more sensitive to over current than fu

(3) Quick restoration of supply cannot be possible in case of fuse.

(4) Handling MCB is more electrically safe than fuse.

(5) In MCB, the switch operating knob comes at its off position during tripping and can be easily identified but in case of fuse, the fuse wire should be checked.

The only disadvantage of MCB over fuse is that this system is more costlier than fuse unit system.

## \* Moulded case Circuit Breaker (MCCB) :-

MCBs are electro-mechanical devices which protect a circuit from over-current and short circuit with in the range of 32 amps to 3000 amps.

Their primary functions are to provide a means to manually open a circuit and automatically open a circuit under overload or short circuit conditions.

MCBs can be easily reset after a fault and offers improved operational safety and convenience without incurring operating cost.

## \* Working of MCCB :-

MCCBs generally have a.

- Thermal element for over-current and
- Magnetic element for short circuit release.

Like MCB, the MCCB will operate under thermal effect and short-circuit effect.

The thermal effect is achieved by deformation of bimetallic strip by releasing the spring-loaded trigger which in turn will cut off the electrical circuit.

During short-circuit condition, sudden rising of current causes the displacement of the bimetallic strip directly and releasing the spring-loaded trigger which return will cut off the MCCB contact.

MCCBs are now available with a variety of releases and these are given below:-

### (1) Thermal Magnetic Release :-

It is used bimetallic and electro-magnetic assemblies to provide over-current protection. For higher level over-currents, instantaneous trip allows MCCBs to interrupt suddenly.

## (2) Electronic Release MCCB :-

MCBs uses power electronic circuitry to provide over-current protection. Mainly a current transformer (CT) is used as an MCCB release in this stage which act first during the short-circuit condition.

## (3) Microprocessor Release MCCB :-

Microprocessor release MCBS uses microprocessors to provide the over-current protection. It works on monitoring of current with true value of current and give the tripping effect. It is highly flexible and reliable in comparison to other releases.

## \* Earth Leakage Circuit Breaker (ELCB) :-

Earth leakage circuit breaker (ELCB) is a device used to directly detect currents leaking to earth from an installation and cut the power.

There are two types of ELCBs:-

### (1) Voltage Earth leakage Circuit Breaker (V-ELCB).

Name of Lecturer: .....

### (2) Current Earth leakage Circuit Breaker (C-ELCB).

(1) Voltage Base ELCB :-

Voltage ELCB is a voltage operated circuit breaker. The device will function when the current passes through the ELCBs.


It contains a relay coil which is connected to the metallic load body at one end and it is connected to ground wire at the other end.

If the voltage of the equipment body rises which could cause the difference between earth & load body voltage, as a result the danger of electric shock could occur. This voltage difference will produce an electric current from the load metallic body passes the relay coil and to the earth.

When the voltage on the equipment metallic body rises to the danger level which exceed to 50V the housing current through relay coil could move the relay contact by disconnecting the supply current to avoid from any danger electric shock.

The ELCB detects faults from live to the earthing wire within the installation it protects. If sufficient voltage appears across the ELCB's sense coil, it will switch off the power and remain off until manually reset.

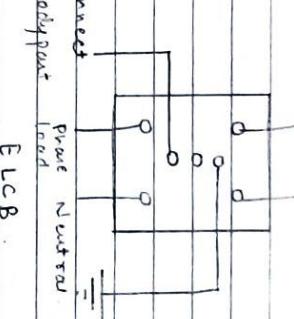The wiring diagram of V-ELCB is shown below:-



→ The way to identify an V-ELCB is by looking for green and yellow earth wires entering the device.

The ELCB is the brain for the shock protection and the grounding is the backbone. Therefore, without a functional grounding there is no protection against electrical shocks in your house even if you have purchased the ELCBs.


(2) Current-operated ELCB (RCD) :-

Current-operated ELCBs are generally known as Residual-current devices (RCD). They provide protection against earth leakage. Both the input conductors she run through a sensing coil. Any imbalance of the currents means the magnetic field does not perfectly cancel. The device detects

the imbalance and trip the contact.
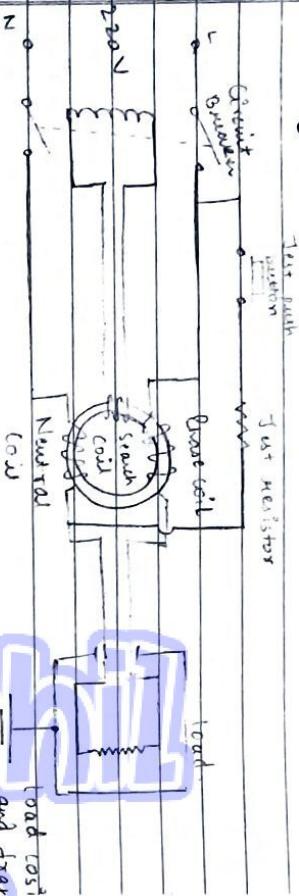
### \* Working of RCD :-

The typical circuit of RCD is shown below as



RCD circuit.

→ The supply coil, the neutral coil and the search coil all wound on a common former core.

During the normal operation, the same current passes through the phase coil, the load and return back through the neutral coil. Both the phase and neutral coils are wound in such a way that they will produce an opposing magnetic flux. With the same current passing through both coils, their magnetic effect will cancel out each other under a normal condition.

During the fault operation, or a leakage to earth in the load circuit, or anywhere between the load circuit and the output connection of the RCD the

The current returning through the neutral coil has been reduced. Then the magnetic flux inside the transformer core is not balanced anymore so the total sum of the opposing magnetic flux is no longer zero. Thus net remaining flux is what we call a residual flux.

The periodically changing residual flux inside the transformer core creates path with the winding of the search coil. This action produces an emf across the search coil which in turn producing a current inside the winding of the trip circuit. This current operates the trip coil of the circuit breaker.

### Sensitivity of RCB :-

→ High sensitivity :- 6-10-30 mA (for direct-contact fire, injury protection)


Medium sensitivity :- 100-300-500-1000 mA (for fire protection).

Low sensitivity :- 3-10-30 A (for protection of machine).
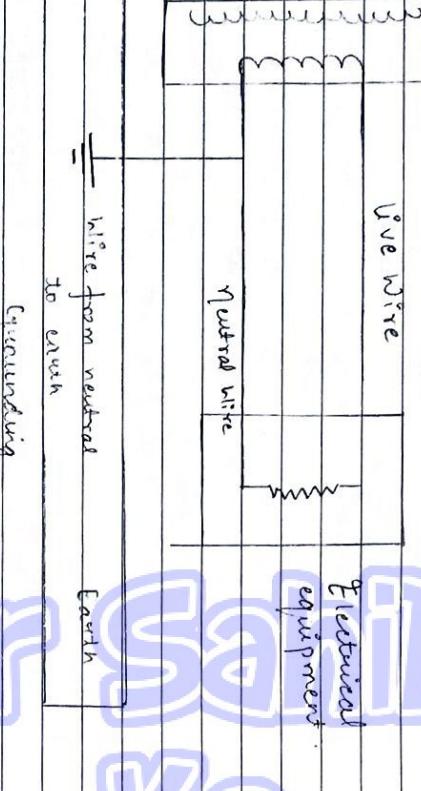
## \* Earthing System / Grounding System :-

In an electrical installation, an earthing system or grounding system connects specific parts of the installation with the earth's conductive surface for safety and functional purposes.

The diagram of earthing system is shown below:



Current supply

Equipment

Earth

Neutral wire

Live wire

Equipment

Earth

Neutral wire

the system from damage and shock.

### \* Importance of earthing :-

The earthing is essential because of the following reasons :-

- Protects the personnel from the short circuit current.
- Provides the easiest path to the flow of short circuit current.
- Protects the machinery and personnel from the high voltage surges and lightning discharge.

### \* Difference between earthing and grounding

#### Grounding

Definition: The current carrying part is connected to the ground.

Location: Between neutral & Earth.

Symbol:



Potential: It does not have zero potential.

It has zero potential.

Application: Provide the return path to current.

Discharges the electrical energy to the earth.

Examples: Neutral of Generator and Power transformers connected to the ground.

The enclosure of the appu connected to the ground

#### Earthing

The body of the equipment connected to the ground

Between equipment body & ea

